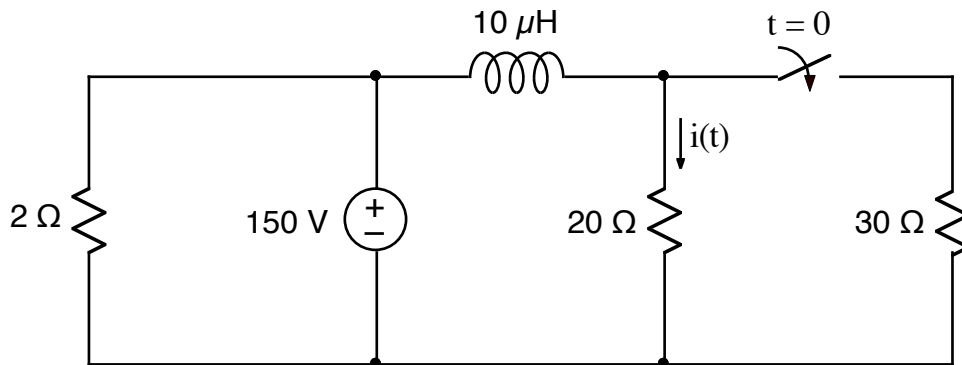



Ex:



After being closed for a long time, the switch closes at $t = 0$.


Find $i(t)$ for $t > 0$.

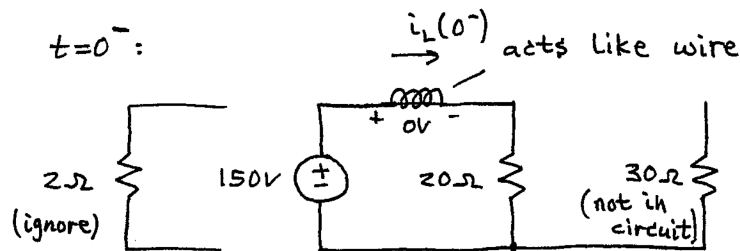Sol'n: At $t = 0^-$, switch is open and $L = \text{wire}$. We note that the 2Ω resistor is a 2nd circuit across the $150V$ source and may be ignored.



$$i_L(0^-) = \frac{150V}{20\Omega} = 7.5A$$

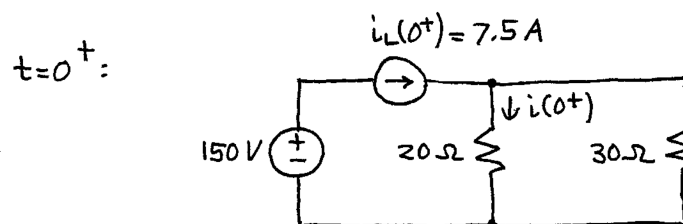At $t = 0^+$, switch is closed and we model L as current source with $i_L(0^+) = i_L(0^-) = 7.5A$.




We have a current divider.

$$i(0^+) = i_L(0^+) \cdot \frac{30\Omega}{20\Omega + 30\Omega} = 7.5A \cdot \frac{3}{5} = 4.5A$$

As $t \rightarrow \infty$, switch is closed and $L = \text{wire}$.

$t \rightarrow \infty$:

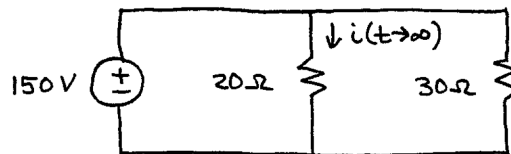


We have 150V across the 20 ohm resistor.

$$i(t \rightarrow \infty) = \frac{150V}{20\Omega} = 7.5A$$

The time constant is $\frac{L}{R_{Th}}$ where we look

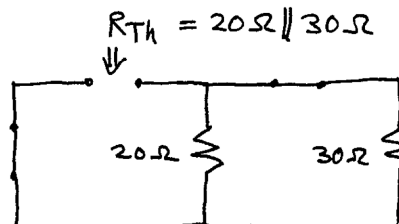into the circuit from the terminals where L is attached. We can find R_{Th} by turning off the 150V source and seeing what R value we have looking into the circuit from the terminals where L is attached.



Note: switch is closed since $t > 0$.

$$R_{Th} = 20\Omega \parallel 30\Omega = 12\Omega$$

The time constant is $\frac{L}{R_{Th}} = \frac{10\mu\text{H}}{12\Omega} = \frac{5}{6}\mu\text{s}$.

We plug values into the general form of solution:

$$i(t>0) = i(t\rightarrow\infty) + [i(t=0^+) - i(t\rightarrow\infty)] e^{-t/\frac{L}{R_{Th}}}$$

$$i(t>0) = 7.5\text{A} + [4.5\text{A} - 7.5\text{A}] e^{-t/\frac{5}{6}\mu\text{s}}$$

$$\text{or } i(t>0) = 7.5\text{A} - 3\text{A} e^{-t/\frac{5}{6}\mu\text{s}}$$