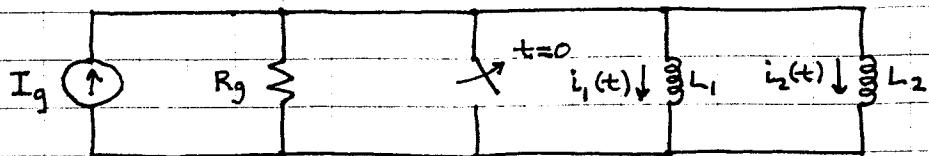


ex:



No energy stored in L_1 and L_2 when switch opens

- a) Find $i_1(t \geq 0)$ and $i_2(t \geq 0)$. b) Find $i_1(t \rightarrow \infty)$ and $i_2(t \rightarrow \infty)$


ans: a) $i_1(t \geq 0) = I_g \frac{L_2}{L_1 + L_2} (1 - e^{-t/\tau})$ where $\tau = L_1 \parallel L_2$

$$i_2(t \geq 0) = I_g \frac{L_1}{L_1 + L_2} (1 - e^{-t/\tau})$$

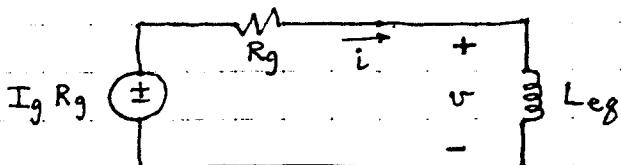b) $i_1(t \rightarrow \infty) = I_g \frac{L_2}{L_1 + L_2}$ $i_2(t \rightarrow \infty) = I_g \frac{L_1}{L_1 + L_2}$

sol'n: a) Take Thvenin equiv. of I_g and R_g on left.

Solve for v across L 's by replacing L 's with equivalent L :



circuit for $t \geq 0$

L 's in parallel give $L_{eq} = L_1 \parallel L_2 = \frac{L_1 L_2}{L_1 + L_2}$.

(L 's in parallel are like R 's in parallel in terms of the formula we use.)

Now we use the general solution for $v(t \geq 0)$:

$$v(t \geq 0) = v(t \rightarrow \infty) + [v(0^+) - v(t \rightarrow \infty)] e^{-t/\tau}$$

time constant

To find $v(0^+)$, we use $i_1(0^+) = i_1(0^-)$ and $i_2(0^+) = i_2(0^-)$. But $i_1(0^-) = i_2(0^-) = 0$ since no energy is stored in L_1 and L_2 at $t=0$.

a) cont.

Since $i_1(0^+)$ and $i_2(0^+) = 0$, we must have no current through R_g at $t = 0^+$.

\therefore At $t = 0^+$, we have no v drop across R_g .

$$\therefore v(t=0^+) = V_{Th} = I_g R_g$$

For $v(t \rightarrow \infty)$ we observe that the L's act like wires, and $v(t \rightarrow \infty) = 0$.

Plugging into the general sol'n gives

$$v(t \geq 0) = I_g R_g e^{-t/(L_g/R_g)}$$

Note: The time constant for circuit with L and R is L_g/R_{Th} . Taking the Thvenin equivalent always gives the needed R.

Now we can also write down a formula for $i(t) = i_1(t) + i_2(t)$ for $t \geq 0$:

$$i(t \geq 0) = i(t \rightarrow \infty) + [i(0^+) - i(t \rightarrow \infty)] e^{-t/(L_g/R_g)}$$

Note: All i's and v's have same time constant.

$$\text{We know } i(0^+) = i_1(0^+) + i_2(0^+) = i_1(0^-) + i_2(0^-) = 0$$

At $t \rightarrow \infty$, the L's act like wires, giving $i = I_g$.

$$\therefore i(t \geq 0) = I_g [1 - e^{-t/(L_g/R_g)}]$$

Now we determine how $i(t \geq 0)$ is divided between the two L's to give $i_1(t \geq 0)$ and $i_2(t \geq 0)$.

a) cont.

Since both L's have same V across them, we have

$$v = L_1 \frac{di_1}{dt} = L_2 \frac{di_2}{dt} \quad \therefore \frac{\frac{di_1}{dt}}{\frac{di_2}{dt}} = \frac{L_2}{L_1}$$

Now we calculate currents:

$$i_1(t) = \int \frac{di_1}{dt} dt = \int \frac{L_2}{L_1} \frac{di_2}{dt} dt = \frac{L_2}{L_1} \int di_2$$

$$\text{or } i_1(t) = \frac{L_2}{L_1} i_2(t)$$

$$\text{Also, } i_1(t) + i_2(t) = i(t).$$

$$\text{Solving these two eqns gives } i_1(t) = \frac{L_2}{L_1 + L_2} i(t)$$

$$i_2(t) = \frac{L_1}{L_1 + L_2} i(t)$$

$$\text{Thus, } i_1(t \geq 0) = I_g \frac{L_2}{L_1 + L_2} \left(1 - e^{-t/(L_{eg}/R_g)} \right)$$

$$i_2(t \geq 0) = I_g \frac{L_1}{L_1 + L_2} \left(1 - e^{-t/(L_{eg}/R_g)} \right)$$

$$b) \text{ At } t \rightarrow \infty \text{ we have } e^{-t/(L_{eg}/R_g)} \rightarrow 0.$$

$$\therefore i_1(t \rightarrow \infty) = I_g \frac{L_2}{L_1 + L_2}$$

$$i_2(t \rightarrow \infty) = I_g \frac{L_1}{L_1 + L_2}$$