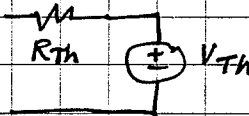


switch has been open for a long time when it closes at $t=0$. Find $i_o(t)$, $t \geq 0$.


sol'n: Find $i_o(t=0^-)$. Then $i_o(t=0^+) = i_o(t=0^-)$ since current in L cannot change instantly. Use Thevenin equivalents for right side of circuit, as needed.

Qualitative sol'n: L looks like wire at $t=0^-$ since circuit has been sitting for a long time.

Thevenin equiv for right side will reduce it to:




Then we will have an RL problem:

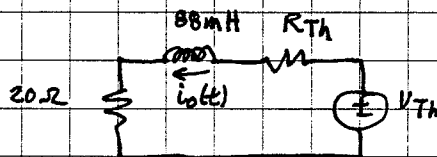

We then plug in initial $i_o(t)$ and write differential equation by summing V 's around loop.

Quantitative sol'n:

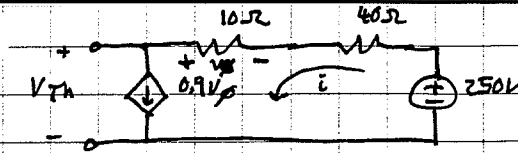Find Thevenin equiv when switch is open. First find V_{Th} for open circuit.



$i = 0.9V_\phi$ since current source is in series with 10Ω and 40Ω


$$\text{Also, } i = \frac{250V - V_{Th}}{10\Omega + 40\Omega} \quad \text{and} \quad V_\phi = -10\Omega \cdot i$$

$$\therefore V_\phi = -10\Omega \cdot 0.9V_\phi = -9V_\phi$$

Only solution $V_\phi = 0$. Then $i = 0$, $V_\phi = 0$, current source draws no current.

Thus, $V_{Th} = 250V$.

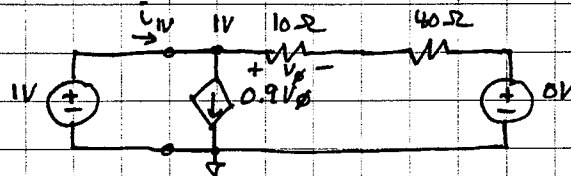Now find R_{Th} by connecting 1V source at the two terminals on left and turning 250V (independent) source to 0V.



We have 1V across $10\Omega + 40\Omega$. By V divider formula $V_\phi = 1V \cdot \frac{10\Omega}{10\Omega + 40\Omega} = 0.2V$.


$$\text{Total } i_{1V} = 0.9V_\phi + \frac{1V}{10\Omega + 40\Omega} = 0.9 \cdot 0.2A + 0.02A$$

$$i_{1V} = 0.2A$$

$$R_{Th} = \frac{1V}{i_{1V}} = 5\Omega$$


$$\begin{aligned} \text{Now } i_0(t=0^-) &= \frac{V_{Th}}{R_{Th} + 20\Omega} \quad (\text{see circuit with Thevenin on preceding page}) \\ &= \frac{250V}{5\Omega + 20\Omega} = \frac{250V}{25} = 10A \end{aligned}$$

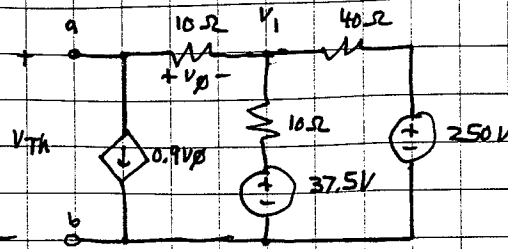Now find Thevenin equiv after switch closed.




Once again we observe that $V_p = 0$, $0.9V_p = 0$ is a solution. So we just find V_1 , as labeled on circuit, and we have $V_{TH} = V_1$, since $V_p = 0V$

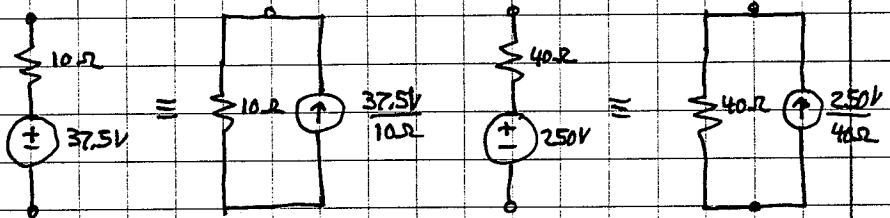
Use v-divider to find V_1 , or we can use Norton equivalents:



Put the Norton equivalents together:


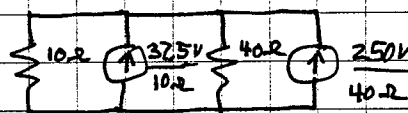


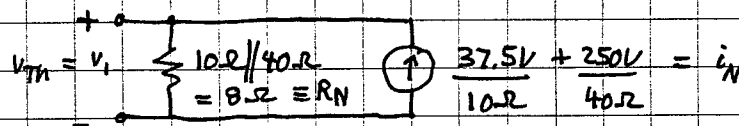Combine current sources (add them) and use $10\Omega // 40\Omega$.



$$V_{TH} = V_1 = i_N \cdot R_N = (3.75 + 6.25)A \cdot 8\Omega = 80V$$

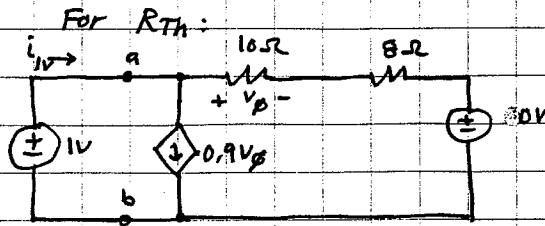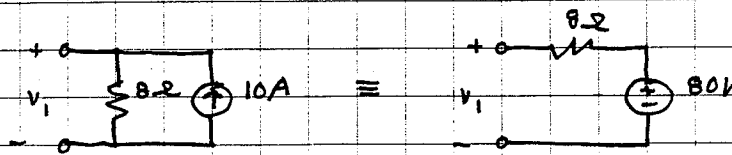Now attach IV at terminals of the Norton converted back to Thevenin equiv plus 10Ω and $0.9V_p$. Then turn V_{TH} to $0V$




As before $v_0 = 1V \cdot \frac{10\Omega}{10\Omega + 8\Omega} = \frac{10}{18}V$
we have V -divider


$$i_{1V} = 0.9V_0 + \frac{1V}{10\Omega + 8\Omega} = 0.9 \cdot \frac{10}{18} + \frac{1}{18} = \frac{10}{18} A$$

$$R_{Th} = \frac{1V}{i_{1V}} = \frac{18}{10} = 1.8\Omega$$

Now we can solve the RL problem:

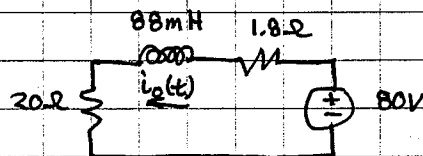

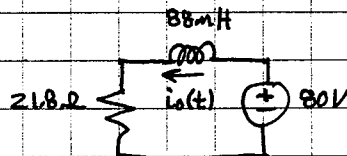If all we need is $i_0(t)$, we can combine R 's:



$$i_0(t) \cdot 21.8\Omega + 88mH \cdot \frac{di_0(t)}{dt} - 80V = 0V$$

↑
sum V 's around loop

Solution is always of form $i_0(t) = i_0(t=0^+) + \frac{(i_0(t \rightarrow \infty) - i_0(t=0^+))}{(1 - e^{-t/4ms})}$

$$i_0(t \rightarrow \infty) = \frac{80V}{21.8\Omega} \quad (L \text{ like wire as } t \rightarrow \infty) \quad i_0(t \rightarrow \infty) = 3.7 A$$

$$L/R = \frac{88mH}{21.8\Omega} = 4.0ms$$

$$\therefore i_0(t) = 10 + (3.7 - 10) (1 - e^{-t/4ms})$$