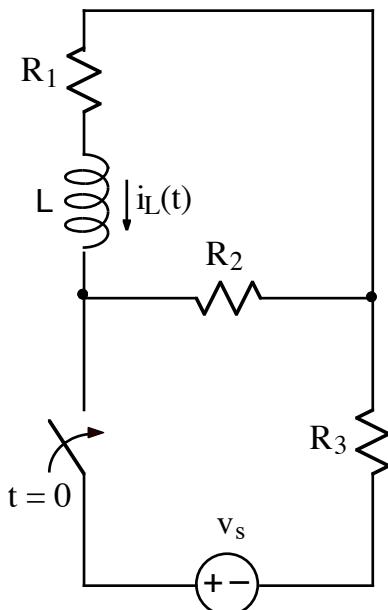



Ex:



- Write an expression for $i_L(t = 0^+)$
- Write an expression for $i_L(t > 0)$ in terms of R_1, R_2, R_3, v_s , and L .

Sol'n: a) $i_L(0^+) = i_L(0^-)$

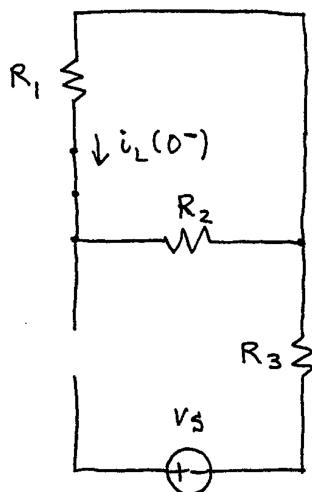At $t = 0^-$, L acts like wire.
Switch is open at $t = 0^-$.



There is no power source in the R_1, R_2 loop, and v_s is disconnected.
 $\therefore i_L(0^-) = 0A$

Thus, $i_L(0^+) = i_L(0^-) = 0A$


b) For $i_L(t>0)$, we use the general

form of sol'n for RL problems:

$$i_L(t>0) = i(t \rightarrow \infty) + [i_L(0^+) - i_L(t \rightarrow \infty)] e^{-t/L/R_{Th}}$$


$t=0^+$: We model L as i-src with value $i_L(0^+) = i_L(0^-) = 0 A$.

Switch is closed.

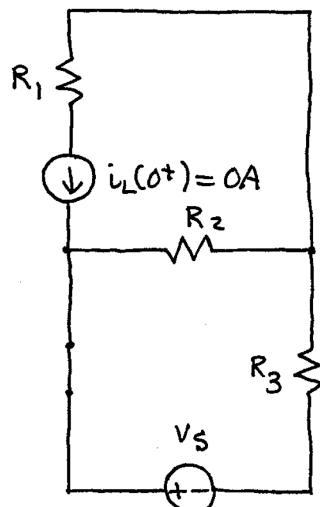

Since the quantity we are looking for is $i_L(0^+)$, we do not have to solve the circuit, but this is the circuit we would use.

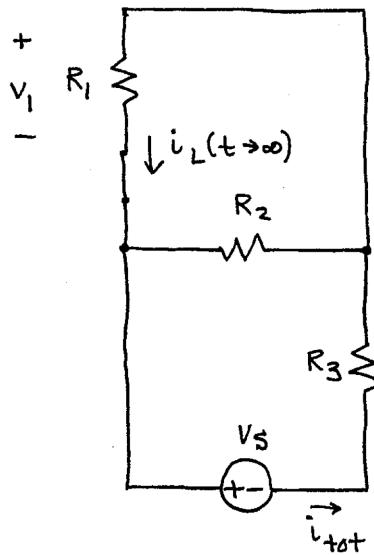$t \rightarrow \infty$: L acts like wire
 Switch is closed



We can calculate i_{tot} as

$$i_{tot} = -\frac{V_s}{R_1 \parallel R_2 + R_3}$$

Then we can use a current divider to find $i_L(t \rightarrow \infty)$:

$$i_L(t \rightarrow \infty) = i_{tot} \cdot \frac{R_2}{R_1 + R_2}$$

$$i_L(t \rightarrow \infty) = \frac{-V_s}{R_1 \parallel R_2 + R_3} \cdot \frac{R_2}{R_1 + R_2}$$

Another way to calculate i_{tot} is to write $R_1 \parallel R_2$ in a different way:

$$R_1 \parallel R_2 = \frac{R_1}{1 + \frac{R_1}{R_2}}$$

Then we use a voltage divider formula:

$$V_1 = -V_S \frac{\frac{R_1}{1 + R_1/R_2}}{\frac{R_1}{1 + R_1/R_2} + R_3}$$

$$V_1 = -V_S \frac{R_1}{R_1 + R_3(1 + R_1/R_2)}$$

We divide V_1 by R_1 to find $i_L(t \rightarrow \infty)$:

$$i_L(t \rightarrow \infty) = -\frac{V_S}{R_1 + R_3(1 + R_1/R_2)}$$

This answer is equivalent to our previous answer

R_{Th} : We turn off the V_S source and look in from the terminals where L is connected. Switch is closed.

