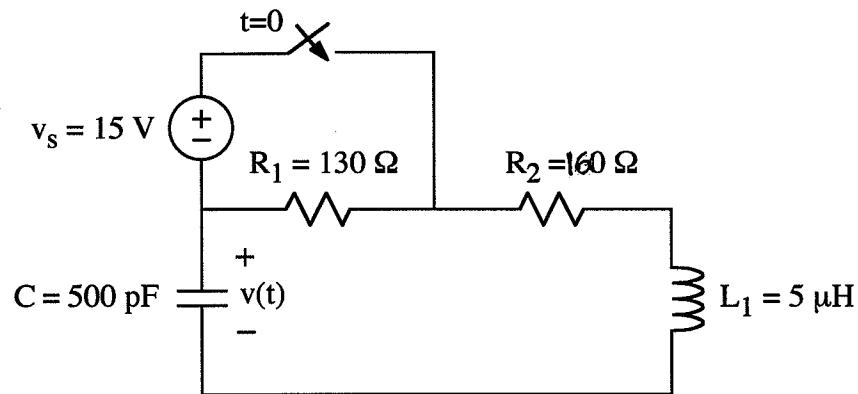


EX:



After being open for a long time, the switch closes at  $t = 0$ .

Find  $v(t)$  for  $t > 0$ .

Sol'n: First, we find the characteristic roots for the circuit. After  $t=0$  we have a series RLC circuit with a voltage source.  $R_1$  is bypassed so we use  $R=R_2$ .

$$\text{For series RLC, } \alpha = \frac{R}{2L}, \quad \omega_0^2 = \frac{1}{LC}$$

$$\alpha = \frac{160\Omega}{2 \cdot 5\mu\text{H}}, \quad \omega_0^2 = \frac{1}{5\mu\text{H} \cdot 500\text{pF}}$$

$$\alpha = 16 \text{ M r/s}, \quad \omega_0^2 = 400 \text{ M}^2 (\text{r/s})^2$$

$$\omega_0 = 20 \text{ M r/s}$$

$\omega_0 > \alpha$  so we have underdamped case:

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{(20\text{M})^2 - (16\text{M})^2} \text{ r/s}$$

$$\omega_d = 12 \text{ M r/s}$$

Note:  $\omega_d > \alpha$  can happen but  $\omega_d < \omega_0$  always.

Our sol'n form is


$$v(t) = A_1 e^{-\alpha t} \cos \omega_d t + A_2 e^{-\alpha t} \sin \omega_d t + A_3$$

Second, we find  $A_3 = v(t \rightarrow \infty)$ .

As  $t \rightarrow \infty$ ,  $C = \text{open}$   $L = \text{wire}$  switch closed

model:

( $t \rightarrow \infty$ )

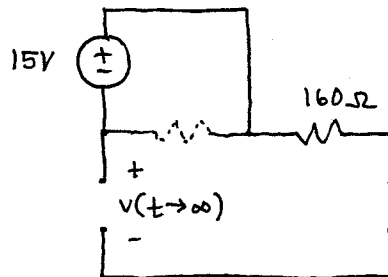


No current in  $R$   
so no  $V$ -drop for  
 $R$ . Thus,  $15V$   
from source is  
across  $C$ .

$$v(t \rightarrow \infty) = -15V$$

$$\therefore A_3 = -15V$$

Third, we find  $i_L(t=0^-)$  and  $v_C(t=0^-)$  as  
a precursor to finding  $v(0^+)$  and  $\left. \frac{dv}{dt} \right|_{t=0^+}$ .

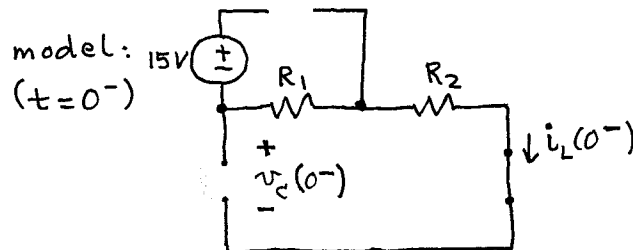At  $t=0^-$ ,  $C = \text{open}$   $L = \text{wire}$  switch open




Source  
not connected  
so  $i_L(0^-) = 0$   
and  $v_C(0^-) = 0$ .

Fourth, we have  $i_L(0^+) = i_L(0^-)$  and  $v_C(0^+) = v_C(0^-)$  since these are energy variables ( $w = \frac{1}{2} Li^2$  and  $w = \frac{1}{2} Cv^2$ ) that cannot change instantly.

At  $t=0^+$ , we model  $L$  as a current source with value  $i_L(0^+)$  and  $C$  as a voltage source with value  $v_C(0^+)$ .

model:  
( $t=0^+$ )

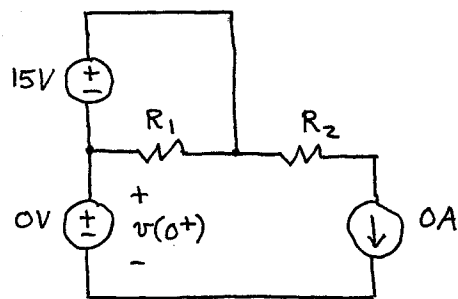

Fifth, we solve the circuit to find  $v(0^+)$ . Here, we have that  $v(0^+) = 0V$  without doing any additional work.

For the form of sol'n we are using, we have

$$v(0^+) = A_1 e^{-\alpha t} \cos(\omega_d t) + A_2 e^{-\alpha t} \sin(\omega_d t) + A_3 \Big|_{t=0^+}$$

$$" = A_1 \cdot e^{-0^+} \cos(0) + A_2 \cdot e^{-0^+} \sin(0) + A_3$$

$$" = A_1 \cdot 1 \cdot 1 + A_2 \cdot 1 \cdot 0 + A_3$$

$$" = A_1 + A_3$$

Equating the known value of  $v(0^+) = 0V$  with the symbolic sol'n, we conclude that:

$$0V = A_1 + A_3 = A_1 - 15V \quad \text{or} \quad A_1 = 15V$$

Sixth, we use the circuit model at  $t=0^+$  to find  $\left. \frac{dv(t)}{dt} \right|_{t=0^+}$ .

The method we use to find any derivative value at  $t=0^+$  is to write an expression for  $v(t)$  in terms of only  $i_L(t)$  and  $v_C(t)$  plus component values.

Here, we have the simple result that

$$v(t) = v_C(t)$$

Now we differentiate this entire eq'n:

$$\frac{dv(t)}{dt} = \frac{dv_C(t)}{dt}$$

From  $i_C(t) = C \frac{dv_C(t)}{dt}$  we have  $\frac{dv_C(t)}{dt} = \frac{i_C(t)}{C}$ .  
(Although we don't require it here, we also have  $v_L(t) = L \frac{di_L(t)}{dt}$  or  $\frac{di_L(t)}{dt} = \frac{v_L(t)}{L}$ .)

$$\text{Thus} \quad \left. \frac{dv(t)}{dt} \right|_{t=0^+} = \left. \frac{dv_C(t)}{dt} \right|_{t=0^+} = \left. \frac{i_C(t)}{C} \right|_{t=0^+}$$

We use our model for  $t=0^+$  to find  $i_C(t=0^+)$ . (See above.) From the model,  $i_C(0^+) = 0A$  since  $C$  is in series with a  $0A$  source.

$$\therefore \left. \frac{dv(t)}{dt} \right|_{t=0^+} = \left. \frac{i_c(t)}{C} \right|_{t=0^+} = \frac{0A}{C} = 0 \text{ V/s}$$

Equating this known value of  $\left. \frac{dv(t)}{dt} \right|_{t=0^+}$  with  $\left. \frac{d}{dt} \right|_{t=0^+}$  of the symbolic sol'n,

we have

$$0V = \left. \frac{d}{dt} v(t) \right|_{t=0^+} = \left. \frac{d}{dt} \left[ A_1 e^{-\alpha t} \cos(\omega_d t) + A_2 e^{-\alpha t} \sin(\omega_d t) \right] \right|_{t=0^+}$$

$$= \left. \begin{aligned} & A_1 (-\alpha) e^{-\alpha t} \cos(\omega_d t) + A_1 e^{-\alpha t} [-\sin(\omega_d t)] \omega_d \\ & + A_2 (-\alpha) e^{-\alpha t} \sin(\omega_d t) + A_2 e^{-\alpha t} \cos(\omega_d t) \omega_d \end{aligned} \right|_{t=0^+}$$

$$= A_1 (-\alpha) 1 \cdot 1 + A_1 \cdot 1 \cdot \omega_d \cdot 0 + A_2 (-\alpha) 1 \cdot 0 + A_2 \cdot 1 \cdot \omega_d \cdot 1$$

$$0V = A_1 (-\alpha) + A_2 \omega_d$$

$$\text{Thus, } A_2 = \frac{A_1 \alpha}{\omega_d} = \frac{15V \cdot 16 \text{ Mr/s}}{12 \text{ Mr/s}} = 20V$$

$$\begin{aligned} \therefore v(t > 0) &= 15V e^{-16Mt} \cos(12Mt) \\ &+ 20V e^{-16Mt} \sin(12Mt) \\ &- 15V \end{aligned}$$

$$\text{Check: } v(0^+) = 15V - 15V = 0V \quad \checkmark$$

$$\text{When } \left. \frac{dv}{dt} \right|_{t=0^+} = 0 \text{ we should have } A_1 \alpha = A_2 \omega_d \quad \checkmark$$