

TUTORIAL: STATE VARIABLES and MATLAB®

Time-domain analysis of circuits with more than one L and C is difficult because it requires solution of characteristic equations higher than second degree. This supplement illustrates the use of MATLAB® functions, ode23 and ode45, for solving a system of coupled first-order differential equations of the form

$$d\mathbf{x}/dt = f(\mathbf{x},t)$$

where \mathbf{x} is a vector called the *state vector*, and t is the independent variable, which in our case will be time. As indicated in *Mastering MATLAB® 7*, Chapter 25, a differential equation can always be expressed as a system of coupled first-order differential equations. The MATLAB® functions are powerful because they can be used to solve nonlinear as well as linear differential equations.

Consider the third-order circuit in Fig. 1 as an example for illustrating the use of the state vector (state variables) and ode45. Let's use MATLAB® to plot v_2 as a function of time. Using Kirchhoff's laws in the time domain, we could write the third-order differential equation for v_2 and then convert it to three coupled first-order equations following the procedure outlined in the MATLAB® book. It is much easier, however, to obtain the system of coupled first-order equations directly in terms of what are called the *state variables*. For circuits, the state variables are the currents through inductances and the voltages across capacitances. Using Kirchhoff's laws in the time domain, it is easy to write first-order differential equations in terms of these variables because $i = C dv/dt$ for a capacitance, and $v = L di/dt$ for an inductance, both of which involve first derivatives.

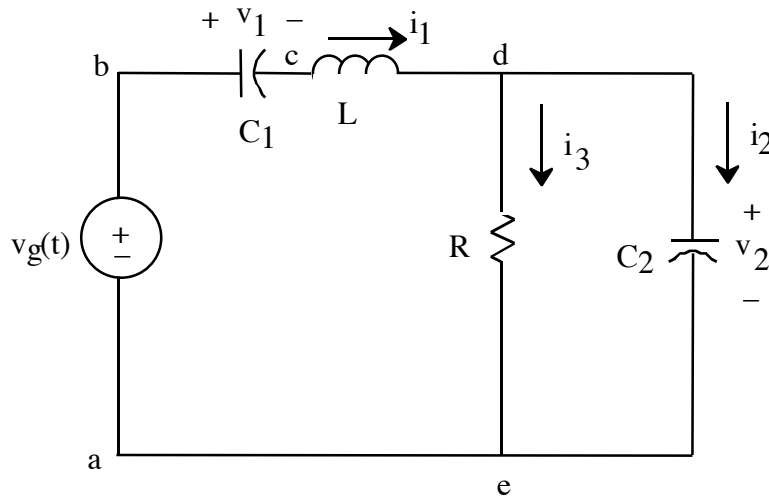


Fig. 1. Third-order circuit. $v_g(t)$ is a step function that switches from $-v_0$ to v_0 at $t = 0$.

The state variables for the circuit in Fig. 1 are v_1 , v_2 , and i_1 . The first equation is easily obtained from the relationship between the voltage and current for C_1 :

$$(1) \quad dv_1/dt = i_1/C$$

The second equation is obtained by writing Kirchhoff's voltage equation around the closed path $abcdea$:

$$-v_g + v_1 + L di_1/dt + v_2 = 0$$

from which we get

$$(2) \quad di_1/dt = -v_1/L - v_2/L + v_g/L$$

The third equation is obtained by using Kirchhoff's current law,

$$i_1 = i_2 + i_3$$

and $i_3 = v_2/R$, $i_2 = C_2 dv_2/dt$ to get

$$(3) \quad dv_2/dt = i_1/C_2 - v_2/RC_2$$

Now defining the state vector (note that x is a column vector) as

$$(4) \quad x = [v_1 \ i_1 \ v_2]^T$$

we get the three coupled first-order differential equations from (1), (2), (3), and (4):

$$(5) \quad dx_1/dt = x_2/C_1$$

$$(6) \quad dx_2/dt = -x_1/L - x_3/L + v_g/L$$

$$(7) \quad dx_3/dt = x_2/C_2 - x_3/RC_2$$

Before writing the Matlab® program, we need the initial conditions on the vector x . The initial conditions for x are much easier to obtain than for the third-order differential equation for v_2 . Because the current cannot change instantaneously through an inductance, and because the voltage across a capacitance cannot change instantaneously,

$$v_1(0+) = v_1(0-) = -v_0$$

$$i_1(0+) = i_1(0-) = 0$$

$$v_2(0+) = v_2(0-) = 0$$

The initial value of x is thus

$$(8) \quad x_0 = [-v_0 \ 0 \ 0]'$$

The ode45 function requires a function that calculates \dot{x} (which stands for dx/dt) as a function of t and x (see MATLAB® book). Here is a function that calculates \dot{x} as described by (5)-(7):

```
function xdot = ckt(t,x)
vg=1;
C1=100e-9;
C2=100e-9;
R=30;
L=184e-6;
xdot(1) = x(2)/C1;
xdot(2) = -(x(1) + x(3))/L + vg/L;
xdot(3) = x(2)/C2 - x(3)/(R*C2);
xdot = [xdot(1); xdot(2); xdot(3)];
```

To solve for x and plot v_2 , we can now type the following in the command window:

```
t0=0; tf=60e-6;  
tspan=[t0,tf];  
x0=[-1 0 0]';  
[t,x]=ode45('ckt',tspan,x0);  
plot(t,x(:,3))
```

We could also plot all three components of x by using `plot(t,x)`, as shown in Fig. 2.

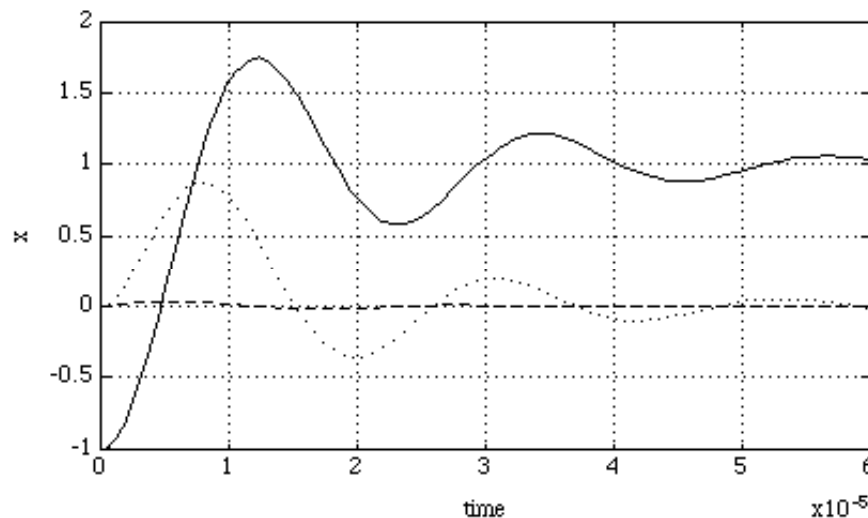


Fig. 2. Graph of the state vector x versus time for the circuit of Fig. 1.

If t_f is chosen to be too large, the matrix size limitation in the student edition of MATLAB® will be exceeded. Also, sometimes choosing t_f to be too large will cause a message "singularity expected," and the function will not be executed.

EX: Use `ode45` to solve for x for the circuit in Fig. 3 when $R_1 = 20 \Omega$, $R_2 = 5 \Omega$, $C_1 = 100 \text{ nF}$, $C_2 = 200 \text{ nF}$, $L = 300 \mu\text{H}$, $v_o = 1 \text{ V}$. Then plot i_1 versus t and i_3 versus t .

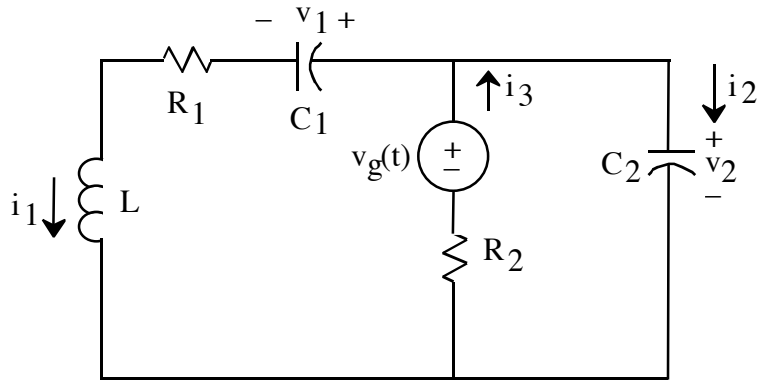


Fig. 3. The voltage $v_g(t)$ changes instantly from $-v_o$ to v_o at $t = 0$.

GIVEN:

$$x = [i_1 \ v_1 \ v_2]'$$

$$dx_1/dt = (x_3 - x_2)/L - x_1 R_1/L$$

$$dx_2/dt = x_1/C_1$$

$$dx_3/dt = -x_1/C_2 + (v_g - x_3)/(R_2 C_2)$$

$$x_o = [0 \ -v_o \ -v_o]'$$

ANS:

