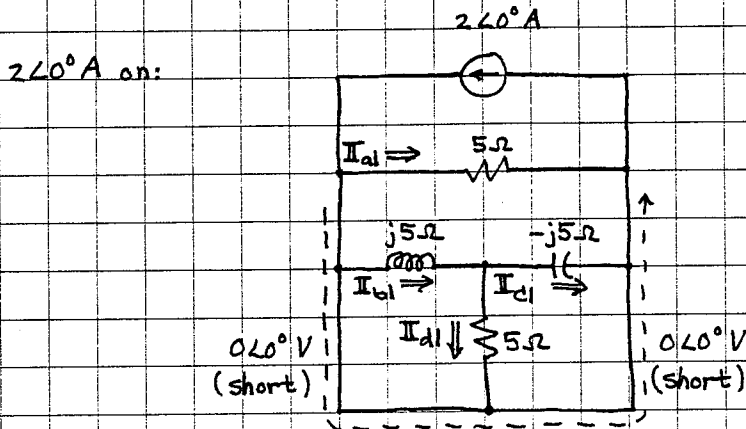


ex: (See circuit diagram for mesh-current sol'n)


Use superposition to find I_a , I_b , I_c , and I_d .

sol'n: Turn on one independent source at a time.
Sum currents or voltages from each such circuit.



Observe that all the current will flow thru the path indicated by the dashed line.
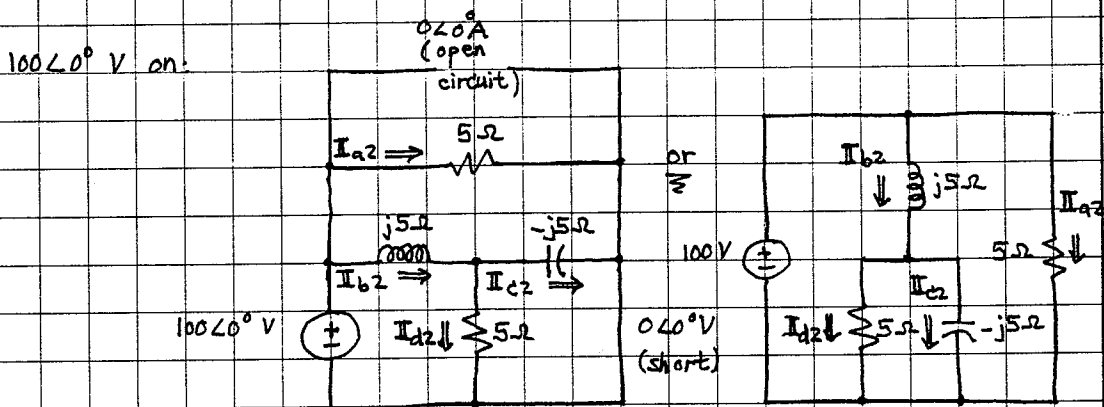
$$\therefore I_{a1} = 0A \quad I_{b1} = 0A \quad I_{c1} = 0A \quad I_{d1} = 0A$$



$$I_{a2} = \frac{100V}{5\Omega} = 20A \quad (\text{since } 5\Omega \text{ across } 100V \text{ source})$$

$$I_{b2} = \frac{100V}{j5\Omega + 5\Omega \parallel (-j5)\Omega} \quad (\text{since 3 components across } 100V)$$

$$= \frac{20}{j + 1 - j} A = \frac{20}{1} A = 20A$$

$$I_{b2} = \frac{40}{j2 + 1 - j} \text{ A} = \frac{40}{1 + j} = \frac{40(1-j)}{(1+j)(1-j)} = \frac{40(1-j)}{2} = 20 - j20 \text{ A}$$


$$I_{c2} = I_{b2} \frac{5\Omega}{5 - j5\Omega} \quad (\text{I-divider})$$

$$= \frac{20(1-j)}{(1-j)} \frac{5}{5} = 20 \text{ A}$$

$$I_{d2} = I_{b2} \frac{-j5\Omega}{5 - j5\Omega} \quad (\text{I-divider})$$

$$= \frac{20(1-j)}{(1-j)} \frac{-j5}{5} = -j20 \text{ A}$$

50∠0° V on:

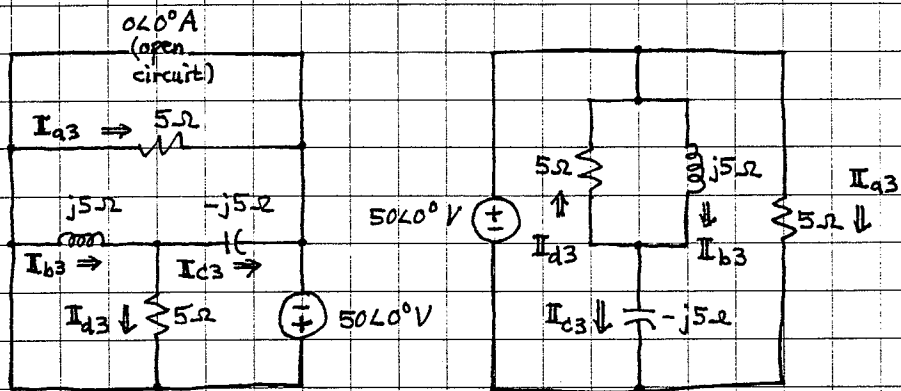

$$I_{a3} = \frac{50\angle 0^\circ \text{ V}}{5\Omega} = 10 \text{ A}$$

$$I_{c3} = \frac{50\angle 0^\circ \text{ V}}{5\Omega \parallel j5\Omega + -j5\Omega} = \frac{10}{1 \parallel j - j} \text{ A} = \frac{10}{\frac{j}{1+j} - j} = \frac{10(1+j)}{j - j(1+j)} \text{ A}$$

$$= 10 + j10 \text{ A}$$

$$I_{b3} = I_{c3} \frac{5\Omega}{5\Omega + j5\Omega} = \frac{10(1+j)}{(1+j)} \frac{5}{5} = 10 \text{ A}$$

$$I_{d3} = -I_{c3} \frac{j5\Omega}{5\Omega + j5\Omega} = -10 \frac{(1+j) - 5j}{(1+j) - 5} = -j10A$$

Now sum the currents from each circuit to get total I 's:

$$I_a = I_{a1} + I_{a2} + I_{a3} = 0A + 20A + 10A = 30A$$

$$I_b = I_{b1} + I_{b2} + I_{b3} = 0A + 20 - j20A + 10A = 30 - j20A$$

$$I_c = I_{c1} + I_{c2} + I_{c3} = 0A + 20A + 10 + j10A = 30 + j10A$$

$$I_d = I_{d1} + I_{d2} + I_{d3} = 0A + -j20A + -j10A = -j30A$$

Our answers agree with the mesh-current method.

Note how the superposition method reveals that the $2\angle 0^\circ A$ source adds nothing to currents I_a , I_b , I_c , and I_d .