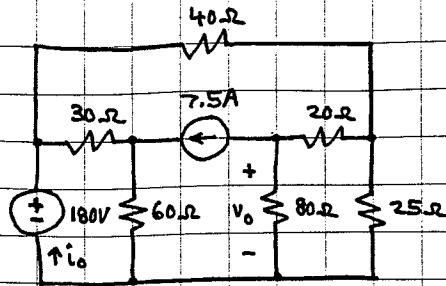


ex:




Use superposition to solve for  $i_o$  and  $v_o$  in the circuit.

Sol'n: We turn on one v- or i- source at a time, find  $i$ 's and  $v$ 's, and then sum results from each circuit to find total  $i$ 's and  $v$ 's.

Circuit 1: 180V source on, 7.5A source set to 0A (open circuit).

Use '1' subscripts.

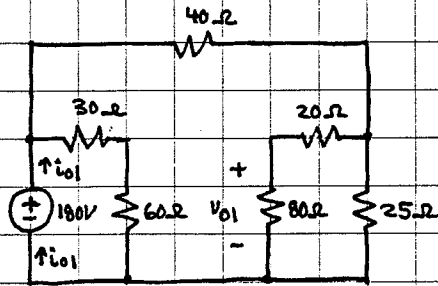

$$i_{o1} = \frac{180V}{30+60\Omega} + \frac{180V}{40 + \frac{(80\parallel 25)\Omega}{+20}} = 5A$$

$$v_{o1} = 180V \frac{(20+80)\parallel 25\Omega \cdot 80\Omega}{40 + \frac{(80\parallel 25)\Omega}{+20} + 20 + 80\Omega} = 48V$$


v-divider, can ignore 30Ω, 60Ω

or use  $v_{o1} = 80\Omega \cdot 3A \cdot \frac{25\Omega}{20+80+25\Omega}$  i-divider


Circuit 2: 180V source off, 7.5A source on

(= 0V = wire)

Use '2' subscripts

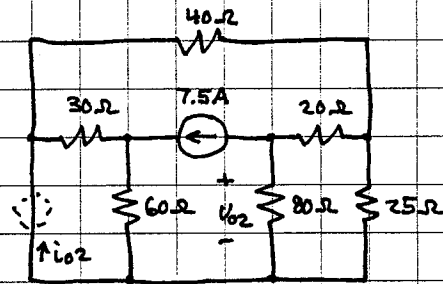

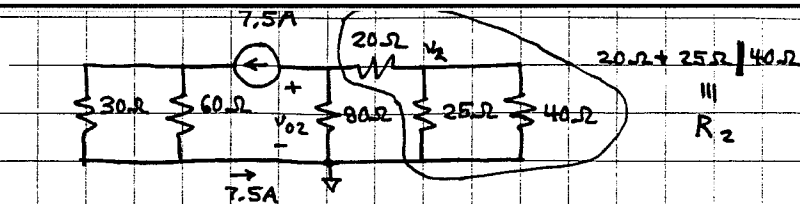Note that the 40Ω R is actually in parallel with the 25Ω R on the right. We can find  $v_{o2}$  (but not  $i_{o2}$ ) with the following circuit:



Now we have an  $i$ -divider on the right.

$$i_{80\Omega} = -7.5A \cdot \frac{R_2}{R_2 + 80\Omega} \quad v_{02} = i_{80\Omega} \cdot 80\Omega$$

$$v_{02} = -7.5A \cdot \frac{R_2 \cdot 80\Omega}{R_2 + 80\Omega} = -7.5A \cdot R_2 \parallel 80\Omega \quad (\text{of course!})$$

$$R_2 = 30 + 5\Omega \cdot 5 \parallel 8 = 20 + 5 \cdot \frac{40}{13} = \frac{460}{13}$$

$$R_2 \parallel 80\Omega = \frac{460 \cdot 80}{13 \cdot \left(\frac{460}{13} + 80\right)} = \frac{460 \cdot 8}{46 + 13 \cdot 8} = \frac{3680}{150} = \frac{368}{15}$$

$$v_{02} = -7.5 \cdot \frac{368}{15} = -\frac{368}{2} = -184V$$

Now <sup>for</sup>  $i_{02}$ . We can find  $v_2$  shown on above circuit diagram. Then this will give us the current in the  $40\Omega$  R. This will also give us the current through the  $80\Omega$  and  $25\Omega$  R's.

We also observe that the  $30\Omega$  and  $60\Omega$  R's form a current divider.

$$i_{30\Omega} = 7.5A \cdot \frac{60\Omega}{30\Omega + 60\Omega} = 5A$$

$$i_{60\Omega} = 7.5A \cdot \frac{30\Omega}{30\Omega + 60\Omega} = 2.5A$$


We find  $v_2$  from  $V$ -divider:

$$v_2 = v_{02} \cdot \frac{25 \parallel 40\Omega}{20\Omega + 25 \parallel 40\Omega} = -184V \cdot \left( \frac{\frac{200}{13}}{\frac{460}{13}} = \frac{200}{460} = \frac{10}{23} \right)$$

$$v_2 = -80V$$

$$i_{40\Omega} = \frac{80V}{40\Omega} = 2A$$

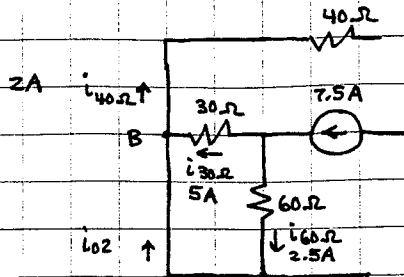Now back to the original circuit #2 for a detailed look at  $i_{o2}$ :



$$A \rightarrow 7.5A - i_{40\Omega} = 5.5A$$

↑ This current +  $i_{40\Omega}$  must equal 7.5A from source.

$$i_{o2} = i_{60\Omega} - 5.5A = 2.5A - 5.5A = -3A$$

from sum of currents out of node A = 0A.

$$\text{check } i_{o2} = i_{40\Omega} - i_{30\Omega} = 2A - 5A = -3A \checkmark$$

from sum of currents out of node B = 0A.

Now add results from circuits 1 and 2:

$$v_o = v_{o1} + v_{o2} = 48V + -184V = -136V$$

$$i_o = i_{o1} + i_{o2} = 5A + -3A = 2A.$$