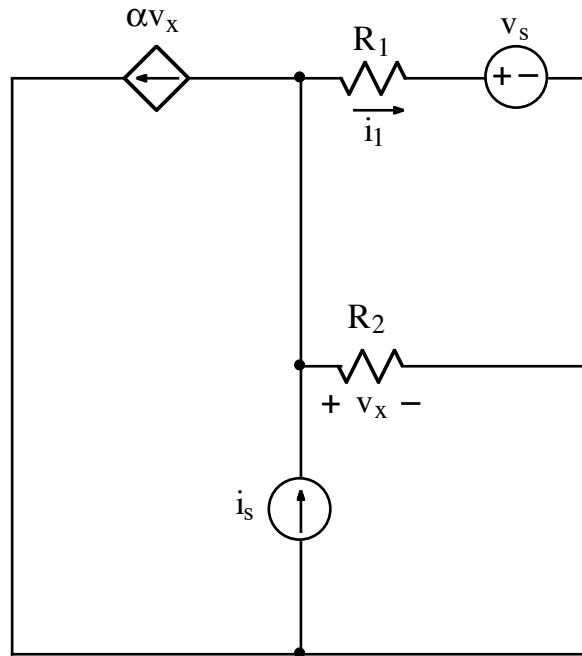



Ex:



Using superposition, derive an expression for  $i_1$  that contains no circuit quantities other than  $i_s$ ,  $v_s$ ,  $R_1$ ,  $R_2$ , and  $\alpha$ , where  $\alpha > 0$ .

Sol'n: We turn on one source at a time.  
(Never turn off dependent source.)

case I:  $v_s$  on,  $i_s$  off

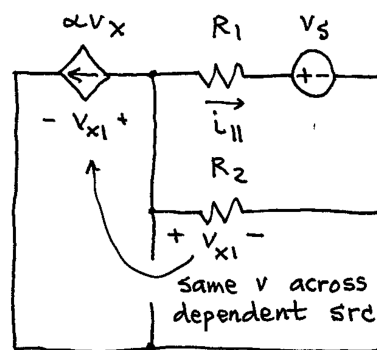

The dependent source is equivalent to  $R_{eq} = \frac{v}{i} = \frac{V_{x1}}{\alpha V_{x1}} = \frac{1}{\alpha}$ .

$$\text{or } i_{12} = i_s \frac{\frac{R_2/\alpha}{R_2 + 1/\alpha}}{\frac{R_2/\alpha}{R_2 + 1/\alpha} + R_1}$$

$$\text{or } i_{12} = i_s \frac{R_2/\alpha}{R_2/\alpha + R_1(R_2 + 1/\alpha)}$$

$$\text{or } i_{12} = i_s \frac{R_2}{R_2 + R_1(\alpha R_2 + 1)}$$

We sum  $i_{11}$  and  $i_{12}$  to get  $i_1$ :

$$i_1 = i_{11} + i_{12}$$

$$\text{or } i_1 = -\frac{V_s}{R_1 + R_2 \parallel \frac{1}{\alpha}} + i_s \frac{R_2}{R_2 + R_1(\alpha R_2 + 1)}$$

Note: When a current source is off it becomes an open circuit.  
When a voltage source is off it becomes a wire.