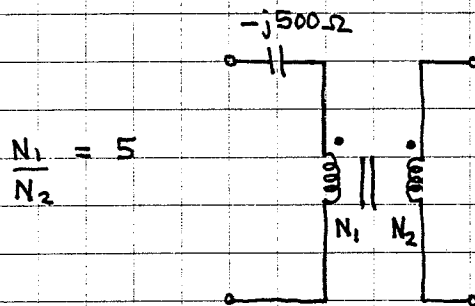


Use ideal transformer and inductance or capacitance to achieve max power absorption.

ans:




sol'n:

For an ideal transformer, the secondary impedance reflected into the primary is  $z_{IN} = \left(\frac{N_1}{N_2}\right)^2 z_L$ .

Here,  $z_L = 20 + j20 \Omega$ .

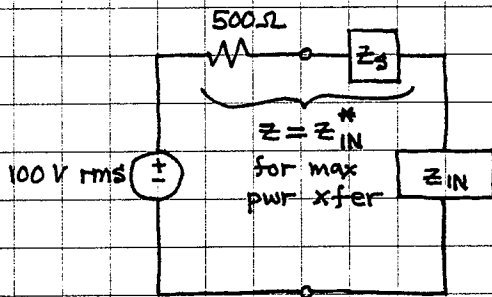To maximize power absorption, we want the series impedance in the primary to equal the complex conjugate of the reflected impedance:



See p. 512 of Text for max pwr xfer discussion.

$$z_{IN}^* = \left(\frac{N_1}{N_2}\right)^2 (20 + j20)^* \Omega$$

$$= \left(\frac{N_1}{N_2}\right)^2 20 - j \left(\frac{N_1}{N_2}\right)^2 20 \Omega$$

Since  $z_s$  was specified to be an inductance or capacitance we must have  $500 \Omega = \left(\frac{N_1}{N_2}\right)^2 \cdot 20 \Omega = \text{Re}[z_{IN}^*]$ .  $\therefore \frac{N_1}{N_2} = 5$

To match  $j\text{Im}[z_{IN}^*] = -j 5^2 \cdot 20 \Omega = -j500 \Omega$  use  $z_s = -j500 \Omega$  capacitor.