

Given an ideal transformer in the above circuit, calculate  $i(t)$ .

$$\text{ans: } i(t) = 6 \cos\left(\frac{20 \cdot 10^4 t}{9} + 143^\circ\right) A$$

sol'n: As shown in the Text, we have the following relationships for currents and voltages:


$$\frac{V_1}{N_1} = \frac{V_2}{N_2} \quad \frac{I_1}{I_2} = \frac{N_2}{N_1}$$

$$\text{or } V_2 = \frac{N_2}{N_1} V_1 \quad \text{or } I_2 = \frac{N_1}{N_2} I_1$$

Note: We have positive signs in these eqn's if we define  $V_1$ ,  $V_2$ ,  $I_1$ , and  $I_2$  as shown in the diagram above. In particular  $I_1$  is in the direction of the passive sign convention, but  $I_2$  is opposite the passive sign convention. Also,  $V_1$  and  $V_2$  are measured with the plus sign on the dotted side of transformer windings.

For the ideal transformer, we do not know what the impedances inside the transformer are. Thus, we must use only the ideal transformer relationships to write eqn's from which we solve for  $I$  (or  $i(t)$ ).

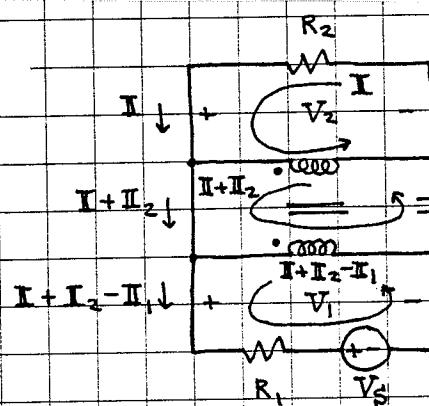We write mesh current eqn's for the three loops and then use the ideal transformer relationships.



- We have current  $I$  on the outside of the top loop.

- We have current  $I + I_2$  on the outside left side of the middle loop.

- We have current  $I + I_2 - I_1$  on the outside of the bottom loop

Mesh loop eqns from top to bottom:

$$-I \cdot R_2 - V_2 = 0 \quad \text{or} \quad I R_2 + V_2 = 0 \quad (1)$$

$$V_2 - V_1 - \frac{1}{jwC} (I + I_2) = 0 \quad (2)$$

$$V_1 - R_1 (I + I_2 - I_1) - V_s = 0 \quad (3)$$

Use ideal transformer relationships to eliminate

$$I_2 \text{ and } V_2: \quad I_2 = \frac{N_1}{N_2} I_1 = \frac{I_1}{10}$$

$$\text{Also, } \frac{1}{jwC} = -j9 \quad V_2 = \frac{N_2}{N_1} V_1 = 10V_1$$

$$I R_2 + 10V_1 = 0 \quad \text{or} \quad V_1 = -\frac{R_2}{10} I = -\frac{I}{10} \quad (1)$$

$$10V_1 - V_1 + j9(I + \frac{I_1}{10}) = 0 \quad (2)$$

$$V_1 - R_1(I + \frac{I_1}{10} - I_1) - V_s = 0 \quad (3)$$

Now use (1) to eliminate  $V_1$  in (2) and (3):

$$\left( -10 + 1 \right) I + j9I + j9 \frac{I_1}{10} = 0 \quad (2)$$

$$-I - R_1 \left( I - \frac{9I_1}{10} \right) - V_s = 0 \quad (3)$$

Now use (2) to express  $I_1$  in terms of  $I$ :

$$I_1 = j \frac{10}{9} (-9 + j9) I = j 10 (-1 + j) I$$

Substitute for  $\mathbb{I}_1$  in (3):

$$-\mathbb{I} - \frac{1}{2} \left( \mathbb{I} - \frac{9}{10} j 10(-1+j) \mathbb{I} \right) - V_s = 0$$

$$\left[ -\frac{3}{2} + \frac{9}{2} j (-1+j) \right] \mathbb{I} - V_s = 0$$

$$\left( -\frac{3}{2} - \frac{9}{2} - j \frac{9}{2} \right) \mathbb{I} - V_s = 0$$

$$\left( -6 - j \frac{9}{2} \right) \mathbb{I} - V_s = 0$$

$$\mathbb{I} = \frac{V_s}{-6 - j \frac{9}{2}} = \frac{-45}{6 + j \frac{9}{2}} = \frac{-15}{2 + j \frac{3}{2}}$$

$$" = \frac{-30}{4 + j 3} = \frac{-30 (4 - j 3)}{25} = \frac{6 (4 - j 3)}{5}$$

$$" = -\frac{6}{5} \cdot 5 \angle -37^\circ$$

$$" = \frac{6}{5} \angle 180^\circ - 37^\circ$$

$$\mathbb{I} = 6 \angle 143^\circ A$$

$$\therefore i(t) = 6 \cos(\omega t + 143^\circ) A \quad \omega = \frac{20 \cdot 10^4}{9} \text{ rad/s}$$