
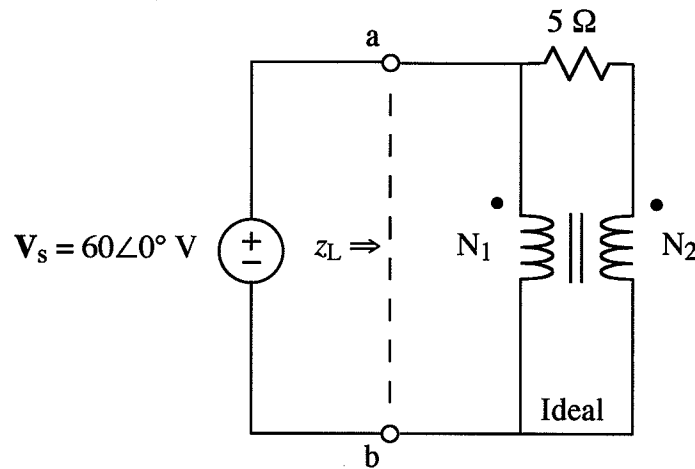


EX:

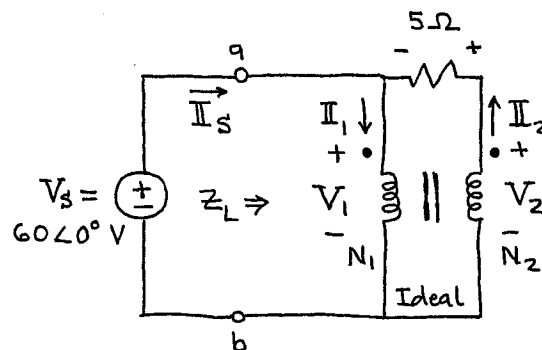

Given $N_1/N_2 = 9$, calculate the impedance, z_L , seen by the voltage source in the above transformer circuit.

Sol'n: We begin by labeling the transformer V 's and I 's.



Note: The + signs for V_1 and V_2 are at the dots. I_1 flows into the dot, and I_2 flows out of the dot.

Now we use Ohm's law to find z_L as $z_L = V_s / I_s$.

From a current summation at the node to the left of the 5Ω resistor, we have

$$-I_3 + I_1 - I_2 = 0A. \quad (1)$$

Since one node is always redundant for current summations, this is the only current summation equation for the circuit.

We do, however, have that I_2 flows thru the 5Ω resistor, giving a voltage drop with the polarity indicated on the above circuit diagram.

This V -drop is part of the voltage loop on the right side which yields the following eq'n:

$$V_1 + I_2 \cdot 5\Omega - V_2 = 0V \quad (2)$$

We also have the voltage loop on the left:

$$V_3 - V_1 = 0V \quad \text{or} \quad V_3 = V_1 \quad (3)$$

Now we use the ideal transformer eq'ns:

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} \quad \frac{I_1}{I_2} = \frac{N_2}{N_1}$$

Eg'n (2) becomes (also using $V_1 = V_S$)

$$I_2 \cdot 5\Omega = V_2 - V_1$$

$$" = V_1 \frac{N_2}{N_1} - V_1$$

$$I_2 \cdot 5\Omega = V_1 \left(\frac{N_2}{N_1} - 1 \right)$$

$$I_2 = \frac{V_1 \left(\frac{N_2}{N_1} - 1 \right)}{5\Omega} = \frac{V_S \left(\frac{N_2}{N_1} - 1 \right)}{5\Omega}$$

$$I_2 = \frac{60\angle 0^\circ V \cdot \left(\frac{1}{9} - 1 \right)}{5\Omega}$$

$$= 12\angle 0^\circ A \cdot \left(-\frac{8}{9} \right)$$

$$I_2 = -\frac{32}{3}\angle 0^\circ A = -10.67\angle 0^\circ A$$

Eg'n (1) becomes

$$I_S = I_1 - I_2$$

$$= I_2 \frac{N_2}{N_1} - I_2$$

$$= I_2 \left(\frac{N_2}{N_1} - 1 \right)$$

$$= I_2 \left(\frac{1}{9} - 1 \right)$$

$$I_S = I_2 \left(-\frac{8}{9} \right)$$

Now we compute $z_L = \frac{V_s}{I_s}$.

$$z_L = \frac{V_s}{I_s} = \frac{V_s}{I_2 \left(\frac{-8}{9} \right)} = \frac{V_s}{\frac{V_s \left(\frac{N_2 - 1}{N_1} \right) \left(\frac{N_2 - 1}{N_1} \right)}{5 \Omega} \uparrow \frac{-8}{9}}$$

$$z_L = \frac{5 \Omega}{\left(\frac{N_2 - 1}{N_1} \right)^2} = \frac{5 \Omega}{\left(\frac{-8}{9} \right)^2}$$

$$z_L = 5 \Omega \cdot \frac{9^2}{8^2} = 5 \Omega \cdot \frac{81}{64}$$

$$z_L = 6.3 \Omega$$