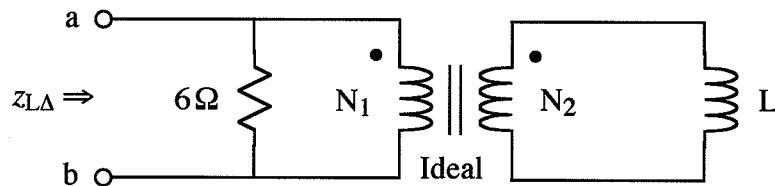


**Ex:**


Given  $N_1/N_2 = 2$  and  $\omega = 100 \text{ rad/s}$ , find a numerical value for  $L$  to make  $z_{L\Delta} = 3 + j3 \Omega$ .

**Sol'n:** We use the idea of reflected impedance.

We replace the transformer and the secondary's impedance,  $z_L$ , with  $z_r$ :

$$z_r = \left(\frac{N_1}{N_2}\right)^2 j\omega L = 2^2 \cdot j100 \text{ r/s } L$$

circuit model:

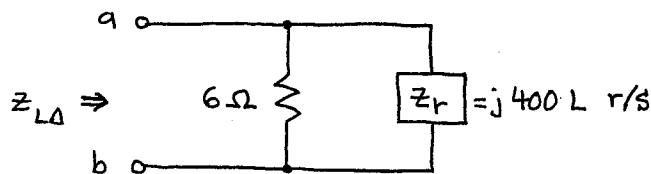

We are given  $z_{L\Delta} = 3 + j3 \Omega = 3(1+j) \Omega$ .

Since we have parallel impedances, it simplifies matters if we use conductance:

$$\frac{1}{z_{L\Delta}} = \frac{1}{3(1+j)\Omega} = \frac{1}{6\Omega} + \frac{1}{j400L \text{ r/s}}$$

"

$$\frac{1}{z_{L\Delta}} = \underbrace{\frac{1-j}{3(1+j)(1-j)\Omega}}_2 = \frac{1}{6\Omega} + \frac{-j}{400L \text{ r/s}}$$

$$\frac{1}{z_{L\Delta}} = \frac{1}{6\Omega} - \frac{j}{6\Omega} = \frac{1}{6\Omega} - \frac{j}{400L \text{ r/s}}$$

We have  $400L \text{ r/s} = 6\Omega$

$$\text{or } L = \frac{6\Omega}{400 \text{ r/s}}$$

$$\text{or } L = 15 \text{ mH}$$