

Digital Electronics

Neil E Cotter

ECE DEPT. UNIVERSITY OF UTAH



Digital Electronics

Binary Numbers:

Voltages

Binary Add

Binary Multiply

Logic Gates:

NOT


OR

AND

NAND

DeMorgan

Digital Electronics

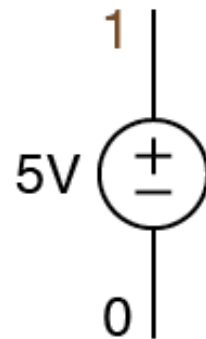

Binary voltages:

$$5V = 1$$

$$0V = 0$$

Digital Electronics

Binary Add:

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 10$$

Digital Electronics

Binary Multiply:

$$0 * 0 = 0$$


$$0 * 1 = 0$$

$$1 * 0 = 0$$

$$1 * 1 = 1$$

Digital Electronics

NOT

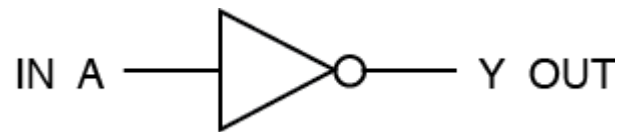

IN	OUT
0	1
1	0

Digital Electronics


OR



IN A	IN B	OUT
0	0	0
0	1	1
1	0	1
1	1	1

Digital Electronics


AND

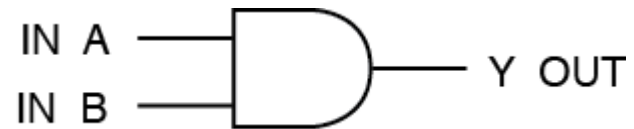

IN A	IN B	OUT
0	0	0
0	1	0
1	0	0
1	1	1

Digital Electronics


NAND

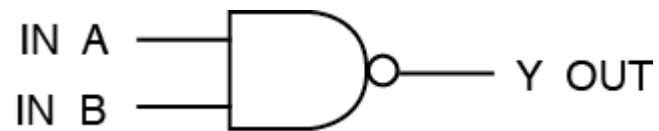

IN A	IN B	OUT
0	0	1
0	1	1
1	0	1
1	1	0

Digital Electronics


Flip-Flop

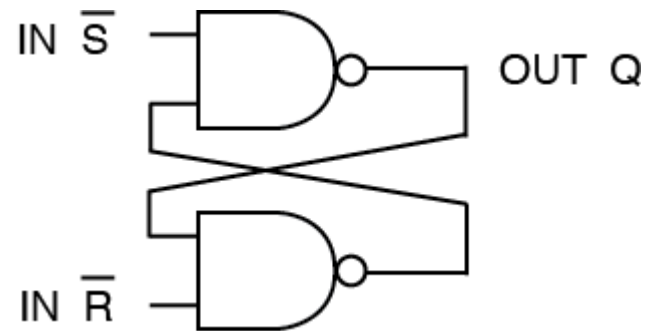

R	S	OUT
0	1	1
1	0	0
0	0	Last Out

Digital Electronics

DeMorgan's Theorem

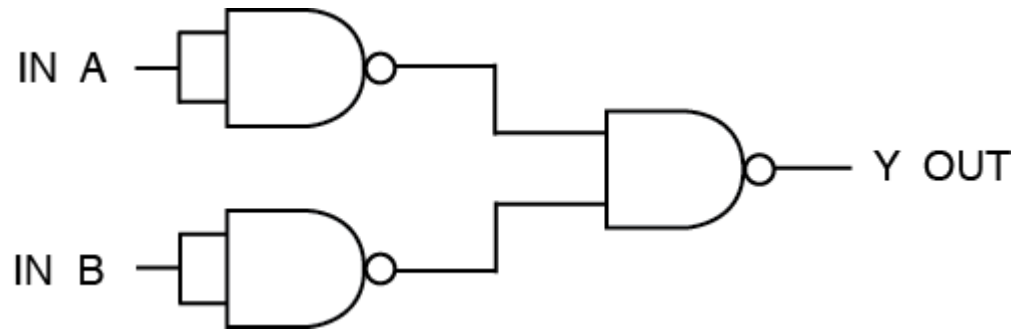

IN A	IN B	OUT
0	0	1
0	1	1
1	0	1
1	1	0