

YOUR NAME(S): _____

PROB: The bandwidth, β , for an *RLC* filter is the difference of cutoff frequencies, ω_{C1} and ω_{C2} :

$$\text{bandwidth} \equiv \beta \equiv \omega_{C2} - \omega_{C1}$$

where the cutoff frequencies satisfy the following equation (obtained by setting the filter gain equal to $1/\sqrt{2}$):

$$\frac{1}{R} \left(\omega L - \frac{1}{\omega C} \right) = \pm 1.$$

Think of ω as x , and think of β as the difference between roots of the above equation, which turns out to be a quadratic equation after multiplying both sides by ω . However, the ± 1 actually means we have two quadratic equations. So we have four roots! We use the two positive roots. ω_{C2} is the larger of the positive roots, and ω_{C1} is the smaller of the positive roots. The bandwidth is $\beta = \omega_{C2} - \omega_{C1}$. Remember to convert the bandwidth in Hz to bandwidth in rad/s when finding the value of R . Curiously, the value of C will be absent from your final equation for R .

The following information is given:

$$B = 1600 \text{ (bandwidth in Hz)}$$

$$\beta = 2\pi B \text{ (to convert frequency in Hz to rad/s)}$$

$$L = 0.1 \text{ H}$$

Find the value of R for the given bandwidth.

$$R = \underline{\hspace{2cm}}$$