

CIRCUIT: The circuit shown below in Fig. 1 produces a rectangular wave with frequency controlled by potentiometer, R_a , R_b . The duty cycle varies with v_{ctrl} . For an op-amp such as the LM324 with asymmetric rail voltages, the duty cycle will be greater than 50% when the control voltage is at reference. A control voltage halfway between the rail voltages, however, produces a 50% duty cycle waveform.

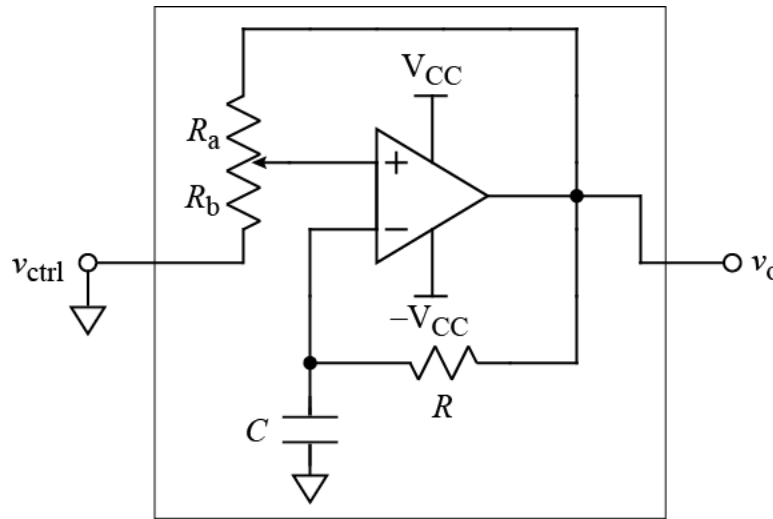


Fig. 1. Oscillator.

Fig. 2 shows the waveforms for the oscillator.

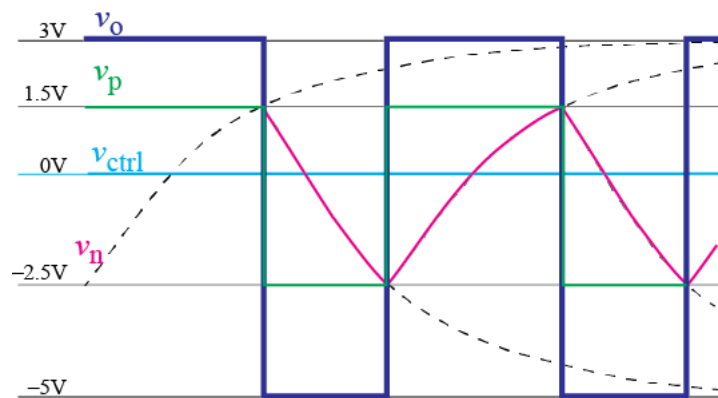


Fig. 2. Oscillator waveforms for LM324 op-amp [1] with $\pm 5V$ supplies.

When the output goes high, the capacitor starts charging toward the positive rail voltage. The positive rail voltage, along with potentiometer, R_a , R_b , and the control voltage, v_{ctrl} , create a voltage divider that determines how high the output voltage, v_o , rises before the op-amp, acting as a comparator, switches to negative rail voltage

output. The same voltage divider is now fed by a negative voltage that determines how low the output voltage, v_o , drops before the op-amp, acting as a comparator, switches to positive rail voltage output. The cycle then repeats.

Analysis of circuit:

To determine the timing of the output waveform, we solve RC charging problems for the rising capacitor voltage. The solution for falling capacitor voltage is obtained by switching the v_{+rail} and v_{-rail} and inverting the value of v_{ctrl} .

The initial voltage for the RC charging problems is the trip point, v_p in Fig. 2, determined by the voltage divider fed by $v_o = v_{-rail}$ and v_{ctrl} .

$$v_C(0^-) = v_p(0^-) = \frac{v_{-rail}R_b + v_{ctrl}R_a}{R_a + R_b}$$

The final destination voltage is the positive rail voltage for v_o , although switching occurs before this voltage is reached.

$$v_C(t \rightarrow \infty) = v_{+rail}$$

The time constant, RC , primarily determines the oscillation frequency, whereas v_{ctrl} primarily controls the duty cycle.

$$\tau = RC$$

It is recommended that the duty cycle be set first with v_{ctrl} . Then R may be adjusted to set the oscillation frequency.

The equation for the charging and discharging curves:

$$v_C(t) = \left[v_C(0^-) - v_C(t \rightarrow \infty) \right] e^{-t/\tau} + v_C(t \rightarrow \infty).$$

Solving for the time of a half-cycle, we set the trip point equal to the capacitor voltage:

$$v_C(t) = v_p = \frac{v_{+rail}R_b + v_{ctrl}R_a}{R_a + R_b} = \left[v_C(0^-) - v_C(t \rightarrow \infty) \right] e^{-t/\tau} + v_C(t \rightarrow \infty)$$

or

$$v_C(t) = \frac{v_{+rail}R_b + v_{ctrl}R_a}{R_a + R_b} = \left[\frac{v_{-rail}R_b + v_{ctrl}R_a}{R_a + R_b} - v_{+rail} \right] e^{-t/\tau} + v_{+rail}$$

or

$$\ln \left(\frac{\frac{v_{+rail}R_b + v_{ctrl}R_a}{R_a + R_b} - v_{+rail}}{\frac{v_{-rail}R_b + v_{ctrl}R_a}{R_a + R_b} - v_{+rail}} \right) = -t / \tau$$

or

$$t = -\tau \ln \left(\frac{\frac{v_{+rail}R_b + v_{ctrl}R_a}{R_a + R_b} - v_{+rail}}{\frac{v_{-rail}R_b + v_{ctrl}R_a}{R_a + R_b} - v_{+rail}} \right) = \tau \ln \left(\frac{\frac{v_{-rail}R_b + v_{ctrl}R_a}{R_a + R_b} - v_{+rail}}{\frac{v_{+rail}R_b + v_{ctrl}R_a}{R_a + R_b} - v_{+rail}} \right)$$

or

$$t = \tau \ln \left(\frac{v_{-rail}R_b + v_{ctrl}R_a - v_{+rail}(R_a + R_b)}{v_{+rail}R_b + v_{ctrl}R_a - v_{+rail}(R_a + R_b)} \right)$$

or

$$t = \tau \ln \left(\frac{v_{-rail} \frac{R_b}{R_a} + v_{ctrl} - v_{+rail} \left(1 + \frac{R_b}{R_a}\right)}{v_{ctrl} - v_{+rail}} \right) = \tau \ln \left(\frac{v_{ctrl} - v_{+rail} - v_{+rail} \frac{R_b}{R_a} + v_{-rail} \frac{R_b}{R_a}}{v_{ctrl} - v_{+rail}} \right)$$

or, reversing signs in the numerator and denominator,

$$t = \tau \ln \left(\frac{v_{+rail} - v_{ctrl} + (v_{+rail} - v_{-rail}) \frac{R_b}{R_a}}{v_{+rail} - v_{ctrl}} \right) = \tau \ln \left(1 + \frac{v_{+rail} - v_{-rail}}{v_{+rail} - v_{ctrl}} \cdot \frac{R_b}{R_a} \right).$$

If we set $v_{ctrl} = 0V$, we obtain the following simplified form.

$$t = \tau \ln \left(1 + \frac{v_{+rail} - v_{-rail}}{v_{+rail}} \cdot \frac{R_b}{R_a} \right) = \tau \ln \left(1 + \left[1 - \frac{v_{-rail}}{v_{+rail}} \right] \cdot \frac{R_b}{R_a} \right)$$

For $R_a = R_b$, as in Figs. 2 and 3,

$$t = \tau \ln \left(2 - \frac{v_{-rail}}{v_{+rail}} \right).$$

For the waveforms in Fig. 2, we have the following ratio of rail voltages:

$$\frac{v_{-rail}}{v_{+rail}} = \frac{-5V}{3V} = -\frac{5}{3}.$$

For the waveforms in Fig. 2, we have the following calculation:

$$t = \tau \ln \left(2 - -\frac{5}{3} \right) = \tau \ln \left(\frac{11}{3} \right) \approx \tau \cdot 1.3 \text{ for output high,}$$

and

$$t = \tau \ln \left(2 - -0.6 \right) = \tau \ln \left(2.6 \right) \approx \tau \cdot 0.95 \text{ for output low.}$$

REF: [1] <https://www.fairchildsemi.com/datasheets/1N/1N914.pdf> (accessed 23 July 2017)