

**CIRCUIT:** The Wien bridge oscillator, see Fig. 1, consists of two voltage dividers. It oscillates (approximately) sinusoidally at the frequency that produces the same voltage out of both voltage dividers. When the two waveforms from the voltage divider are the same, the op-amp sees two waveforms that differ by the offset voltage of the op-amp, which is nonzero. This causes the output waveform at that frequency to be large, since changing the size of the output signal cannot eliminate the offset. This renders the negative feedback ineffective, and the open-loop gain of the op-amp applies to the offset voltage.

The Wien-bridge oscillator circuit is followed by a voltage follower with a DC-blocking capacitor.

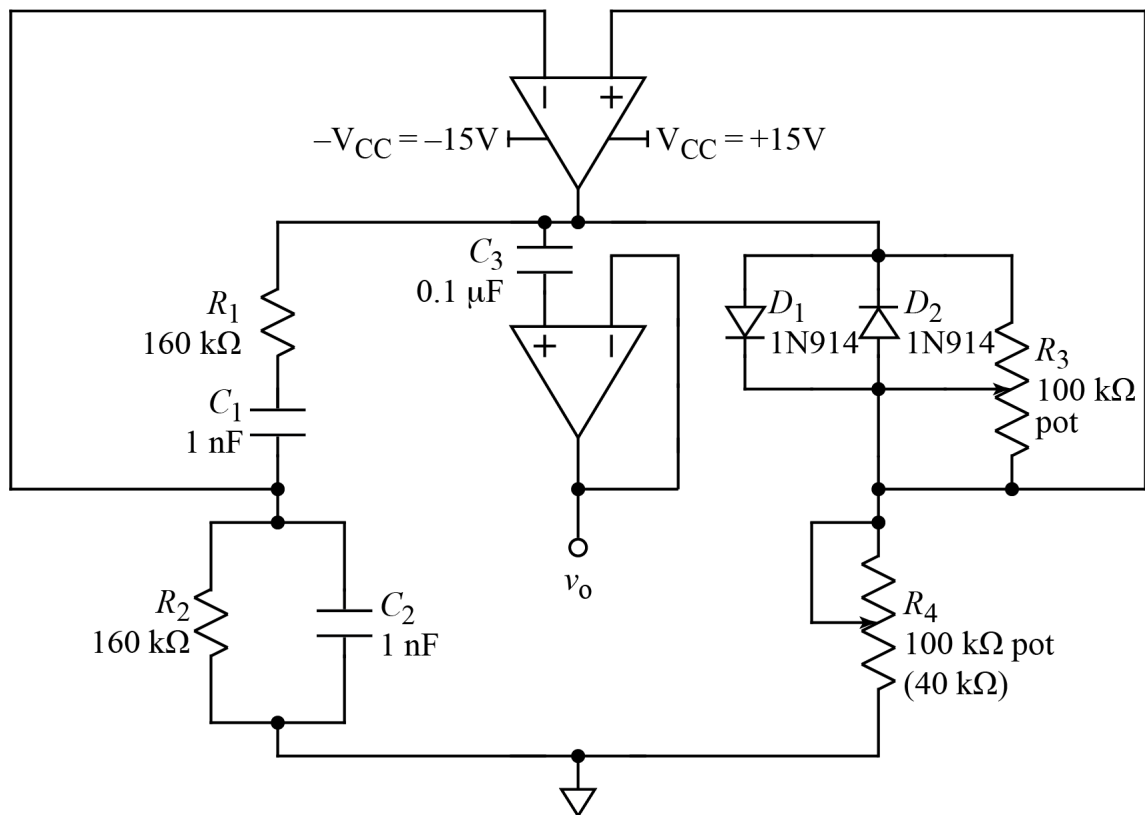


Fig. 1. Wien-bridge oscillator.

The diodes keep the output waveform from getting too large.

In terms of poles, the circuit has poles just to the right of the real axis. The diodes ensure that the poles are just to the right of the real axis at all times, preventing the output waveform from dying out if the poles were to drift into the left half-plane.

**Analysis of circuit** (skip to "To adjust the oscillator" if desired):

We equate the voltages out of the two voltage dividers and perform many steps of algebra to find the poles.

$$\frac{R_4}{R_3 + R_4} = \frac{R_2 \parallel \frac{1}{sC_2}}{R_1 + \frac{1}{sC_1} + R_2 \parallel \frac{1}{sC_2}}$$

or

$$\frac{1}{1 + \frac{R_3}{R_4}} = \frac{1}{1 + \frac{R_1 + \frac{1}{sC_1}}{R_2 \parallel \frac{1}{sC_2}}}$$

or

$$1 + \frac{R_1 + \frac{1}{sC_1}}{R_2 \parallel \frac{1}{sC_2}} = 1 + \frac{R_3}{R_4}$$

or

$$\frac{R_1 + \frac{1}{sC_1}}{R_2 \parallel \frac{1}{sC_2}} = \frac{R_3}{R_4}$$

or

$$R_1 + \frac{1}{sC_1} = \frac{R_3}{R_4} \cdot R_2 \parallel \frac{1}{sC_2}$$

or

$$R_1 + \frac{1}{sC_1} = \frac{R_3}{R_4} \cdot R_2 \parallel \frac{1}{sC_2}$$

or

$$R_1 + \frac{1}{sC_1} = \frac{R_3}{R_4} \cdot \frac{\frac{R_2}{sC_2}}{R_2 + \frac{1}{sC_2}} = \frac{R_3}{R_4} \cdot \frac{R_2}{1 + sR_2C_2}$$

or

$$\frac{1 + sR_1C_1}{sC_1} = \frac{R_3}{R_4} \cdot \frac{R_2}{1 + sR_2C_2}$$

or

$$s^2 R_1 C_1 R_2 C_2 + s(R_1 C_1 + R_2 C_2) + 1 = sR_2 C_1 \frac{R_3}{R_4}$$

or

$$s^2 + s \left( \frac{1}{R_2 C_2} + \frac{1}{R_1 C_1} \right) + \frac{1}{R_1 C_1 R_2 C_2} = s \frac{1}{R_1 C_2} \frac{R_3}{R_4}$$

or

$$s^2 + s \left( \frac{1}{R_2 C_2} + \frac{1}{R_1 C_1} - \frac{1}{R_1 C_2} \frac{R_3}{R_4} \right) + \frac{1}{R_1 C_1 R_2 C_2} = 0$$

or

$$s^2 + s \left( \frac{1}{\tau_{22}} + \frac{1}{\tau_{11}} - \frac{1}{\tau_{12}} \frac{R_3}{R_4} \right) + \frac{1}{\tau_{11} \tau_{22}} = 0$$

or

$$s = -\frac{1}{2} \left( \frac{1}{\tau_{11}} + \frac{1}{\tau_{22}} - \frac{1}{\tau_{12}} \frac{R_3}{R_4} \right) \pm \sqrt{\left[ \frac{1}{2} \left( \frac{1}{\tau_{11}} + \frac{1}{\tau_{22}} - \frac{1}{\tau_{12}} \frac{R_3}{R_4} \right) \right]^2 - \frac{1}{\tau_{11} \tau_{22}}}$$

For purely imaginary roots, we want the real part (in front of the square root), to be zero. In actuality, we want the real part to be just slightly positive so our poles will be in the right half-plane.

$$-\frac{1}{2} \left( \frac{1}{\tau_{11}} + \frac{1}{\tau_{22}} - \frac{1}{\tau_{12}} \frac{R_3}{R_4} \right) \cong 0$$

or

$$\left( \frac{1}{\tau_{11}} + \frac{1}{\tau_{22}} - \frac{1}{\tau_{12}} \frac{R_3}{R_4} \right) = 0$$

or

$$\left( \frac{1}{R_1 C_1} + \frac{1}{R_2 C_2} - \frac{1}{R_1 C_2} \frac{R_3}{R_4} \right) = 0$$

or

$$R_1 C_1 + R_2 C_2 - R_2 C_1 \frac{R_3}{R_4} = 0$$

or

$$\frac{R_1}{R_2} + \frac{C_2}{C_1} - \frac{R_3}{R_4} = 0$$

or

$$\frac{R_3}{R_4} = \frac{R_1}{R_2} + \frac{C_2}{C_1}$$

For the roots to be in the right half-plane,  $R_3/R_4$  must be larger than the right side of the equation. The diodes in the circuit, move the poles toward the left half-plane by lowering the value of  $R_3$  when the amplitude of the output signal gets too large.

$$s = \pm j \sqrt{\frac{1}{\tau_{11} \tau_{22}}} = \pm j \sqrt{\frac{1}{R_1 C_1 R_2 C_2}}$$

If  $C_1 = C_2 = 1$  nF, we get poles at audio frequencies using  $R$ 's that draw only modest current from the op-amp.

$$s = \pm j \frac{1}{C_1} \sqrt{\frac{1}{R_1 R_2}} = \pm j 1 \text{Gr/s} \sqrt{\frac{1}{R_1 R_2}}$$

For example, if we want an oscillation frequency at 1 kHz, we have the following calculations:

$$s = \pm j1 \text{Gr/s} \sqrt{\frac{1}{R_1 R_2}} = \pm j1 \text{Gr/s} \sqrt{\frac{1}{R_1 R_2}} = \pm j1 \text{kHz} \cdot 2\pi$$

or

$$\sqrt{\frac{1}{R_1 R_2}} = \frac{1 \text{kHz} \cdot 2\pi}{1 \text{Gr/s}}$$

or

$$R_1 R_2 = \left( \frac{1 \text{Gr/s}}{1 \text{kHz} \cdot 2\pi} \right)^2 \cong (160 \text{k}\Omega)^2$$

For  $R_1 = R_2$  we have a solution with a standard 5% resistor value:

$$R_1 = R_2 = 160 \text{k}\Omega$$

For this solution, we need  $R_3 = 2R_4$  for poles on the imaginary axis.

Now we turn to the question of how to pick  $R_3$  so that the peak current through  $R_3$  will result in a voltage across the diodes that will conduct enough current to move poles to the left half-plane. That is, the current in the diodes should be a significant proportion of the current in  $R_3$ .

We assume a desired magnitude 1 V sinusoidal output.

TABLE I: 1N914 DIODE  $i$ - $v$  DATA (FAIRCHILD) [1]

$i_d$	$v_d$
1 $\mu\text{A}$	0.273 V
5 $\mu\text{A}$	0.352 V
10 $\mu\text{A}$	0.380 V
100 $\mu\text{A}$	0.505 V

Since  $R_3 = 2R_4$  and the output voltage is across  $R_4$ , we will have 1 V across  $R_4$  and 2 V across  $R_3$ . Say the value of  $R_3 = 100 \text{ k}\Omega$ .

$$i_{R3} = \frac{2 \text{ V}}{100 \text{ k}\Omega} = 20 \mu\text{A}$$

Say we wish to have 25% of the current in  $R_3$ , i.e.,  $5 \mu\text{A}$ , flowing in the diodes. This effectively reduces the resistance to an equivalent of  $R_3 = 80 \text{ k}\Omega$ . Thus, we adjust  $R_4$  to  $40 \text{ k}\Omega$  so it will be half the value of the equivalent  $R_3$ . From the data for the 1N914 diode, the voltage drop across the diodes will be 0.352 V.

The part of  $R_3$  that drops 0.352 V when the current is  $10 \mu\text{A}$  is given by Ohm's law:

$$R_{3 \text{ top}} = \frac{0.352 \text{ V}}{10 \mu\text{A}} = 35.2 \text{ k}\Omega$$

**To adjust the oscillator**, first adjust  $R_4$  until the circuit oscillates. Then adjust  $R_3$  until the amplitude of the oscillation is as desired.

**REF:** [1] <https://www.fairchildsemi.com/datasheets/1N/1N914.pdf> (accessed 23 July 2017)