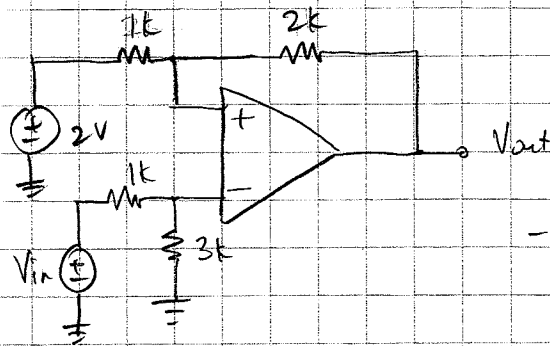


Review Problems


(± 5 V Supplies)

Example:



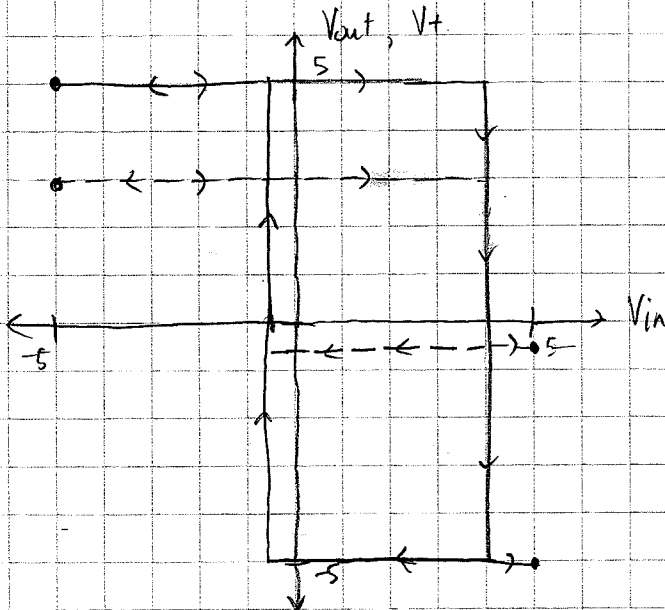(a) Plot VTC for Vout vs Vin and V+ vs Vin.

- start at $V_{in} = -5V \rightarrow V_- = -3.75V$
 $\rightarrow V_{out} = 5V$
 $\rightarrow V_+ = 2 + \frac{(5-2) \cdot 1}{1+2} = 3V$



\rightarrow Switches when $V_+ = V_-$

$$3 = V_{in} \cdot \frac{3}{4}$$

$$\Rightarrow V_{in} = 4V$$

- then $V_{out} = -5V$, $V_+ = 2 - \frac{(5+2) \cdot 1}{1+2} = -0.33V$


\rightarrow Now head back in other direction

- Switches when $V_+ = V_-$


$$-0.33 = V_{in} \cdot \frac{3}{4}$$

$$\Rightarrow V_{in} = -0.44V$$

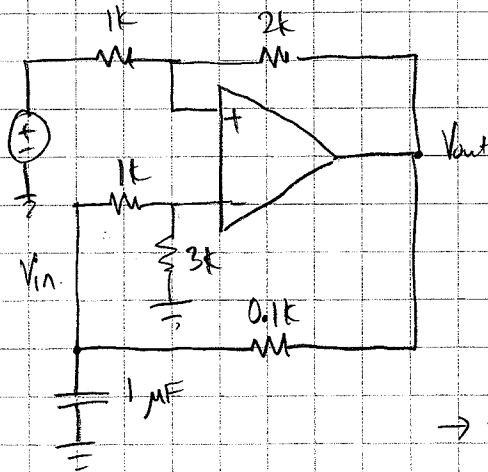(b) Extra R & C are added, what is the freq. of oscillation?



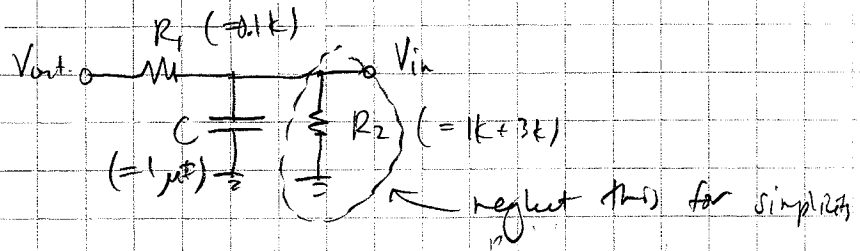- After output switches, Vin changes through R-C network:



$$\rightarrow \text{Find } \frac{V_{in}}{V_{out}} = \frac{1/sC}{R_1 + 1/sC}$$

$$= \frac{1}{1 + sR_1C}$$

1 + sR1C

$$= \frac{R_1/R_2 C}{R_1/R_2 C + s} = H(s) \quad \rightarrow \text{Let } V_{out}(t) = u(t) \quad (\text{step})$$

$$\therefore V_{out}(s) = \frac{1}{s}$$

$$H(s) = \frac{R_1/R_2 C}{R_1/R_2 C + s}$$

$$\rightarrow U_{in}(s) = \frac{1}{s} \cdot H(s)$$


Inverse Laplace transform: $\frac{\alpha}{s(s+\alpha)} \Leftrightarrow (1 - e^{-\alpha t}) u(t)$

$$\Rightarrow \text{So, } V_{in}(t) = (1 - e^{-\alpha t}) u(t) \quad \text{where } \alpha = \frac{1}{R_1 C}$$

$$= \frac{1}{4k \cdot 100 \cdot 10^{-6}}$$

$$= 1.25 \cdot 10^4$$

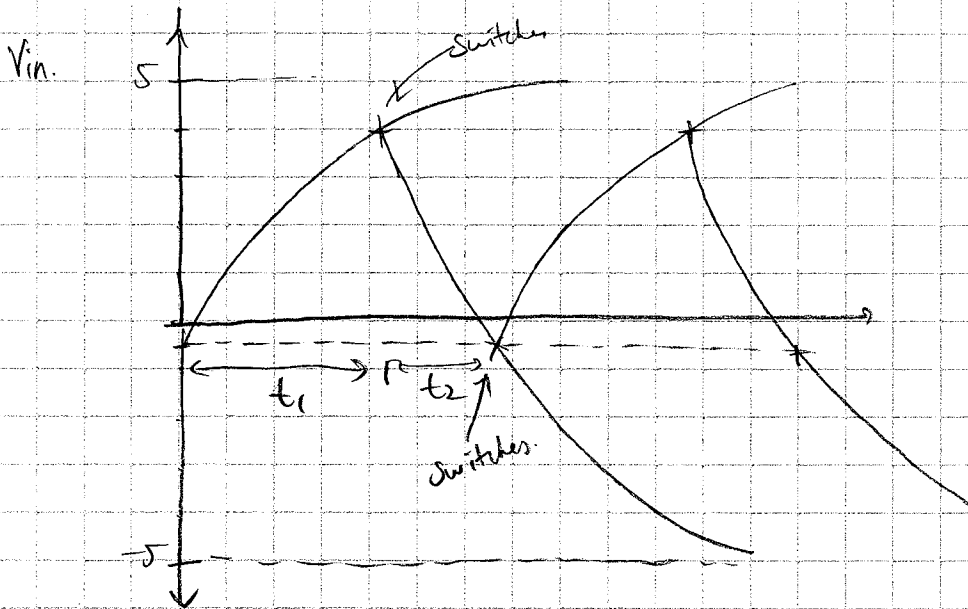→ Let's plot output, assuming V_{in} starts at -0.44
 - V_{out} switches to $5V$.



→ Calculate t_1, t_2 : $t_1: V_{in} = -0.44 + 5.44(1 - e^{-\alpha t}) = 4$

$$1 - e^{-\alpha t} = \frac{4.44}{5.44}$$

$$e^{-\alpha t} = 0.18$$

$$-\alpha t = \ln(0.18)$$

$$t = \frac{\ln(0.18)}{-1.25 \cdot 10^4} = 1.71 \cdot 10^{-4}$$

$$t_2: V_{in} = 4 - 9(1 - e^{-\alpha t}) = -0.44$$

$$1 - e^{-\alpha t} = \frac{4.44}{9}$$


$$e^{-\alpha t} = 0.507$$

$$-\alpha t = \ln(0.507)$$

$$t = \frac{\ln(0.507)}{-1E4} = 6.79E-5$$

$$\Rightarrow \text{freq} = \frac{1}{T_p} = \frac{1}{t_1 + t_2} = \frac{1}{1.71E-4 + 6.79E-5} = 4186 \text{ Hz.}$$

Next Example:

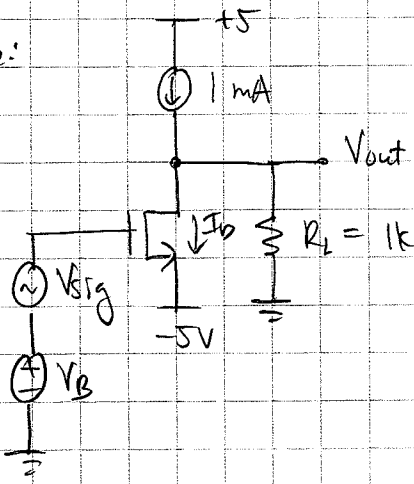

$$-V_E = 1V, \mu_n \text{ Cox } \frac{W}{L} = 2E-3$$

(a) Choose V_B to get $V_{out} = 0V$ for $V_{sig} = 0$.

$$\text{need } I_D = 1 \text{ mA} = \frac{\mu_n \text{ Cox } W}{2L} (V_{GS} - V_E)^2$$

$$1E-3 = 1E-3 \cdot (V_{GS} - V_E)^2$$

$$V_{GS} - V_E = 1V$$

$$V_{GS} = 2V.$$

$$\rightarrow \text{Need } V_B = -3V.$$

(b) For $V_{sig} = 0.7 \cdot \sin(\omega t)$, find min. & max of V_{out} .

- V_{GS} varies from 1.3V to 2.7V.


$$\rightarrow V_{GS} = 1.3V: I_D = 1E-3(0.3)^2 = 0.09 \text{ mA.}$$

$$\rightarrow V_{out} = (1 \text{ mA} - 0.09 \text{ mA}) \cdot 1k = 0.91V$$

$$\rightarrow V_{GS} = 2.7V: I_D = 1E-3(1.7)^2 = 2.89 \text{ mA}$$

$$\rightarrow V_{out} = (1 \text{ mA} - 2.89 \text{ mA}) \cdot 1k = -1.89V$$

(c) Plot V_{in} , V_{out} , I_D

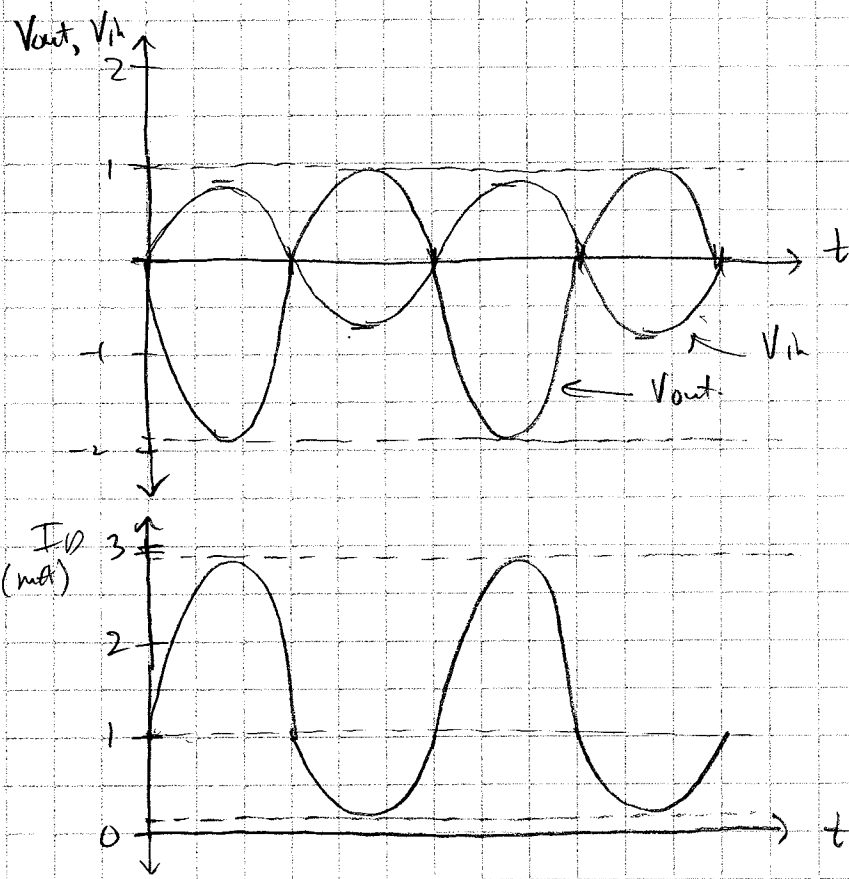

(d) Calculate efficiency

→ Power from supplies:

- positive supply: $P = I \cdot V = 1 \text{ mA} \cdot 5 \text{ V} = 5 \text{ mW}$

- negative supply: Avg. current $\approx \frac{2.89 + 0.09}{2} = 1.49 \text{ mA}$

$$P = I_{\text{avg}} \cdot V = 1.49 \text{ mA} \cdot 5 \text{ V} = 7.45 \text{ mW}$$

→ Power to Load: $P = \frac{V_{\text{rms}}^2}{R} = \left[\frac{(0.91)^2}{2 \cdot 10^3} + \frac{(1.89)^2}{2 \cdot 10^3} \right] \cdot 0.5$
 $= 1.1 \text{ mW}$

→ Efficiency $\eta = \frac{1.1}{7.45} = 14.8\%$

(e) Why so much distortion?

C.S. small signal: $A_v = g_m \cdot R_L$

C.D. small signal: $A_v = \frac{g_m \cdot R_L}{1 + g_m \cdot R_L} \approx 1$

doesn't depend on g_m