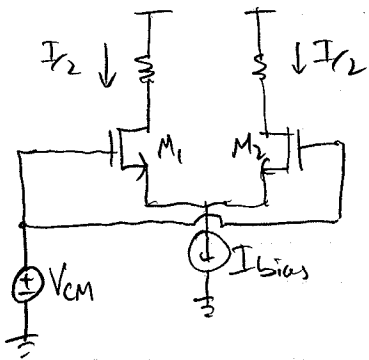


Recap from last class: Differential Pair

- Two parts to analysis:
- ① Large Signal \rightarrow common mode bias (a)
 \rightarrow differential mode bias (b)
 - ② Small Signal \rightarrow differential signal gain (a)
 \rightarrow common mode signal gain (b)


① (a) Large Signal Common Mode Bias



\rightarrow How low/high can the bias voltage on the gates of M_1, M_2 be before the diff. pair stops functioning?


- High: M_1, M_2 pushed out of saturation into triode.
- Low: I_{bias} current source needs minimum output voltage.

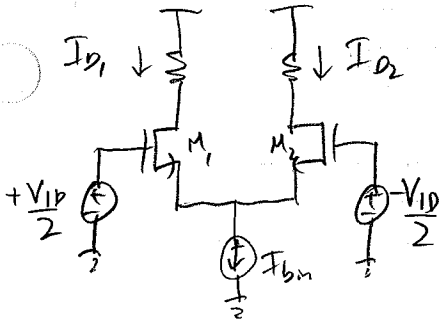① (b) Large Signal Differential Mode Bias




\rightarrow DC transfer function of I_{D1}, I_{D2} as we sweep V_{id} from $-\sqrt{2}V_{ov}$ to $+\sqrt{2}V_{ov}$

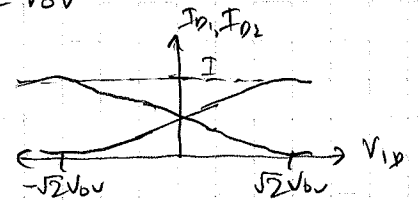- current switches from one side to the other



② (a) Small Signal Diff. Gain

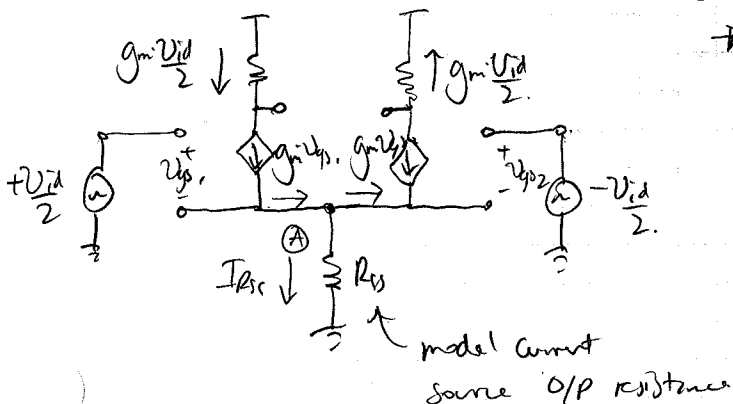- Calculate bias conditions, plug in S.S. models




\rightarrow Why is node A a virtual ground?

KCL @ A: $g_m \frac{V_{id}}{2} + (-g_m \frac{V_{id}}{2}) + \frac{V_A}{R_{SS}} = 0$

$\Rightarrow \frac{V_A}{R_{SS}} = 0 \rightarrow \boxed{V_A = 0}$

model current source O/P resistance

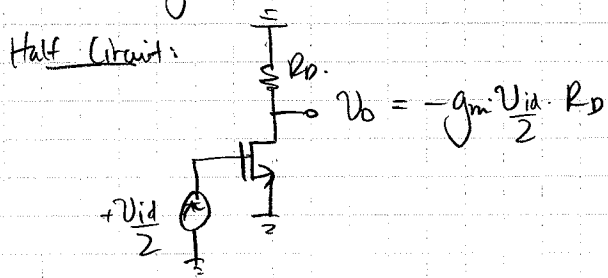
→ S_2 can split into two half circuits.
 - analyze one half circuit, if output is taken differentially, gain will be 2x that of half circuit.



Single Ended Output: $A_d = \frac{V_{o2}}{V_{id}} = \frac{g_m \cdot R_D}{2}$


Diff. Output: $A_d = \frac{V_{o2} - V_{o1}}{V_{id}} = g_m \cdot R_D$

② (b) Small Signal Common Mode Gain

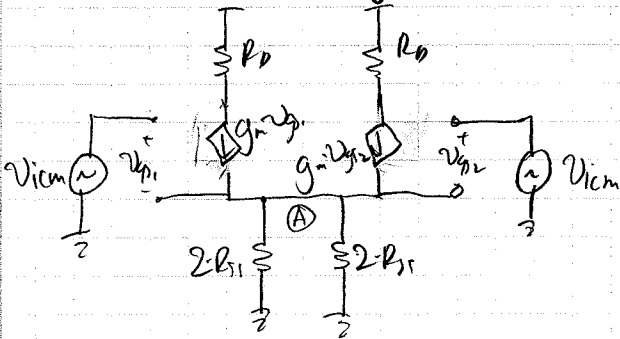

- Can no longer assume (A) is a virtual ground, since R_{SS} will have a net current flow through it.

- split into half circuits:

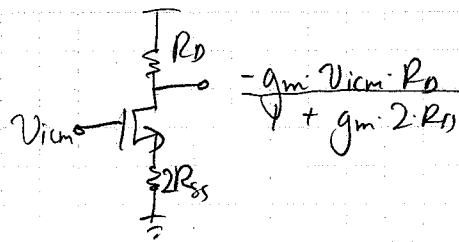

Single-Ended Output: $A_{cm} = \frac{V_{o2}}{V_{icm}} \approx \frac{R_D}{2 \cdot R_{SS}}$ (assuming $\frac{1}{g_m} \ll 2 \cdot R_{SS}$)

Diff. Output: $A_{cm} = \frac{V_{o2} - V_{o1}}{V_{icm}} = 0$