

- HW due
- Lecture notes will be posted online.
- I will put reading assignments in notes (do it before attempting homework)

Ch.1 reading: 1.1 (ignore graded junctions, forward biased junctions)  
 1.2 (all)  
 1.5 (for reference)

Up Until Now: - reviewed MOSFET characteristics at the device level.

Summary of Important Large Signal Concepts & Equations

① Diodes: We only care about diodes in that a MOSFET has reverse biased PN junctions for which we want to know the parasitic capacitances.

Built in potential: 
$$\Phi_0 = \frac{kT}{q} \ln\left(\frac{N_A N_D}{n_i^2}\right)$$



Reverse biased junction capacitance: 
$$C_j = \frac{C_{j0}}{\sqrt{1 + V_R/\Phi_0}}$$
, where 
$$C_{j0} = \sqrt{\frac{q \cdot \epsilon_s \cdot \epsilon_0 \cdot N_A \cdot N_D}{2 \cdot \Phi_0 (N_A + N_D)}}$$

*(Note:  $V_R$  in text points to  $V_R/\Phi_0$ )*

Notes:

- Units are per unit area.
- These are small signal equations, valid for a particular bias point.

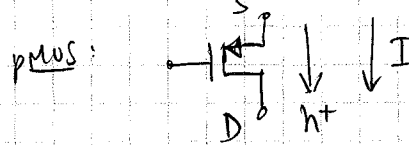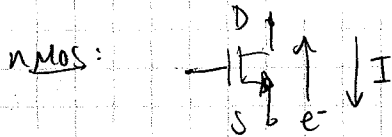
② MOSFETS: MOSFETS are symmetrical devices, designation of drain or source is determined by biasing and direction of current flow.  
 - carriers flow from source to drain



Three important operating regions: 1) Cutoff:  $V_{GS} < V_t$ , no conductive channel forms

$$I_D = 0 \quad (1)$$

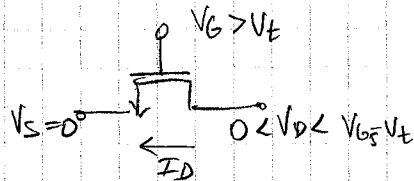
2) Triode: If we increase  $V_{GS} > V_t$ , conductive channel forms. Now if we raise  $V_D$  a current will flow



$$I_D = \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right] \quad (2)$$

- transistor functions like a resistor

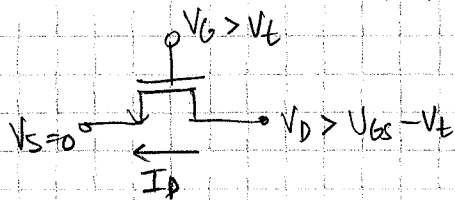2  
 3) Active/Saturation: For the same  $V_{GS}$ , if we continue to increase  $V_D$ , channel pinches off and current does not increase further. (to a first order approx.)



$$I_D = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 \quad (3)$$


- transistor acts like a current source.

→ In reality, as  $V_{DS}$  increases further it does have a small effect on  $I_D$ .  
 - to model these effects we can add a multiplying factor to (3):

$$I_D = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) \quad (4)$$

- slightly different from expression in text.

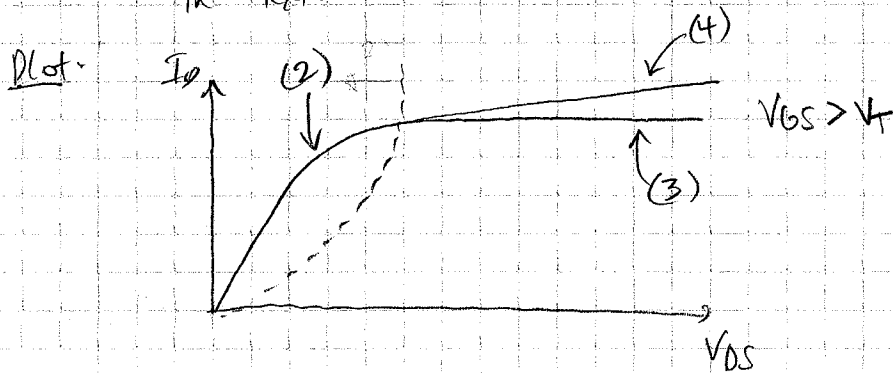$= \frac{1}{V_A}$  don't worry about calculating this.



→ Another important large signal equation is for body effect, which changes  $V_T$  in (2), (3), and (4)

Body effect:

$$V_{th} = V_{th0} + \gamma (\sqrt{|V_{SB} + 2\Phi_F|} - \sqrt{|2\Phi_F|})$$

↑ don't worry about calculating this

→ Final important equation is for charge stored in channel, which can be important when designing switches:

$$Q_{ch} = W \cdot L \cdot C_{ox} (V_{GS} - V_T) \quad \text{where} \quad C_{ox} = \frac{\epsilon_{ox} \epsilon_0}{t_{ox}}$$

↑ oxide thickness.

### PMOS Transistors



→ All preceding equations have been for NMOS.

- exact same equations can be used for PMOS by taking absolute values of everything ( $V_{GS}$ ,  $V_T$ ,  $V_{DS}$ ) and then using common sense to decide in which direction current will flow. (from low voltage to high)


3

Example: For the following transistors, with  $V_{th} = |V_{tp}| = 1V$  and  $V_{DD} = 5V$ :

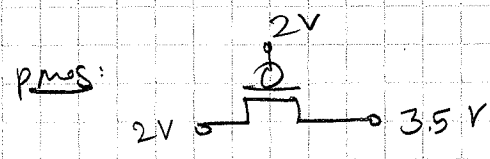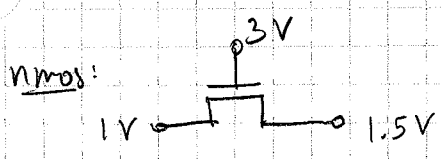- (a) Denote direction of current flow, and source & drain
- (b) Determine region of operation.
- (c) Calculate  $I_D$ .



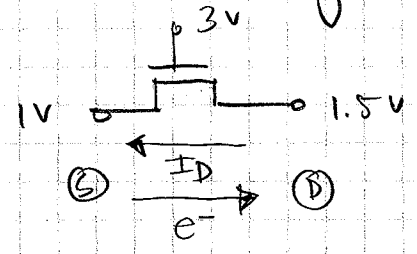nmos: (a) Current flows from high to low voltage:



- majority carriers are electrons, which flow from source to drain


- (b)  $V_{GS} = 3 - 1 = 2V, > V_{th} = 1V$ , so not in cutoff.
- $V_{DS} = 1.5 - 1 = 0.5V, < V_{eff} = V_{GS} - V_t = 2 - 1 = 1V$
- $\therefore$  in triode region.

(c)  $I_D = \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_t) V_{DS} - \frac{V_{DS}^2}{2} \right]$

- body effect?  $V_B = 0V$  (implied since not shown)


$\rightarrow V_{SB} = 1V.$

- calculate new  $V_t$  using  $V_t = V_{th0} + \gamma \left( \sqrt{V_{SB} + 2|\Phi_F|} - \sqrt{2|\Phi_F|} \right)$

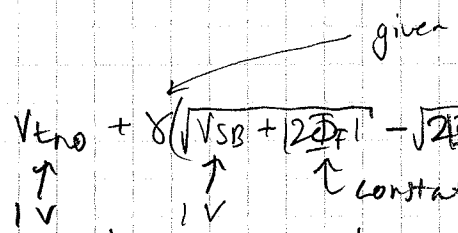

- finally, find  $I_D$  using this value in equation above.

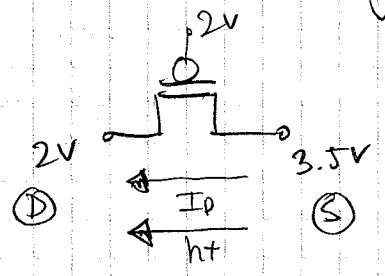pmos: (a) Current flows from high to low voltage



- majority carriers are holes, which flow from source to drain.

- (b)  $|V_{GS}| = 3.5 - 2 = 1.5V, > |V_{tp}| = 1V$ , not in cutoff.
- $|V_{DS}| = 3.5 - 2 = 1.5V, > V_{eff} = |V_{GS}| - |V_{tp}| = 1.5 - 1 = 0.5V$
- $\therefore$  in active (saturation) region.

4

$$I_D = \frac{\mu_n C_{ox} \cdot W}{2} (V_{GS} - V_{T0})^2 (1 + \lambda |V_{DS}|)$$

↑ given

Body effect?  $V_B = 5V$  (implied since not shown)

$$\rightarrow |V_{SB}| = 5 - 3.5 = 1.5V$$


- calculate  $V_T$  using  $|V_{TE}| = |V_{T0}| + \gamma (\sqrt{|V_{SB}| + 2|\Phi_F|} - \sqrt{2|\Phi_F|})$

- finally, find  $I_D$ .

### Small Signal Models

- Small signal models depend on what region the transistor is in.

#### ① Active Region

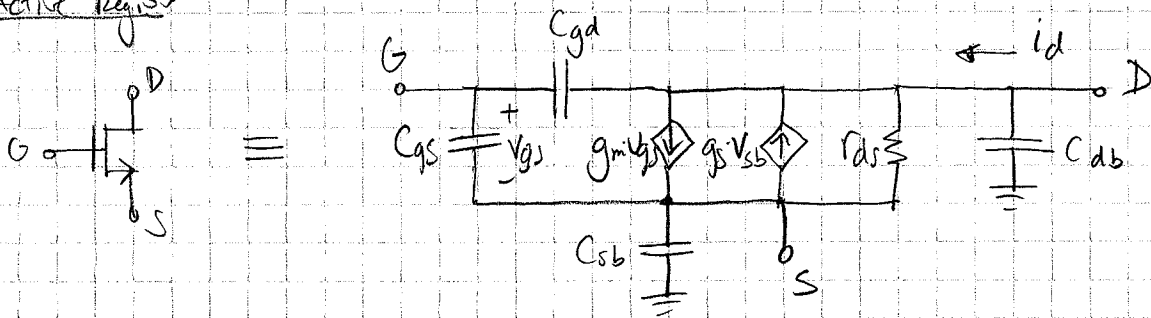



- Same model used in 3110, but with extra capacitors and one extra transconductor.

→ let's go through components one at a time and see where they come from




- models change in  $i_D$  for a change in  $V_{GS}$
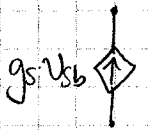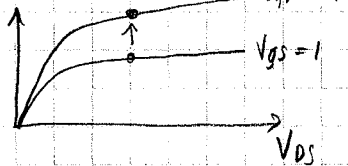
$$\therefore g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TE}) = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$$




- models change in  $i_D$  due to increase in  $V_T$  coming from body effect  
 - "back gate" effect  
 - note direction is opposite to  $g_m$ , since increasing  $V_{SB}$  reduces  $I_D$ .

$$g_s = \frac{\partial I_D}{\partial V_{SB}} = \frac{\partial I_D}{\partial V_T} \frac{\partial V_T}{\partial V_{SB}} = \dots \text{(derivation in text)} = \frac{\gamma g_m}{2\sqrt{|V_{SB}| + 2|\Phi_F|}}$$

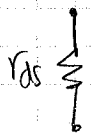

- models finite slope of  $i_D - V_{DS}$  curve (early effect)
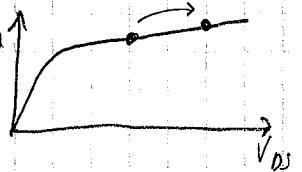
$$\frac{1}{r_{ds}} = \frac{\partial I_D}{\partial V_{DS}} = \dots \text{(derivation in text)} = \lambda \cdot I_D$$



$$\rightarrow r_{ds} = \frac{1}{\lambda \cdot I_D}$$

↑ can calculate, but will usually be given to you