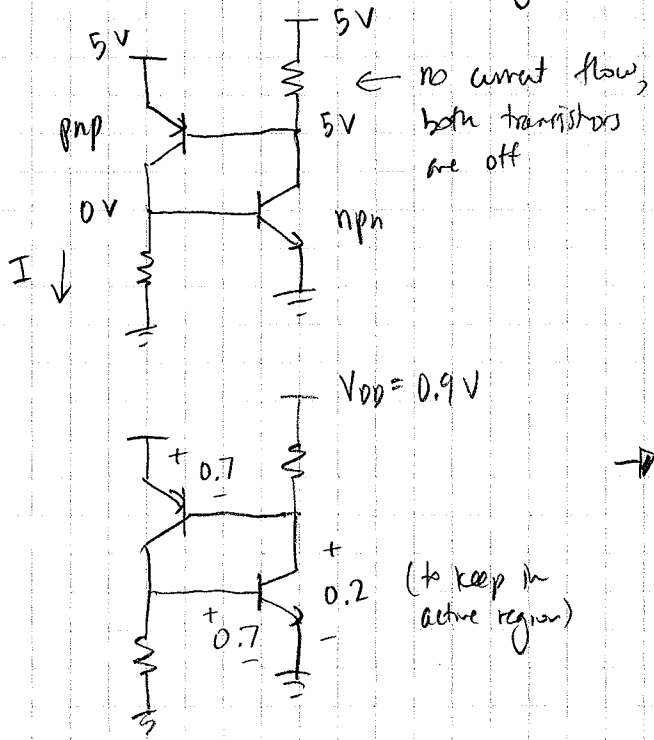


- Consider the circuit formed by the parasitic bipolars:



- Consider the case when for some reason a current flows in the substrate (I)
- Voltage at base of npn rises, turning it on.
- This causes current to flow in other resistor, dropping voltage at base of pnp, turning it on.
- positive feedback, until:

→ Power supply is shorted out to 0.9 V
 - chip catches on fire
 - not good.

Moral of the story:

- Need to keep gain around the feedback loop low
- remember the feedback with gain < 1 will die out.
- do this by keeping gain of two common emitter stages low
- make parasitic resistors (R_p & R_n) small

- How to do this?

- Resistance is a function of two things: doping and size
- have p+ layer under p- substrate (controlled by process guys)
- reduce distance with lots of substrate contacts
- modern processes have design rules with minimum substrate contact distances.


5720/6720: Lecture #6

Jan. 24

Ch. 3: Circuit Design!

- Start with current mirrors: Read Ch. 3 sections 3.1, 3.5, 3.6

Basic Current Mirror [3.1]

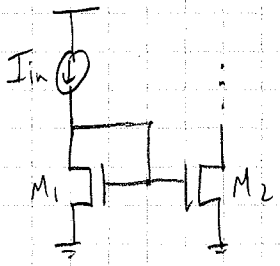

- Consider M_1
- as I_{in} flows, gate of M_1 charges up until it turns on
- M_1 will be in saturation, since $V_{GS} = V_{DS} \Rightarrow V_{DS} > V_{GS} - V_T$

→ M_1 configuration (gate shorted to drain) is called diode connected since $I-V$ characteristics resemble those of a diode.

→ For M_1 (neglecting channel length modulation):

$$I_{D1} = \frac{\mu_n C_{ox} (W/L)_1}{2} (V_{GS1} - V_T)^2$$


- Can solve this to find V_{GS1}

→ Now, $V_{GS1} = V_{GS2}$, so if we assume V_{DS2} is high enough to put it in saturation and ignore C.L.M., we have:

$$I_{D2} = I_{D1} \frac{(W/L)_2}{(W/L)_1}$$

- current in both devices is same, scaled by their (W/L) ratios

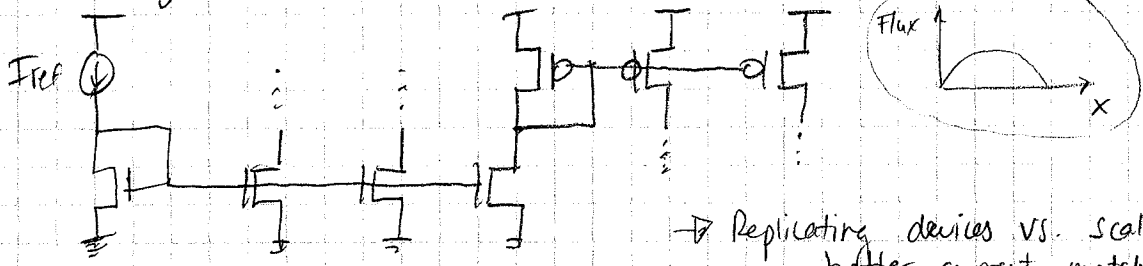
→ Using this circuit, a bias current can be replicated and scaled across many devices:



→ Replicating devices vs. scaling widths
 - better current matching
 - edge effects.

→ What about small signal behavior?

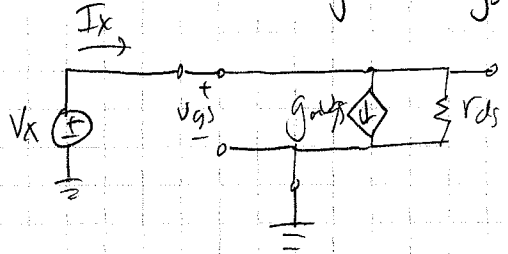- First consider diode connected transistor:
 - usually we analyze current mirrors for low frequency signals
 - ignore parasitic capacitors (open circuit)
 - sources are at ground (no body effect)
 - ignore g_s




- Connect test source V_x , find I_x .

$$I_x = g_m V_x + \frac{V_x}{r_{ds}}$$


$$\therefore R_{in} = \frac{V_x}{I_x} = \left(g_m + \frac{1}{r_{ds}} \right)^{-1} = \frac{1}{g_m} \parallel r_{ds}$$

→ Usually $r_{ds} \gg \frac{1}{g_m}$, $\therefore R_{in} \approx \frac{1}{g_m}$

So, equivalent s.s. model is:

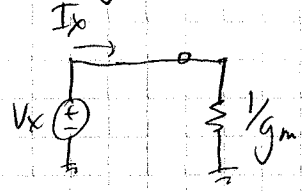

Now consider entire circuit:

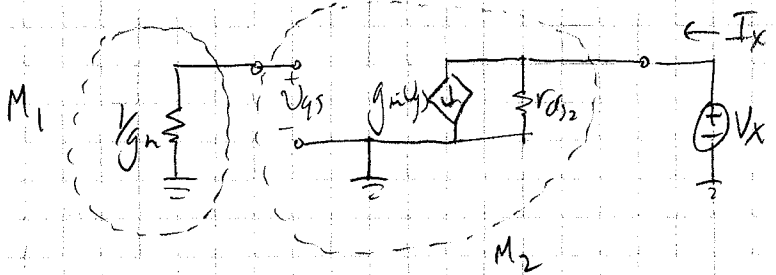

- Open circuited current source.


- We used the simplified model for M_1 (valid since it is diode connected)

- Let's find output impedance.

3

- $V_{gs2} = 0$, \therefore gm current source will be off:

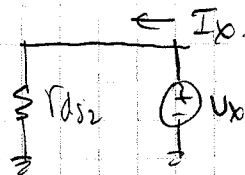
$$\therefore r_{in} = \frac{V_{gs}}{I_{gs}} = r_{ds2} \quad (\text{easy!})$$



→ For the assumption neglecting C.L.M., $r_{ds} = \infty$, but in general r_{ds} will have an effect and we need to consider it.

In general, $r_{ds} \propto \frac{L}{I_D}$.

Example:

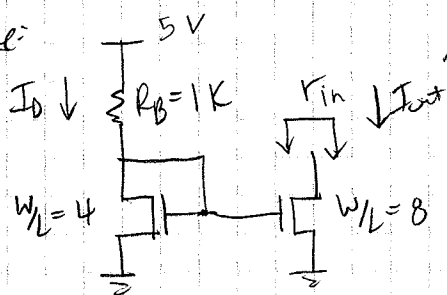

$$Mn_{tox} = 100 \frac{\mu A}{V^2}, \quad V_T = 1V, \quad r_{ds} = \frac{8000 \cdot L}{I_D \cdot \mu A}, \quad L = 1 \mu m$$

Find r_{in} .

- Need to solve large signal equations first

- DON'T use $1/g_m$ for any large signal calculations!!!

$$V_{gs} = 5 - I_D \cdot R_B$$

$$I_D = \frac{Mn_{tox}}{2} \left(\frac{W}{L}\right) (V_{gs} - V_T)^2 \rightarrow I_D = \frac{100E-6 \cdot 4}{2} (5 - I_D \cdot 1000 - 1)^2$$

→ quadratic equation with I_D : $I_D^2 \cdot 1E6 - I_D \cdot 13E3 + 16 = 0$

$$\text{solve using } X = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$


$$\rightarrow \underline{I_D = 1.376 \text{ mA}} \quad \text{or} \quad I_D = 11.6 \text{ mA} \quad \leftarrow \text{leads to -ve } V_{gs}$$

$$\therefore I_{out} = 2 \cdot I_D = 2.752 \text{ mA}$$

$$\therefore r_{in} = r_{ds} = \frac{8000 \cdot 1}{2.752} = 2.907 \text{ k}\Omega \quad (\text{small signal resistance})$$

↑ assuming it stays in saturation.

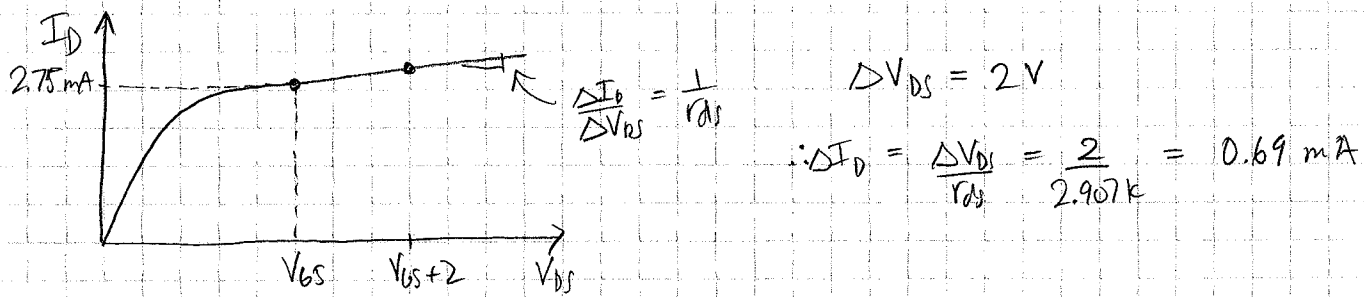Example: In prior example, assume V_{out} increases by 2V above V_{gs} , how much error is introduced into the output current?




→ This corresponds to a $\frac{0.69}{2.75} \times 100\% = 25\%$ error. (Significant!!)

- The finite output resistance of the standard current mirror is their biggest weakness, as it can lead to large errors in the output current.
- to address this we need some way of increasing the output resistance of the current mirror.


Source Regenerated Current Mirrors [3.5]

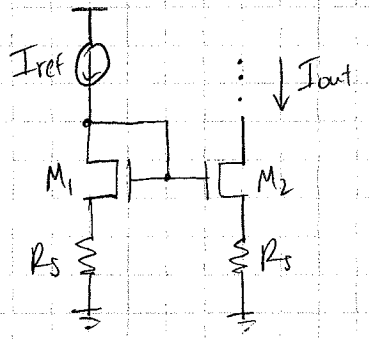- What if we put a resistor in the source of the transistor?



- Why include R_S in both legs? (Matching)
- Let's analyze small signal circuit to find output impedance.

Small signal equivalent:

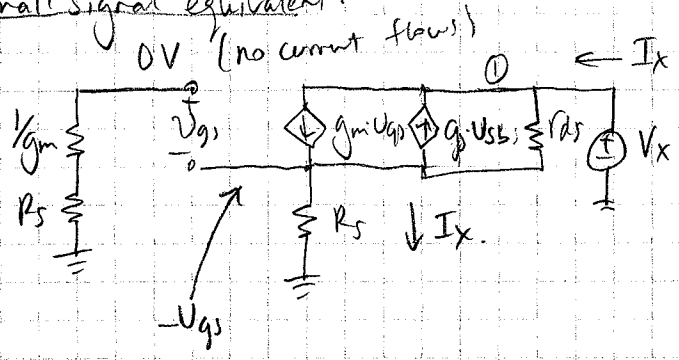

⊗ → $v_{gs} = -I_x \cdot R_S$

→ KCL @ ①: $I_x = g_m v_{gs} + \frac{V_x - (-v_{gs})}{r_{DS2}} - g_s \cdot (-v_{gs})$

Sub in ⊗: $I_x = -I_x \cdot R_S (g_m + g_s) + \frac{V_x - I_x R_S}{r_{DS2}}$
 $\rightarrow R_{out} = \frac{V_x}{I_x} = r_{DS2} \left[1 + R_S (g_m + g_s + \frac{1}{r_{DS2}}) \right]$
 $\approx r_{DS2} [1 + R_S (g_m + g_s)]$

(since $\frac{1}{r_{DS}}$ is small compared to g_m).

→ g_s is usually about 1/5 of g_m , so sometimes it is neglected to yield the simplified result:
 $R_{out} \approx r_{DS2} (1 + g_m R_S)$

Observations: - The o/p resistance has been increased over the nominal case by a factor of $(1 + R_S(g_m + g_s))$.

- This is a general result that is true when analyzing a source degenerated transistor

- Here the body effect works to our advantage, further increasing the output resistance.

Drawbacks: - Need to keep M_2 in saturation, R_S increases the minimum V_D for which this condition holds.

Example: Repeat prior example, but assume there was a source degeneration resistance of 400Ω .

(a) New R_{out} ?

(b) % error for 2V increase in V_{DS} ?

(c) $V_{out, min}$ for saturation?

(a) Need to find g_m (let's ignore g_s for simplicity)

$$g_m = \frac{2I_D}{V_{eff}}$$

$$V_{eff}: V_{DS} = 5V - I_D \cdot R_B \\ = 5 - 1.376 \text{ mA} \cdot 1k \\ = 3.62 \text{ V}$$

$$g_m = \frac{2 \cdot (2.75 \text{ mA})}{2.62} \\ = 2.1 \text{ mS}$$


$$\therefore V_{eff} = V_{DS} - V_T = 2.62 \text{ V}$$

$$\text{Now, } R_{out} \approx r_{ds2}(1 + g_m R_S) = 2.91 \text{ k}\Omega (1 + 2.1 \text{E-3} \cdot 400) = 5.35 \text{ k}\Omega$$

$$(b) \Delta I_D = \frac{\Delta V_{DS}}{R_{out}} = \frac{2}{5.35 \text{ k}} = 0.37 \text{ mA} \Rightarrow \frac{0.37}{2.75} \times 100\% = 13\% \text{ error (better!)}$$

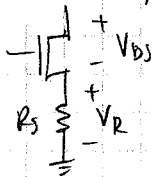(c) In prior case, we needed to maintain $V_{DS} > V_{DS} - V_T = V_{eff} = 2.62 \text{ V}$

→ now, we add voltage across resistor to this



$$V_R = I_{out} \cdot R_S = 2.75 \text{ mA} \cdot 400 = 1.1 \text{ V}$$

$$\Rightarrow V_{out, min} = V_R + V_{DS, min} = 1.1 + 2.62 = 3.72 \text{ V}$$

(reduction in headroom, tradeoff)

This gives some improvement but maybe we can do better.
- also resistors tend to be bulky and poorly controlled, we would like a solution using transistors only.