

Cook book and examples for single stub

Type 1 Series stub with same 50 ohm line

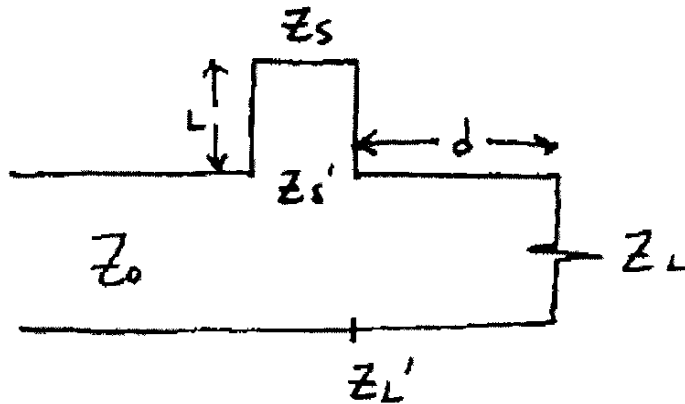


Fig:1 Series stub

- 1) Plot z_L ($z_L = Z_L/Z_0$, normalized)
- 2) Rotate z_L towards the generator until it reaches $r_L = 1.0$ circle (there will be two points, choose the closest one). This is the length (d) between the load and the stub.
- 3) Read the value of x_L at that point
- 4) Impedance of the stub $x_s = -x_L$
- 5) Plot x_s on the smith chart and calculate the length of the stub using one of the following two methods.
 - a) If you need a short circuited stub, distance (l) is measured from the short circuit point (Z_{sc}) towards generator to x_s .
 - b) If you need a open circuited stub, distance (l) is measured from the open circuit point (Z_{oc}) towards generator to x_s .
- 6) The new $z_{in} = 1 + j0$ (bull's-eye)

Type 2 Shunt stub with same 50 ohm line

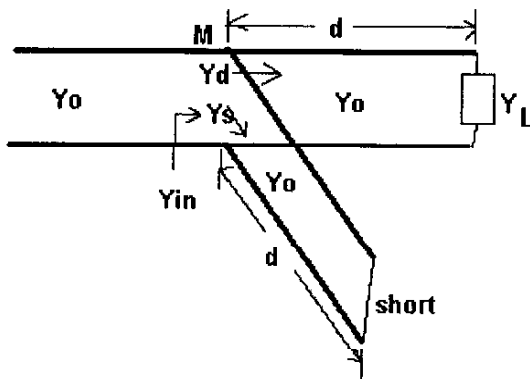


Fig:1 Shunt stub

1. Plot z_L . ($z_L = Z_L/Z_0$, normalized)
2. Reflect it through the origin to find y_L
3. Rotate y_L towards the generator until it reaches $r_L = 1.0$ circle (there will be two points, choose the closest one). This is the length (d) between the load and the stub.
4. Read the value of x_L
5. Impedance of the stub $x_s = -x_L$
6. Plot x_s on the smith chart and calculate the length of the stub using one of the following two methods.
 - a) If you need a short circuited stub, distance (l) is measured from the short circuit point (Y_{sc} not Z_{sc}) towards generator to x_s .
 - b) If you need a open circuited stub, distance (l) is measured from the open circuit point (Y_{oc} not Z_{oc}) towards generator to x_s .
7. The new $y_{in} = 1 + j0$ (bull's-eye)

Q) $Z_L = 75 - j20$
 $Z_0 = 50$

SHUNT STUB


The Complete Smith Chart
 Black Magic Design

Steps

1) $z_L = \frac{Z_L}{Z_0} = 1.5 - j0.4$

2) plot y_L

3) Rotate y_L to
 $R = 1$ circle.

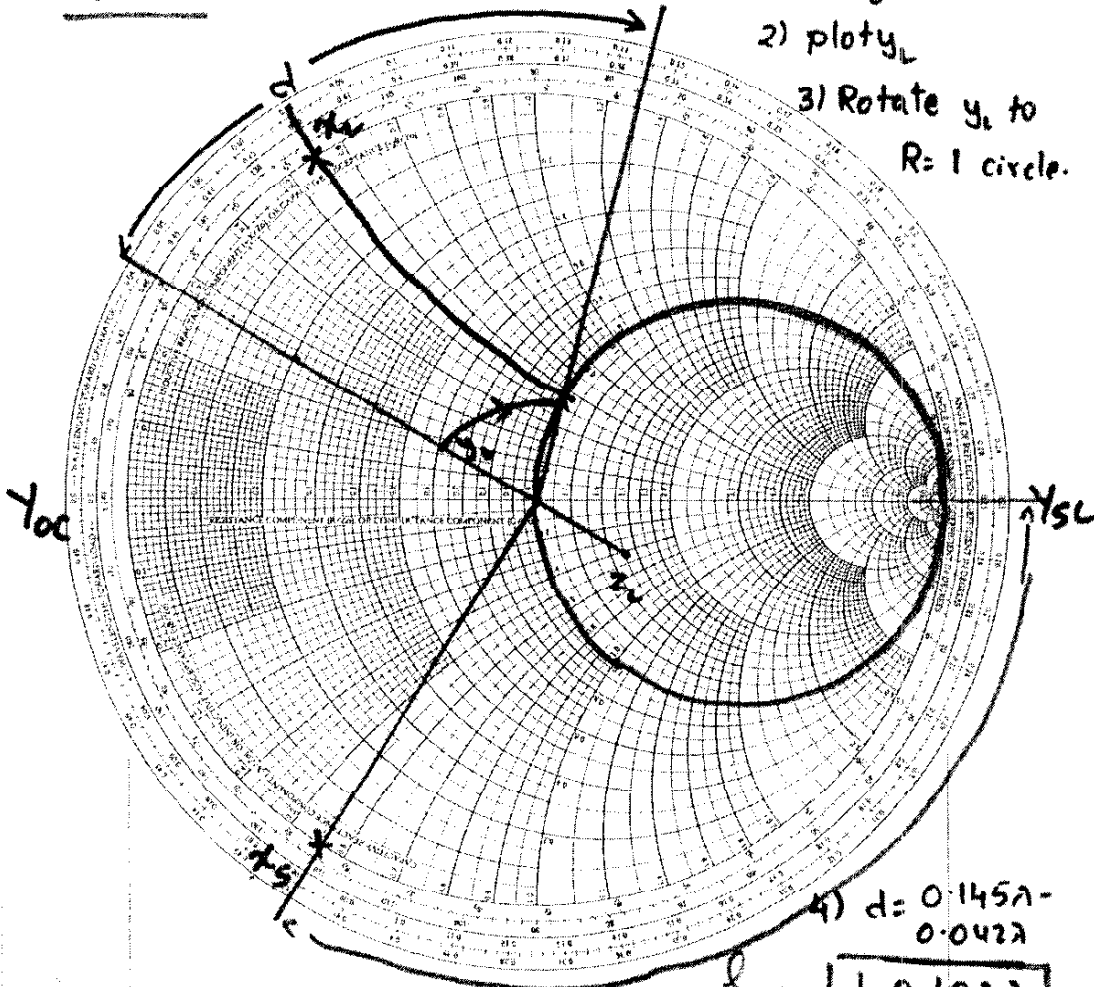

4) $d = 0.145\lambda - 0.042\lambda$

$d = 0.103\lambda$


5) Find $x_L = 0.55$

6) $x_S = -0.55$

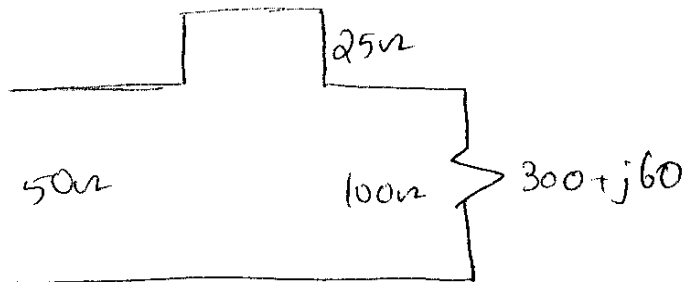7) length of sc stub

$l_{sc} = 0.4\lambda - 0.25\lambda = 0.17\lambda$


Type 3 Series stub with different line impedances



1. Normalise Z_L with respect to Z_{O2} and plot Z_{LN}
2. Get the new matching circle Z_A/Z_{O2}
3. Rotate Z_{LN} towards the generator to the matching circle. This point is Z_{AN} .
Calculate the distance (d) of stub from load
4. Renormalize Z_{AN} to get Z_A ($Y_A = Z_{AN} Z_{O2}$).
5. $Z_{\text{stub}} = -Z_A$ (imaginary part)
6. Normalize Z_{stub} with Z_{os} to get Z_{sn} .
7. Calculate the length of the stub using one of the following two methods.
 - a) If you need a short circuited stub, distance (l) is measured from the short circuit point (Z_{sc}) towards generator to Z_{sn} .
 - b) If you need a open circuited stub, distance (l) is measured from the open circuit point (Z_{oc}) towards generator to Z_{sn} .

1) Design a series stub with different impedances
The Complete Smith Chart

Black Magic Design

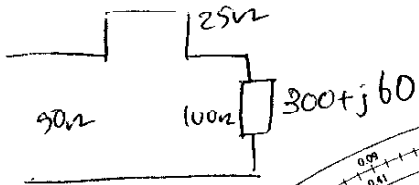

① Normalise Z_L w.r.t Z_{02}
 and plot Z_{LN}

$$\frac{300 + j60}{100} = 3 + j0.6$$

② Get new match

$$\frac{Z_A}{Z_{02}} = \frac{1}{2}$$

③ Rotate Z_L towards generator to match

$$d = 0.366\lambda$$

④ Renormalise

$$Z_{AN}$$

$$Z_A = (0.5 + j0.65)$$

$$\times 100$$



$$Z_A = 50 + j65$$

$$Z_{stub} = -j65$$

6) Normalise Z_{stub}


$$Z_{stub} = \frac{-j65}{25} = -j2.6$$

7) Calculate length

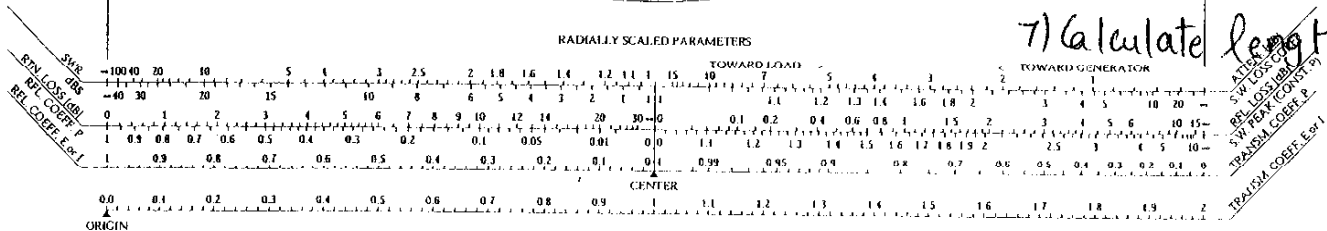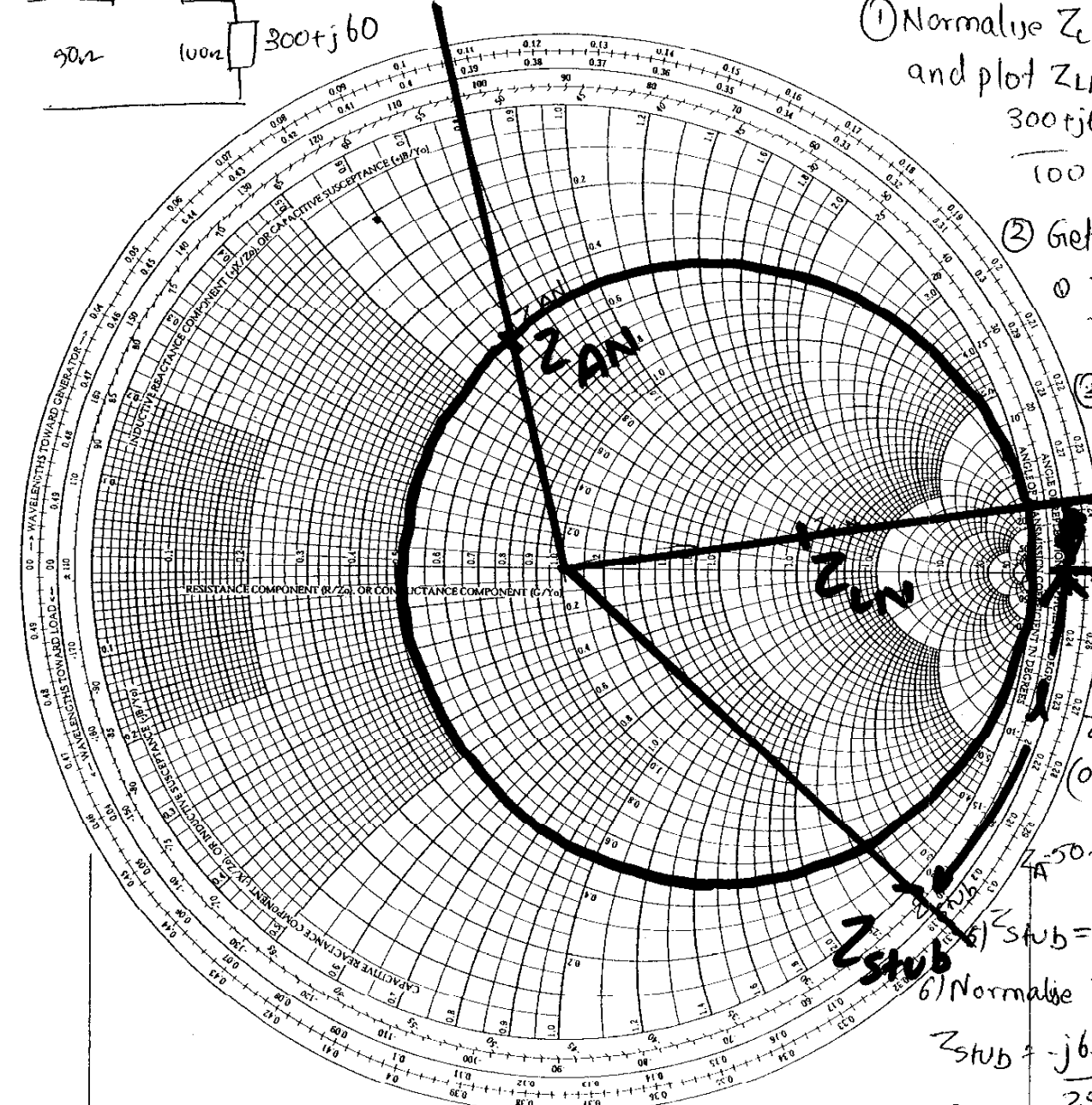

$$l = 0.0587\lambda$$

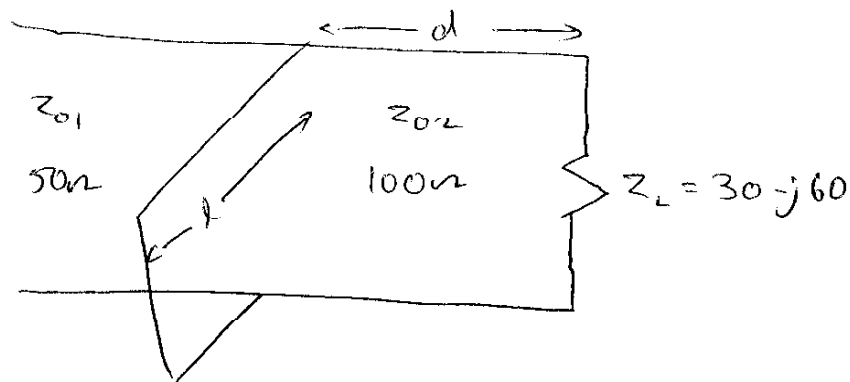Type 4 Shunt stub with different line impedances





1. Normalise Z_L with respect to Z_{02} and plot Z_{LN}
2. Reflect it through the origin to find Y_{LN}
3. Get the new matching circle Y_A/Y_{02}
4. Rotate Y_{LN} towards the generator to the matching circle. This point is Y_{AN} .
Calculate the distance (d) of stub from load
5. Renormalize Y_{AN} to get Y_A ($Y_A = Y_{AN} Y_{02}$).
6. $Y_{\text{stub}} = -Y_A$
7. Normalize Y_{stub} with Y_{0s} to get Y_{sn} .
8. Calculate the length of the stub using one of the following two methods.
 - a) If you need a short circuited stub, distance (l) is measured from the short circuit point (Y_{sc} not Z_{sc}) towards generator to Y_{sn} .
 - b) If you need an open circuited stub, distance (l) is measured from the open circuit point (Y_{oc} not Z_{oc}) towards generator to Y_{sn} .

2) Design a shunt stub for a line with different impedances

The Complete Smith Chart


Black Magic Design

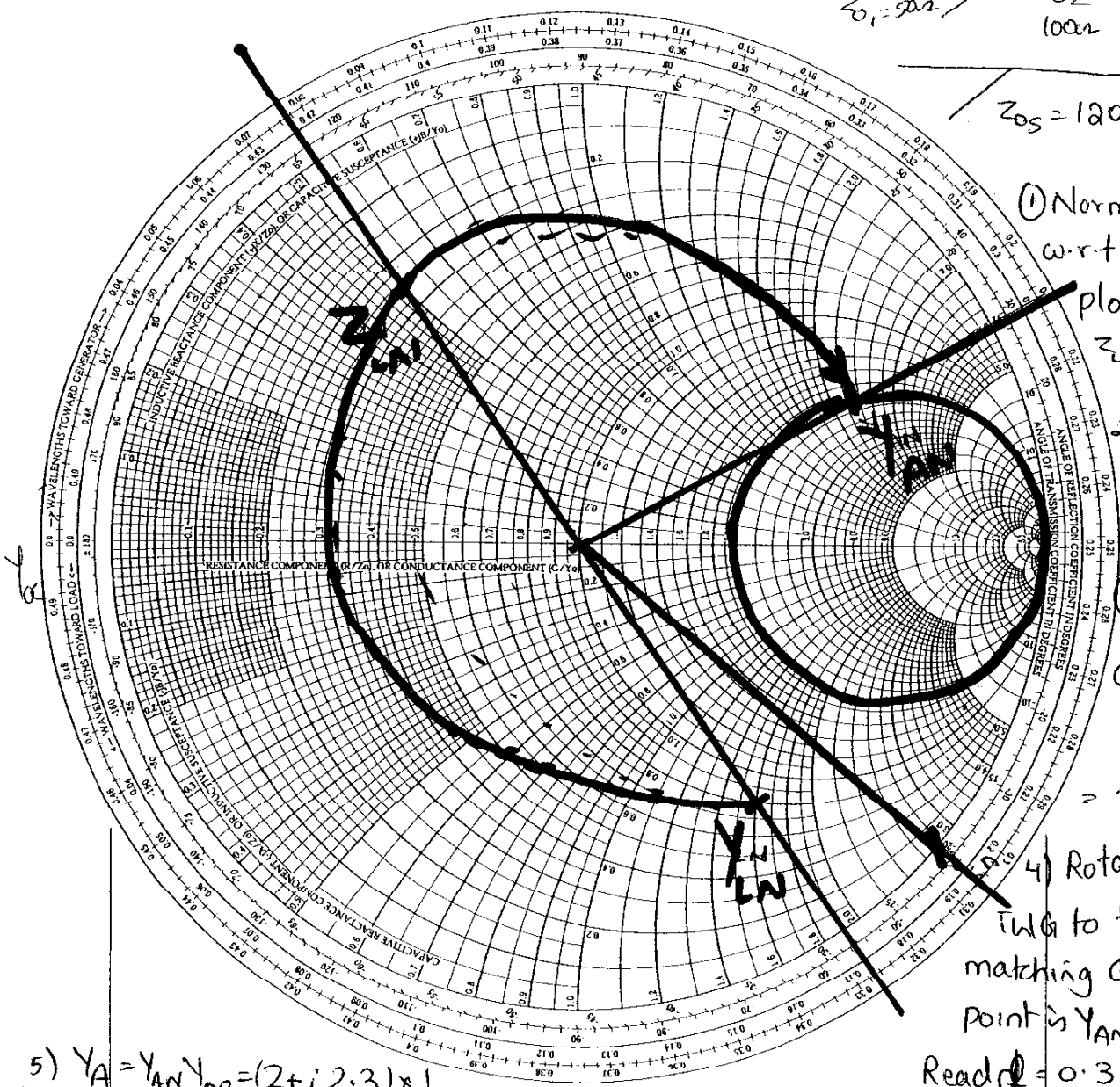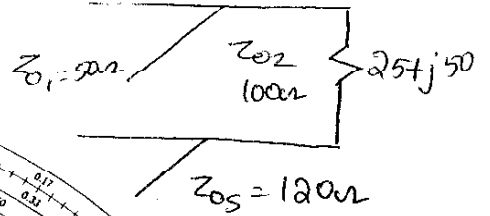

- 1) Normalise Z_L w.r.t Z_0 & plot $Z_{LN} = 0.25 + j0.5$
- 2) Convert to admittance Y_{LN}
- 3) Get the new matching $\frac{Y_A}{Y_0}$ = 2
- 4) Rotate Y_{LN} to the matching \odot This point is Y_{AN}

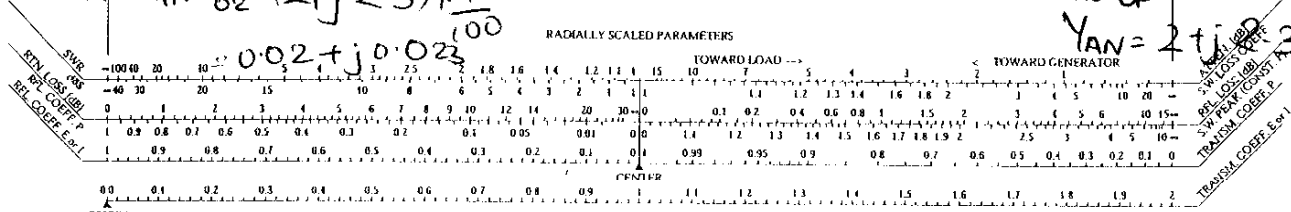
5) $Y_A = Y_{AN} Y_{02} = (2 + j2.3) \times \frac{1}{100}$
 $= 0.02 + j0.023$

Read $\Gamma = 0.382 \angle \theta$
 $Y_{AN} = 2 + j2.3$



6) $Y_S = -j0.023 \text{ u}$ $\eta_{sc} = 0.056 \text{ A (sc)}$
 $Y_{SN} = \frac{Y_S}{Y_0} = \frac{-j0.023}{\frac{1}{120}} = -j2.76$ $\eta_{oc} = 0.306 \text{ A (oc)}$

Cook Book For Double Stub Matching

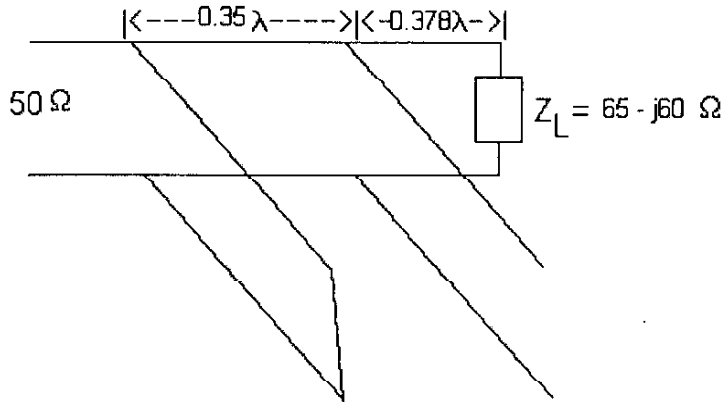

1. Plot $Z_{LN} = 65-j60/50 = 1.3-j1.2$ ($Z_{LN} = Z_L/Z_o$, normalized)
2. Reflect it through the origin to find Y_{LN} (point A)
3. Rotate distance 'd' towards the generator(TWG) on constant $|\Gamma|$ circle to point B
($d=0.378 \lambda$)
4. Draw the matching circle by rotating 0.35λ towards the load.
5. Move B along constant conductance circle towards the generator until it intersects the rotated matching circle. Name this point C. (Read Y_{CN})
6. Rotate 0.35λ towards the generator along the constant $|\Gamma|$ circle . Mark point D
7. Match the stub to 50 ohm line ($Y_{NF} = -Y_{ND}$). Plot point F
8. Measure length from short circuit point. This is l_2
9. Take imaginary part of point C and point B and calculate

$$g_h = g_c - g_b$$

10. Plot H

11. Calculate l_1

① $Z_L = (65 - j60)$

$Z_0 = 50\Omega$

$d = 0.378\lambda$

$d_1 = 0.357\lambda$

Stub ① o.c.

Stub ② s.c.

The Complete Smith Chart

Black Magic Design

① $Z_{LN} = \frac{65 - j60}{50} = 1.3 - j1.2$

② Reflect it through origin to find Y_{LN}


③ Rotate 0.378λ toward the generator on constant $|r|$ to get to point B

④ Move B along constant $|c|$ towards generator until it intersects the rotated matching \odot

⑤ Draw matching \odot by rotating 0.357λ

⑥ Rotate 0.357λ towards the generator along $|r|$ to \odot & mark point D

⑦ Match stub to 50Ω so we get

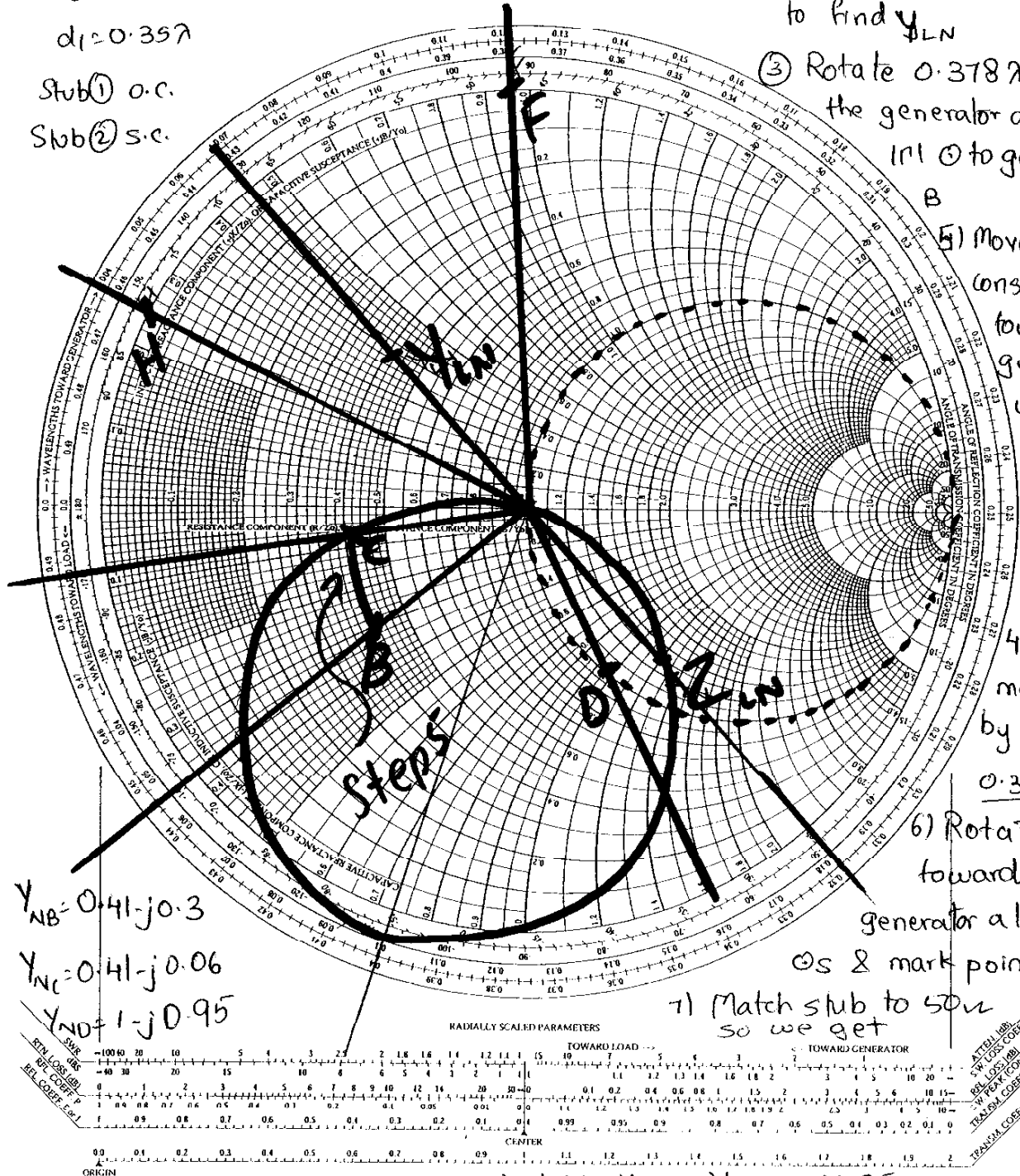


$Y_{NB} = 0.41 - j0.3$

$Y_{NC} = 0.41 - j0.06$

$Y_{ND} = 1 - j0.95$

RADIALLY SCALED PARAMETERS

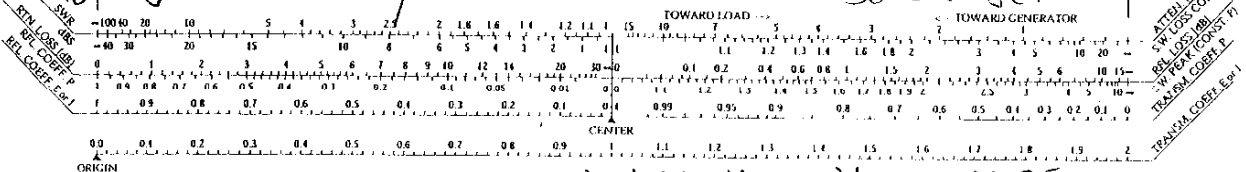

⑧ Measure length from ~~generator~~ point

$l_2 = 0.371\lambda$

short ckt $Y_{NF} = -Y_{ND} = +j0.95$

⑨ $g_H = g_c - g_b$
 $g_H = -j0.06 + j0.95 = j0.89$
 $b_H = j0.24$

Plot H $j0.24$

$l_1 = 0.038\lambda$

3) Design double stub tuner


$$Y_{LN} = 0.4 + j1.2$$

one stub is at load

& separation between the stubs is 0.365λ

The Complete Smith Chart

Black Magic Design

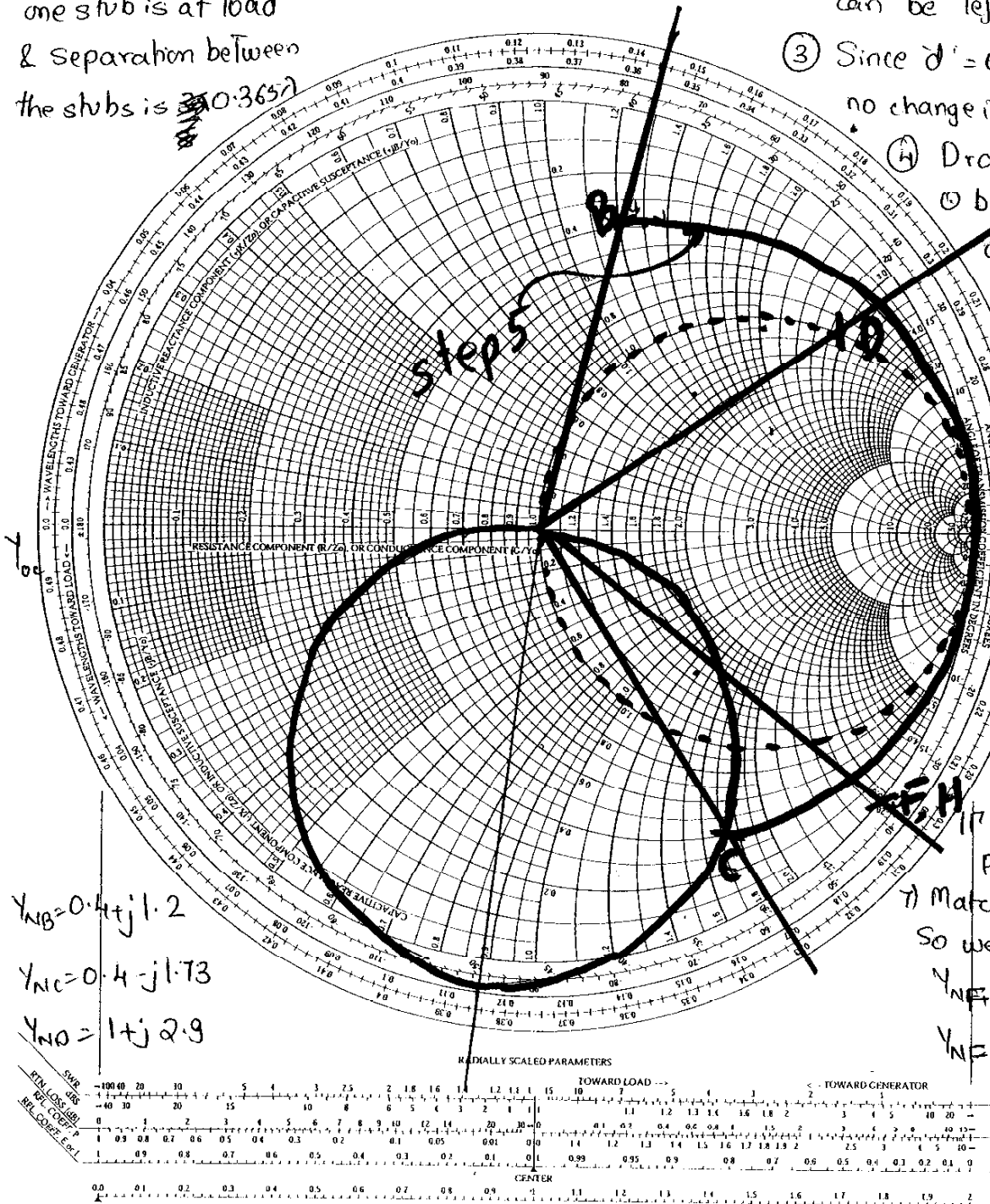

① Since we have been given Y_{LN} first 2 steps can be left off

② Since $d' = 0$ there is no change in Y_{LN} & B

③ Draw matching \odot by rotating 0.365λ

5) Move B along constant conductance \odot towards generator until it intersects the rotated matching \odot

6) Rotate 0.365λ towards the generator along \odot mark point D

7) Match stub to SWR so we get

$$Y_{NE} = -Y_{ND}$$

$$Y_{NE} = -j2.93$$

$$Y_{NB} = 0.4 + j1.2$$

$$Y_{NC} = 0.4 - j1.73$$

$$Y_{ND} = 1 + j2.9$$

8) Measure length from SC point $l_2 = 0.08\lambda$

$$g_1 = g_c - g_b = -j2.93$$

$$l_1 = 0.08\lambda$$

Plot \odot $-j2.93$

