

ECE 6130 – S-Parameters

Text Section 4.3

Describe and Compute S-Parameters
Examples: Chapter 4, Problems 10,11

S-Parameters:

Recall –

Scattering Matrix (S-parameters)


$$\begin{bmatrix} V_1^- \\ V_2^- \\ \vdots \\ V_N^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & \cdots & S_{1N} \\ S_{21} & \ddots & & \\ \vdots & & \ddots & \\ S_{N1} & S_{N2} & \cdots & S_{NN} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \\ \vdots \\ V_N^+ \end{bmatrix}$$

Where

$$S_{ij} = V_i^- / V_j^+ \text{ when } V_k^+ = 0 \text{ for } k \neq j$$

- 1) Terminate all ports except j with matched load.
- 2) Drive port j with V_j^+
- 3) Measure reflected voltage V_i^- on port i.

EXAMPLE: 3dB attenuator

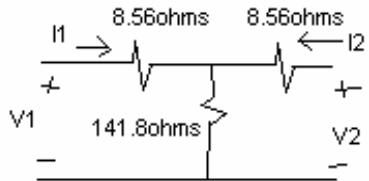

Find S_{11} :

$$Z_2 = 50 \text{ ohms}; Z_{in}(\text{port 1}) = 8.56 + (141.8 \parallel (8.56 + 50)) = 50 \text{ ohms}$$

$$V1^- = 0 \text{ (no reflection)}$$

$$S_{11} = V1^- / V1^+ = 0$$

Find S_{22} :

Circuit is symmetric.

$$S_{22} = S_{11}$$

Find S_{12} :

$$S_{12} = V2^- / V1^+ \text{ when port 2 is terminated}$$

Since $S_{11} = 0$, we know that $V_{1-} = 0$ when port 2 is terminated, and $V_{2+} = 0$ (by definition)

Then $V_{2-} = V_2 = V_{\text{middle}} (8.56 / (8.56 + 50))$

$$V_{\text{middle}} = V_1 (8.56 \parallel 141.8) / (8.56 + 8.56 \parallel 141.8)$$

Return Loss

$$RL = -20 \log(S_{ii}) \text{ dB}$$

Insertion Loss

$$TL = -20 \log(S_{ij}) \text{ dB}$$

EXAMPLES