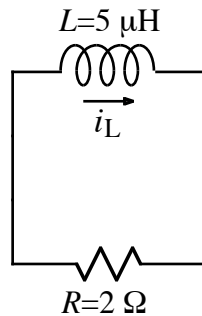


Ex: Find the current, i_L , through the inductor in the circuit below for $t > 0$ if $i_L(t = 0) = 5$ A.



SOL'N: The same current flows in both the L and R, and the voltages are the same except for a minus sign:

$$v_L = L \frac{di_L}{dt} = -i_L R = -v_R$$

The inductor current, i_L , that solves this equation is an exponential:

$$i_L(t) = k e^{-t/(L/R)} = k e^{-t/2.5 \mu\text{s}}$$

To satisfy the initial condition as given for $t = 0$, the value of the constant k must be 5 A, since the exponential has a value of unity: $e^0 = 1$.

$$i_L(t > 0) = 5 \text{ A } e^{-t/2.5 \mu\text{s}}$$

NOTE: We could actually use this solution for $t = 0$ as well, since i_L doesn't change instantly at time zero.