

Ex:



- a) Find an expression for  $i_{L}(t)$  for  $t \ge 0$ . Note: Assume the initial current in the *L* is created by circuitry not shown in the diagram.
- b) Find the energy stored in the inductor at time t = 10 ms.
- **SOL'N:** a) The following general form of solution applies to any RL circuit with a single inductor:

$$i_{L}(t \ge 0) = i_{L}(t \to \infty) + [i_{L}(t = 0^{+}) - i_{L}(t \to \infty)]e^{-t/(L/R_{\text{Th}})}$$

The Thevenin resistance,  $R_{\text{Th}}$ , is for the circuit after t = 0 (with the *L* removed) as seen from the terminals where the *L* is connected. In the present case, we have  $R_{\text{Th}} = 300 \text{ k}\Omega$ .

 $L/R_{\rm Th} = 1 \,\mu {\rm H}/300 \,{\rm k}\Omega = 3.33 \,{\rm ps}$ 

The value of  $i_L(t=0)$  is given in the problem as 12 A, (created by circuitry not shown).

As time approaches infinity, the *L* current will converge to its final value, and the voltage across the *L* will cease to change. Thus,  $di_L/dt = 0$  and  $v_L = 0$ , meaning the *L* will act like a wire. It follows that the current through the *L* will equal the current through the *R*, which will equal 4 V/300 k $\Omega = 13.3 \mu A$ .

$$i_L(t \rightarrow \infty) = 13.3 \,\mu\text{A}$$

Substituting values, we have the following result:

$$i_L(t \ge 0) = 13.3 \ \mu\text{A} + [12 - 13.3 \ \mu\text{A}]e^{-t/3.33 \text{ps}}$$
  
= 13.3 \ \mu\text{A} - 1.3 \ \mu\text{A}e^{-t/3.33 \text{ps}}

b) The energy in an inductor is given by the following formula:

$$w_L = \frac{1}{2}Li_L^2$$

We use the solution to (a) to evaluate  $i_L(t)$  at t = 10 ms.

$$i_L(t = 10 \text{ms}) = 13.3 \ \mu\text{AV} - 1.3 \ \mu\text{A} \cdot e^{-10 \text{ms}/3.33 \text{ps}} \approx 13.3 \ \mu\text{A}$$

**NOTE:** 10 ms is 3 billion time constants, (where the time constant is  $\tau = 3.33$  ps), after time zero. By that time, the inductor current is extremely close to its final value. That is to say  $e^{-3,000,000,000}$  is extremely close to zero.

Using the current at t = 10 ms, we evaluate the energy on the inductor.

$$w_L = \frac{1}{2} 1 \mu \text{H} \cdot (13.3 \mu \text{A})^2 = 88.9 \text{ fJ}$$