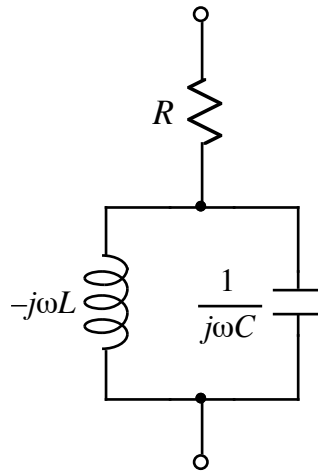


**Ex:** Derive a symbolic expression for the impedance of an  $R$  in series with an  $L$  and  $C$  in parallel at frequency  $\omega$ . Express the answer as a ratio of polynomials with complex coefficients.

**SOL'N:** The circuit is shown below.



When working with parallel impedances, it is typically easier to use the summation of conductance form of parallel impedance.

$$z_{||} = \frac{1}{\frac{1}{j\omega L} + \frac{1}{\frac{1}{j\omega C}}} = \frac{1}{\frac{1}{j\omega L} + j\omega C} = \frac{1}{-j\left(\frac{1}{\omega L} - \omega C\right)} = j \frac{1}{\left(\frac{1}{\omega L} - \omega C\right)}$$

or

$$z_{||} = j \frac{\omega L}{(1 - \omega^2 LC)}$$

We add  $R$  to the above value to obtain the total impedance:

$$z = R + j \frac{\omega L}{(1 - \omega^2 LC)}$$