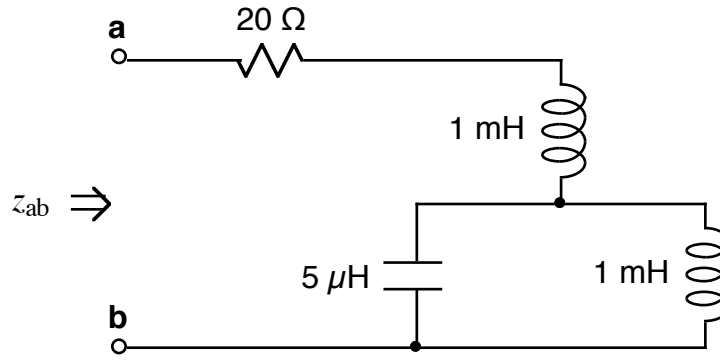


Ex:



Find a frequency, ω , that causes z_{ab} to be real, (i.e., imaginary part equals zero).

Sol'n: $z_{ab} = 20 \Omega + z_{L1} + z_C \parallel z_{L2}$

For z_{ab} to be real, we must have

$$z_{L1} + z_C \parallel z_{L2} = \text{real}$$

One simple sol'n is to let $\omega = 0$ so both L's act like wires and C acts like open circuit.

Other potential sol'ns are $\omega = \infty$, (so L's act like opens, resulting in $z_{ab} = \infty$), and $\omega = \text{frequency where } z_C = -z_{L2}$, (so C and L in parallel have equal but opposite impedances).

The latter case, where $z_C = -z_L$ gives

the interesting result that $z_C \parallel z_L = \frac{L/C}{0} = \infty$

This means $z_{ab} = \infty \Omega$. In this case, (unlike $\omega \rightarrow \infty$), $z_{ab} \rightarrow \infty$ along real axis as $z_C \parallel z_L \rightarrow \infty$.

Another sol'n is that $z_c \parallel z_L$ has a value is minus z_L of the top inductor.

In that case, $z_L + z_c \parallel z_L = 0$ and $z_{ab} = 0 = \text{wire}$.

$$z_L = j\omega L$$

$$\begin{aligned} z_c \parallel z_L &= \frac{-j}{\omega C} \parallel j\omega L = \frac{-j \cdot j\omega L}{\frac{-j}{\omega C} + j\omega L} = \frac{L/C}{j(\omega L - \frac{1}{\omega C})} \\ &= -j \frac{L/C}{\omega L - \frac{1}{\omega C}} \end{aligned}$$

$$\text{Thus, we want } j\omega L - \frac{jL/C}{\omega L - \frac{1}{\omega C}} = 0$$

$$\text{or } \omega L = \frac{L/C}{\omega L - \frac{1}{\omega C}}$$

$$\text{or } \omega L \left(\omega L - \frac{1}{\omega C} \right) = L/C$$

$$\text{or } \omega^2 L^2 - \frac{L}{C} = \frac{L}{C}$$

$$\text{or } \omega^2 L^2 = \frac{2L}{C} \quad \text{or } \omega^2 = \frac{2}{LC}$$

$$\text{or } \omega = \sqrt{\frac{2}{LC}} \quad \text{or } \omega = \sqrt{\frac{2}{5\mu\text{F} \cdot 1\text{mH}}}$$

$$\text{or } \omega = \sqrt{\frac{2 \times 10^6}{5}} \text{ r/s} = \sqrt{400000} \text{ r/s}$$

$$\text{or } \omega = 20\text{k r/s}$$