
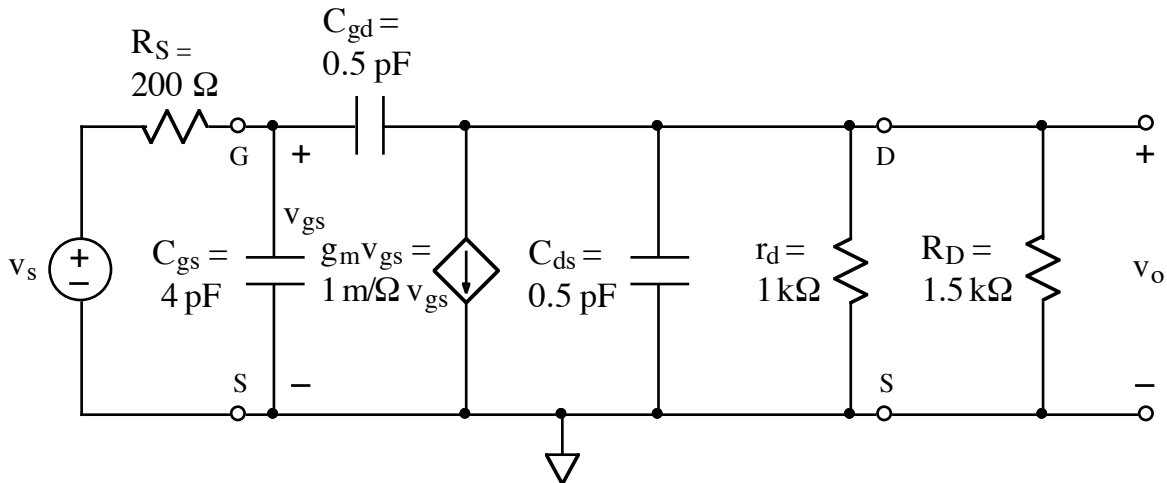


Ex:

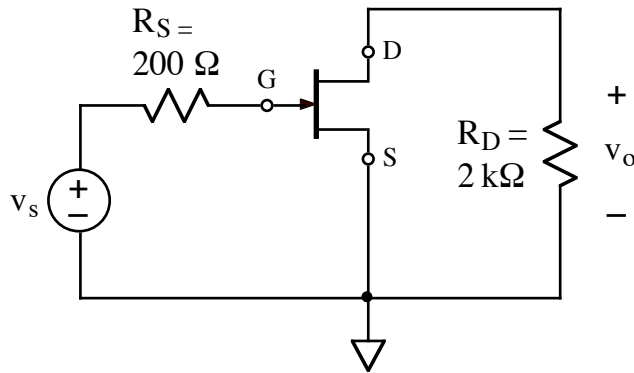

$$v_s(t) = 2 \cos(10kt) \text{ V}$$

The above circuit diagrams show a common-source JFET amplifier and its high-frequency equivalent circuit. Find $v_o(t)$.

Sol'n: In this practical circuit, we have circuit values that allow us to make simplifying approximations.

We first calculate impedance values.

$$\omega = 10k \text{ r/s} \quad \text{from} \quad v_s(t) = 2 \cos(10kt) \text{ V}$$


$$z_{C_{gs}} = \frac{-j}{\omega C_{gs}} = \frac{-j \Omega}{10k \cdot 4p} = -j 25M \Omega$$

$$z_{C_{gd}} = \frac{-j}{\omega C_{gd}} = \frac{-j}{10k \frac{1}{2} p} = -j 200M \Omega$$

$$z_{C_{ds}} = \frac{-j}{\omega C_{ds}} = \frac{-j}{10k \frac{1}{2} p} = -j 200M \Omega$$

The phasor for $v_s(t)$ is $V_s = 2 \angle 0^\circ$ V.

Frequency domain (or s -domain) model:

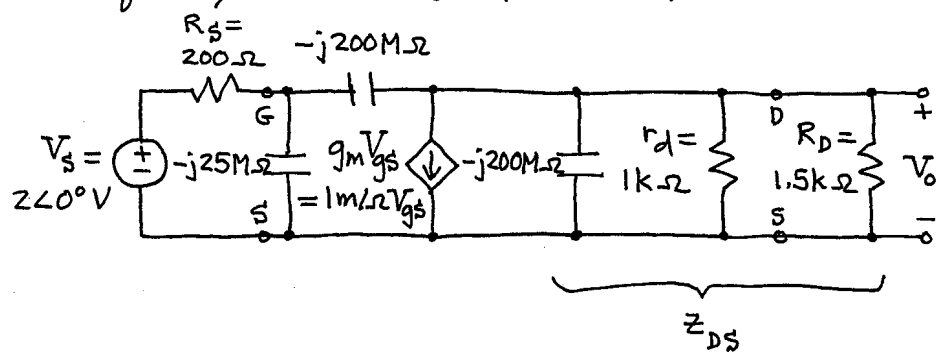

$$z_{DS} = -j 200M \parallel 1k \Omega \parallel 1.5k \Omega$$

Starting with $1k \Omega \parallel 1.5k \Omega$ we have

$$1k \Omega \parallel 1.5k \Omega = 500 \Omega \cdot \frac{2}{3} = 500 \cdot \frac{6}{5}$$

$$= 600 \Omega$$

$$\text{Thus, } z_{DS} = -j 200M \parallel 600 \Omega = \frac{1}{\frac{1}{600} - \frac{1}{j 200M}}$$

Using $-\frac{1}{j} = j$ and rationalizing gives

$$\begin{aligned}
 z_{DS} &= \frac{1}{\frac{1}{600} + \frac{j}{200M}} \frac{1}{\frac{1}{600} - \frac{j}{200M}} \Omega \\
 &= \frac{1}{\frac{1}{600} - \frac{j}{200M}} \frac{1}{\left(\frac{1}{600}\right)^2 + \left(\frac{1}{200M}\right)^2} \Omega \\
 &\approx \frac{1}{\frac{1}{600} - \frac{j}{200M}} \frac{1}{\left(\frac{1}{600}\right)^2} \Omega \quad \text{Since } \frac{1}{200M} \ll \frac{1}{600}
 \end{aligned}$$


$$z_{DS} \approx \frac{1}{\frac{1}{600}} \Omega = 600 \Omega$$

In retrospect, we could have made the approximation that $-j200M \parallel 600 \Omega \approx 600 \Omega$.


We may make this approximation despite the j in one of the quantities. In general, we may make the following approximations of complex values:

$$a + jb \approx a \quad \text{when } |b| \ll |a|$$


$$a + jb \approx jb \quad \text{when } |a| \ll |b|$$

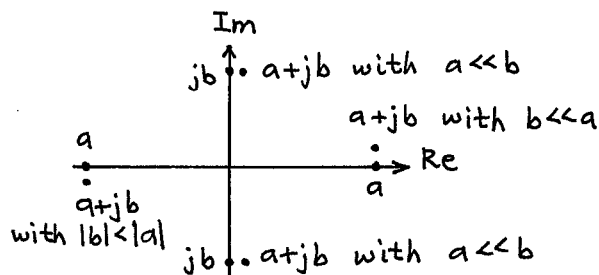

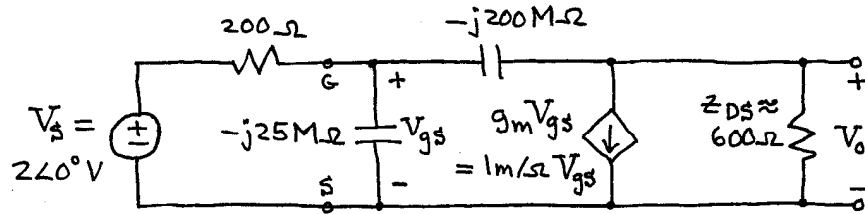With our z_{DS} value, we have a simplified model:



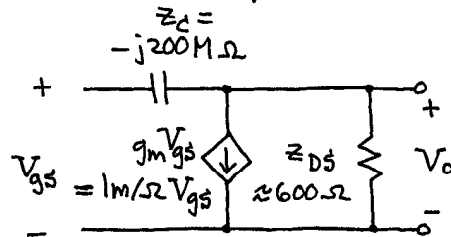We now analyze the dependent source so we can replace it with an impedance, z_{eg} .



$$z_{eg} = \frac{V_o}{g_m V_{gs}} \quad \text{using Ohm's law to write } z_{eg} = V/I$$

Now we find a way to write V_o in terms of V_{gs} . We use a V -divider:

$$V_o = V_{gs} \frac{z_{eg} \parallel z_{DS}}{z_{eg} \parallel z_{DS} + z_c}$$

Substituting for V_o in our z_{eg} eq'n, we have

$$z_{eg} = \frac{V_{gs} \frac{z_{eg} \parallel z_{DS}}{z_{eg} \parallel z_{DS} + z_c}}{V_{gs} \cdot g_m}$$

$$z_{eg} = \frac{1}{g_m} \frac{\frac{z_{eg} z_{DS}}{z_{eg} + z_{DS}}}{\frac{z_{eg} z_{DS}}{z_{eg} + z_{DS}} + z_c}$$

$$z_{eg} = \frac{1}{g_m} \frac{z_{eg} z_{DS}}{z_{eg} z_{DS} + z_c (z_{eg} + z_{DS})}$$

Dividing top and bottom by z_{eg} gives the following:

$$z_{eg} = \frac{1}{g_m} \frac{z_{DS}}{z_{DS} + z_c + \frac{z_c z_{DS}}{z_{eg}}}$$

$$z_{eg} \left(z_{DS} + z_c + \frac{z_c z_{DS}}{z_{eg}} \right) = \frac{1}{g_m} z_{DS}$$

$$z_{eg} (z_{DS} + z_c) + z_c z_{DS} = \frac{1}{g_m} z_{DS}$$

$$z_{eg} \frac{(z_{DS} + z_c)}{z_{DS}} = \frac{1}{g_m} \frac{z_{DS} - z_c z_{DS}}{z_{DS}}$$

$$z_{eg} = \frac{1}{g_m} - z_c = \frac{1 \Omega}{1 \text{ m}} - -j 200 \text{ M} \Omega$$

$$\frac{1 + \frac{z_c}{z_{DS}}}{1 + \frac{-j 200 \text{ M} \Omega}{600 \Omega}}$$

$$z_{eg} = \frac{1 \text{ k} + j 200 \text{ M} \Omega}{1 - j \frac{1}{3} \text{ M}}$$

The imaginary parts of the numerator and denominator are much larger than the real parts. Thus, we ignore the real parts.

$$z_{eg} \approx j 200 \text{ M} \Omega / -j \frac{1}{3} \text{ M} \approx -600 \Omega$$

Now we have a problem: $z_{eg} \parallel z_{DS} = -\frac{600^2}{0} \Omega$.

That means $z_{eg} \parallel z_{DS} = \infty \Omega$.

It is a good idea to try a more exact calculation to be sure that $z_{eg} \parallel z_{DS}$ is much larger than $z_c = -j200 M\Omega$.

We use conductance to simplify calculations.

$$\frac{1}{z_{eg} \parallel z_{DS}} = \frac{1}{z_{eg}} + \frac{1}{z_{DS}} = \frac{1 + \frac{z_c}{z_{DS}}}{\frac{1}{g_m} - z_c} + \frac{1}{z_{DS}}$$

$$= \frac{1}{z_{DS}} \left(\frac{z_{DS} + z_c}{\frac{1}{g_m} - z_c} + 1 \right)$$

$$= \frac{1}{z_{DS}} \left(\frac{z_{DS} + z_c}{\frac{1}{g_m} - z_c} + \frac{\frac{1}{g_m} - z_c}{\frac{1}{g_m} - z_c} \right)$$

$$= \frac{1}{z_{DS}} \left(\frac{z_{DS} + \frac{1}{g_m}}{\frac{1}{g_m} - z_c} \right)$$

$$= \frac{g_m + \frac{1}{z_{DS}}}{1 - g_m z_c}$$

$$= \frac{1 m + \frac{1}{600}}{1 - 1 m (-j200 M)} / \Omega$$


$$z_{eg} \parallel z_{DS} = \frac{1 + j200 K}{\frac{1}{1K} + \frac{1}{600}} \Omega$$

$$z_{eg} \parallel z_{DS} = \frac{1 + j200k \Omega}{\frac{3+5}{3k}} = \frac{3k}{8} (1 + j200k) \Omega$$

$$= \frac{3k}{8} + j75M \Omega$$

We see that the value is smaller than $z_c = -j200M \Omega$.

Our new, simplified model:

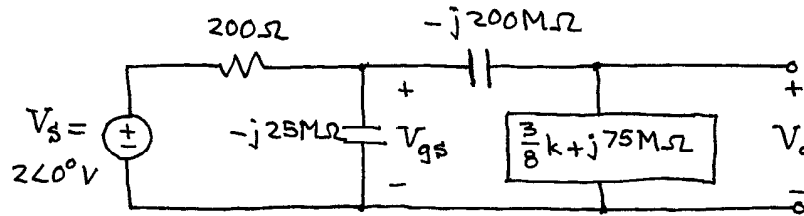

We use V-dividers to find V_o .

$$V_{gs} = V_s \cdot \frac{-j25M\Omega \parallel (-j200M + \overset{\text{small}}{\frac{3}{8}k + j75M\Omega})}{200 + -j25M\Omega \parallel (-j200M + \overset{\text{small}}{\frac{3}{8}k + j75M\Omega})}$$

$$V_{gs} \approx \frac{V_s \cdot (-j25M\Omega \parallel -j125M\Omega)}{200 - j25M\Omega \parallel -j125M\Omega}$$

$$\text{where } -j25M\Omega \parallel -j125M\Omega = -j25M\Omega \cdot \frac{1}{5}$$

$$= -j25M\Omega \cdot \frac{5}{6}$$

$$= -j \frac{125}{6} M\Omega$$

$$V_{gs} = \frac{V_s \cdot \left(-j \frac{125}{6} M\Omega\right)}{\overset{\text{small}}{200} - j \frac{125}{6} M\Omega} \approx V_s$$

$$V_o = V_{gs} \frac{\frac{3}{8} k + j 75 M\Omega}{\frac{3}{8} k + j 75 M\Omega - j 200 M\Omega}$$


$$V_o \approx V_{gs} \frac{j 75 M\Omega}{-j 125 M\Omega} = V_{gs} \left(-\frac{3}{5} \right)$$

$$V_o \approx 2 \angle 0^\circ V \left(-\frac{3}{5} \right) = -\frac{6}{5} \angle 0^\circ V = \frac{6}{5} \angle 180^\circ V$$

Note: a minus sign is the same as 180° of phase shift.

$$v_o(t) = \frac{6}{5} \cos(10kt + 180^\circ) V$$

Alternate approach to solution below.

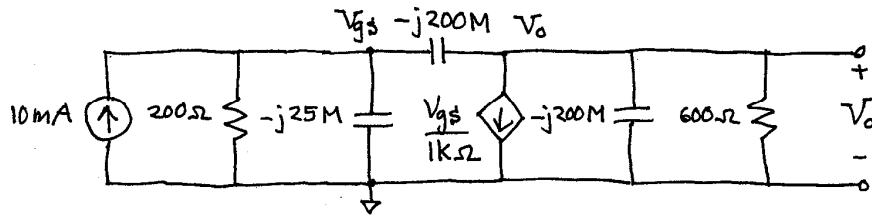

Using exact Node-Voltage method:

$$1) \quad 0A = -10mA + V_{gs} \left(\frac{1}{200\Omega} + \frac{1}{-j25M\Omega} + \frac{1}{-j200M\Omega} \right) - \frac{V_o}{-j200M\Omega}$$

$$2) \quad 0A = V_{gs} \left(\frac{-1}{-j200M\Omega} + \frac{1}{1k\Omega} \right) + V_o \left(\frac{1}{-j200M\Omega} + \frac{1}{-j200M\Omega} + \frac{1}{600\Omega} \right)$$

Solve eq'n (2) for V_{gs} and substitute in eq'n (1).

$$2') \quad V_{gs} = -V_o \frac{\left(\frac{1}{-j200M\Omega} + \frac{1}{600\Omega} \right)}{\frac{1}{j200M\Omega} + \frac{1}{1k\Omega}} = V_o \frac{\left(\frac{-j}{100M\Omega} - \frac{1}{600\Omega} \right)}{\frac{-j}{200M\Omega} + \frac{1}{1k\Omega}}$$

Multiply eq'n (1) by $200M\Omega$ to clear denominator:

$$1') \quad 10mA \cdot 200M\Omega = V_{gs} (1M + j8 + j1) - V_o j$$

Multiply eq'n (2') by $\frac{200M\Omega}{200M\Omega}$:

$$2'') \quad V_{gs} = V_o \frac{\left(-j2 - \frac{1}{3}M \right)}{\left(-j + 200k \right)} = V_o \frac{\frac{1}{3}M + j2}{-200k + j}$$

$$1'') \quad 2MV = V_{gs} (1M + j9) - V_o j = V_o \left[\frac{\left(\frac{1}{3}M + j2 \right) (1M + j9) - j}{-200k + j} \right]$$

$$1''') \quad V_o \approx \frac{2MV(-200k)}{\frac{1}{3}M \cdot 1M} = -1.2V \quad \text{Agrees with previous answer}$$