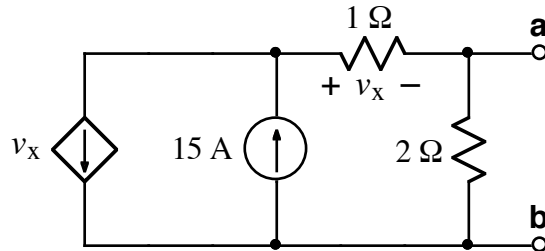



Ex:



- Find the Thevenin equivalent of the above circuit relative to terminals **a** and **b**.
- If we attach R_L to terminals **a** and **b**, find the value of R_L that will absorb maximum power.
- Calculate the value of that maximum power absorbed by R_L .

sol'n: a) $v_{Th} = v_{a,b}$ with nothing connected across a,b

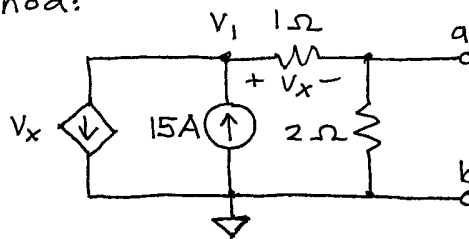One approach is to use the node-voltage method:



Using the voltage-divider formula, we relate v_x to v_1 :

$$v_x = v_1 \cdot \frac{1\Omega}{1\Omega + 2\Omega} = \frac{v_1}{3}$$

Node v_1 eq'n:

$$\frac{v_1}{3} - 15A + \frac{v_1}{1\Omega + 2\Omega} = 0A$$


$$\text{or } \frac{2V_1}{3\Omega} = 15A$$

$$\text{or } V_1 = \frac{3\Omega \cdot 15A}{2} = 22.5V$$


To find V_{Th} , we again use a voltage-divider formula:

$$V_{Th} = V_1 \cdot \frac{2\Omega}{1\Omega + 2\Omega} = 22.5V \cdot \frac{2}{3} = 15V$$

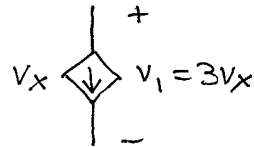Note: Another approach is to replace the dependent source with a resistor. To do so, we write the voltage across the dependent source in terms of dependent variable V_x . From an eq'n above, we have $V_1 = 3V_x$.


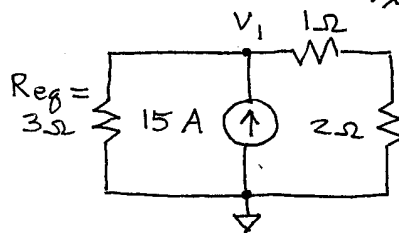
$$R_{eq} = \frac{V}{i} = \frac{3V_x}{V_x} = 3\Omega$$




$$V_1 = 15A \cdot 3\Omega \parallel 3\Omega = 22.5V$$

Note: R_{eq} changes with R across a,b.

One way to find R_{Th} is to use

$$R_{Th} = \frac{V_{Th}}{\bar{i}_{sc}}$$

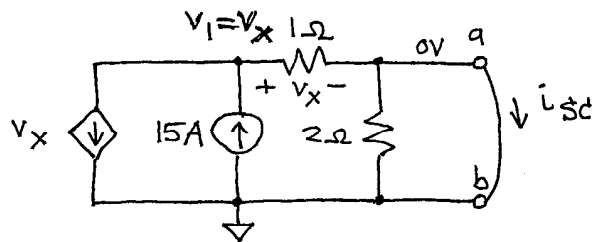where $\bar{i}_{sc} \equiv$ short circuit from **a** to **b**



We may ignore the 2Ω resistor that is shorted out.

Node v_1 eq'n: (Note that $v_x = v_1$.)

$$v_1 - 15A + \frac{v_1}{1\Omega} = 0A$$

or

$$\frac{2v_1}{1\Omega} = 15A$$

or

$$v_1 = 15A \cdot \frac{1\Omega}{2} = 7.5V$$

$$\text{Our current is } \bar{i}_{sc} = \frac{v_1}{1\Omega} = \frac{7.5V}{1\Omega} = 7.5A.$$

$$R_{Th} = \frac{V_{Th}}{\bar{i}_{sc}} = \frac{15V}{7.5A} = 2\Omega$$

Note: we could replace the dependent source with $R_{eq} = \frac{v}{i} = \frac{v_x}{v_x} = 1\Omega$ for \bar{i}_{sc} .

b) $R_L = R_{Th} = 2\Omega$ for max pwr xfer

c) $P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{15^2}{4 \cdot 2\Omega} = 28.125 \text{ W}$