
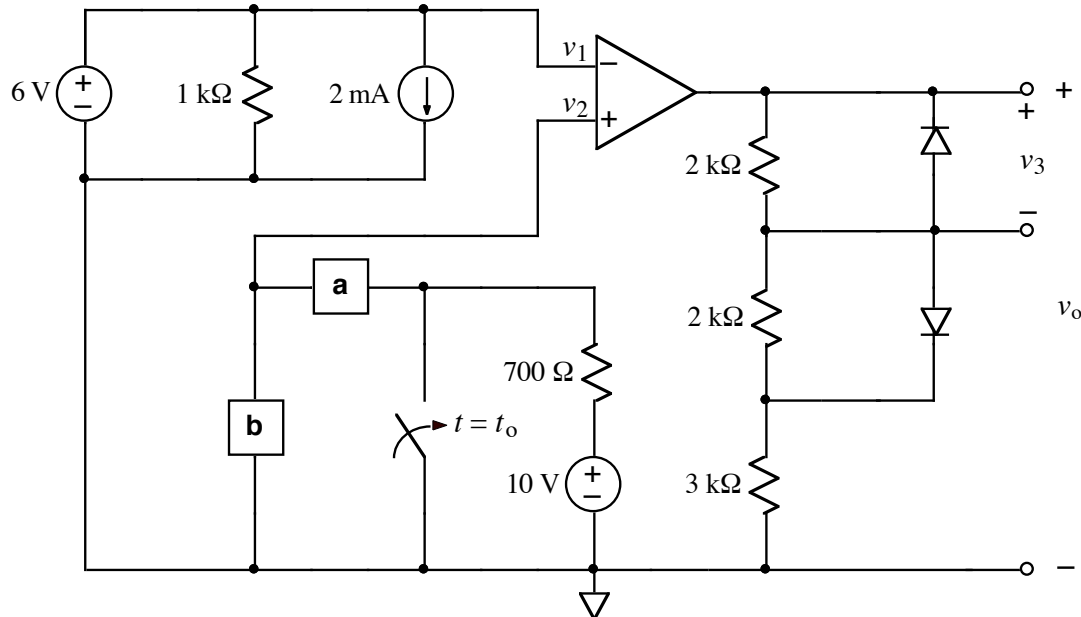


Ex:

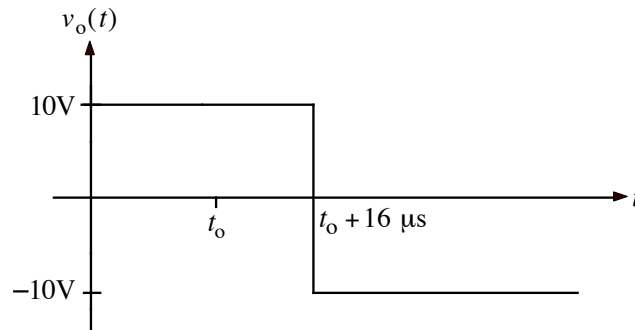

After being open for a long time, the switch closes at time $t = t_0$.

Rail voltages = ± 10 V



- Choose either an R or L to go in box **a** and either an R or L to go in box **b** to produce the $v_o(t)$ shown above. (You will need one R and one L . Use an R value of $1.3 \text{ k}\Omega$. Also, note that v_o stays low forever after $t_0 + 16 \mu\text{s}$.) Specify which element goes in each box and its value.
- Sketch $v_1(t)$, showing numerical values appropriately.
- Sketch $v_2(t)$, showing numerical values appropriately.
- Sketch $v_3(t)$. Show numerical values for $t < t_0$, for $t_0 < t < t_0 + 16 \mu\text{s}$, and for $t > t_0 + 16 \mu\text{s}$. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

sol'n: a) We first find v_1 , which is constant. The $1k\Omega$ resistor and $2mA$ source are across the $6V$ source. Because they are across the $6V$ source, they may be ignored. $v_1 = 6V$ regardless of what is across the $6V$ source.

$$v_1 = 6V$$


For boxes **a** and **b**, we observe that, if we had an L in **b**, that L will act like a wire at $t=0^-$. This would make $v_2(0^-) = 0V$. The op-amp acts like a comparator, with the output equal to $\pm 10V$ according to the sign of $v_2 - v_1$. For $v_2 = 0V$ and $v_1 = 6V$ we would have $v_2 - v_1 = 0 - 6V = -6V$ and $v_o = -10V$ at $t=0^-$. This differs from the plot of $v_o(t)$ given in the problem statement. Thus, **b** must contain an R rather than an L .

Because the output voltage, $v_o(t)$, changes $16\mu s$ after the switch moves, box **a** must contain an L to give the circuit a time-varying behavior.

$$a = L$$

$$b = R \approx 1.3k \text{ (from prob statement)}$$

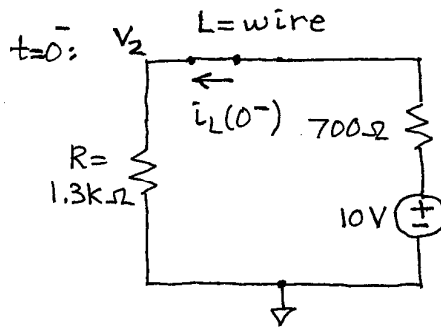At $t=0^-$, we have the following equivalent circuit:



$$i_L(0^-) = \frac{10V}{1.3k\Omega + 700\Omega}$$


$$i_L(0^-) = 5\text{mA}$$

This is a voltage divider.

$$V_2(0^-) = 10V \cdot \frac{1.3k\Omega}{1.3k\Omega + 700\Omega} = 6.5V$$

We note that $v_2(0^-) = 6.5 > v_1(0^-) = 6V$
 and $v_2 - v_1 = 6.5 - 6V = 0.5V > 0V$ so
 $v_0(0^-) = +10V$, as desired.

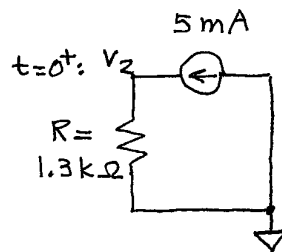At $t=0^+$, we have the following equivalent circuit:




$$V_2(0^+) = 5\text{mA} \cdot 1.3k\Omega$$

$$V_2(0^+) = 6.5V$$

At $t=0^+$, $v_2 - v_1 = 6.5V - 6V = 0.5V > 0V$
 so $v_0(0^+) = +10V$, as desired.

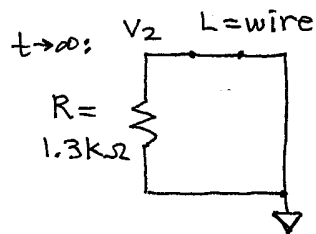As $t \rightarrow \infty$, we have the following equivalent circuit:



Since there is no power source,
 $v_2(t \rightarrow \infty) = 0V$

The time constant of the circuit is

$$\tau = \frac{L}{R_{Th}} = \frac{L}{1.3k\Omega}$$

Using the general form of solution for RL circuits, we write an expression for $v_2(t > 0)$:

$$v_2(t > 0) = v_2(t \rightarrow \infty) + [v_2(0^+) - v_2(t \rightarrow \infty)] e^{-t/\tau}$$

$$\text{or } v_2(t > 0) = 0V + [6.5V - 0V] e^{-t/\tau}$$

$$\text{or } v_2(t > 0) = 6.5V e^{-t/\tau}$$

The op-amp output switches from high to low when $v_2(t) = v_1 = 6V$, which must occur at $t = t_0 + 16\mu s$.

Setting $t_0 = 0$, we solve for L in $v_1 = v_2$ at $t = 16\mu s$.

$$6V = 6.5V e^{-16\mu s/\tau}$$


$$\text{or } \ln(6/6.5) = -16\mu s/\tau$$

$$\text{or } \tau = \frac{-16 \mu\text{s}}{\ln(6/6.5)} \approx 200 \mu\text{s}$$


$$L = \tau \cdot R_{\text{Th}} = 200 \mu\text{s} \cdot 1.3 \text{ k}\Omega = 260 \text{ mH}$$

$R = 1.3 \text{ k}\Omega$ $L = 260 \text{ mH}$

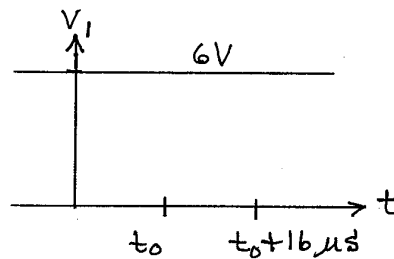
b) From above, $v_1(t) = 6V$ at all times



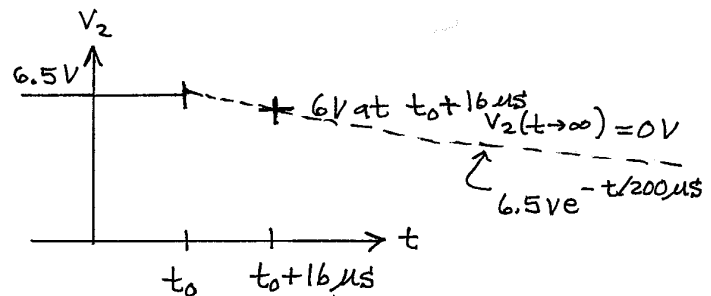c) From above, $v_2(0^-) = 6.5V$ and $v_2(t > 0) = 6.5 e^{-t/200 \mu\text{s}}$ V
 Also, $v_2(t = 16 \mu\text{s}) = v_1 = 6V$



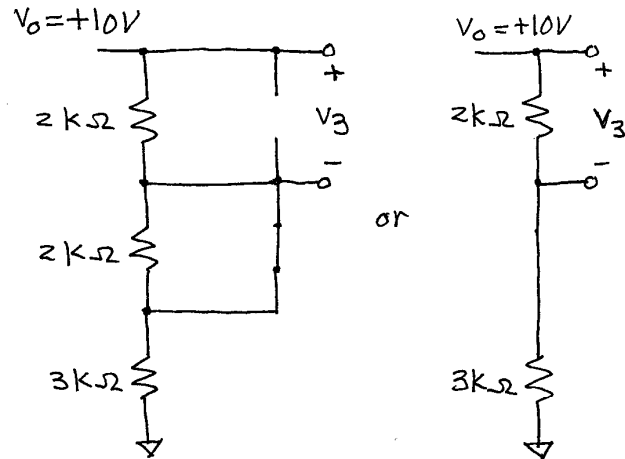
d) When $V_0 = +10V$, the equivalent circuit on the right side is as follows:



We have a voltage divider: $V_3 = \frac{10V \cdot 2k\Omega}{2k\Omega + 3k\Omega}$

$$V_3 = 4V$$

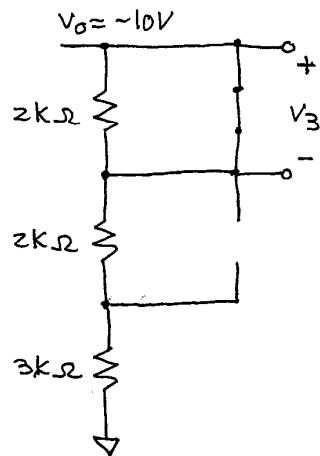When $V_0 = -10V$, the equivalent circuit on the right side is as follows:



Since we have a short across V_3 , $V_3 = 0V$.

