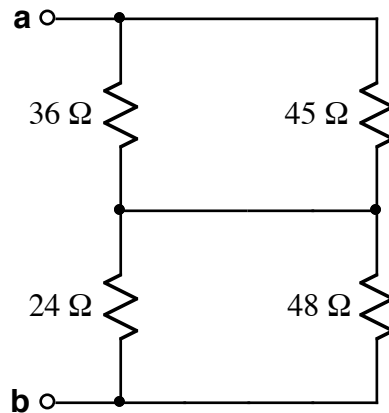


Ex:



Find the value of total resistance between terminals **a** and **b**.

**SOL'N:** The 36 Ω and 45 Ω resistors are in parallel, as are the 24 Ω and 48 Ω resistors:

$$36 \Omega \parallel 45 \Omega = 9 \Omega \cdot 4 \parallel 5 = 9 \Omega \cdot \frac{4 \cdot 5}{4 + 5} = 9 \Omega \cdot \frac{20}{9} = 20 \Omega$$

$$24 \Omega \parallel 48 \Omega = 24 \Omega \cdot 1 \parallel 2 = 24 \Omega \cdot \frac{1 \cdot 2}{1 + 2} = 24 \Omega \cdot \frac{2}{3} = 16 \Omega$$

We replace the 36 Ω and 45 Ω resistors with a single 20 Ω resistor, and we replace the 24 Ω and 48 Ω resistors with a single 16 Ω resistor. This leaves two resistors in series, whose values sum:

$$R_{ab} = 20 \Omega + 16 \Omega = 36 \Omega$$