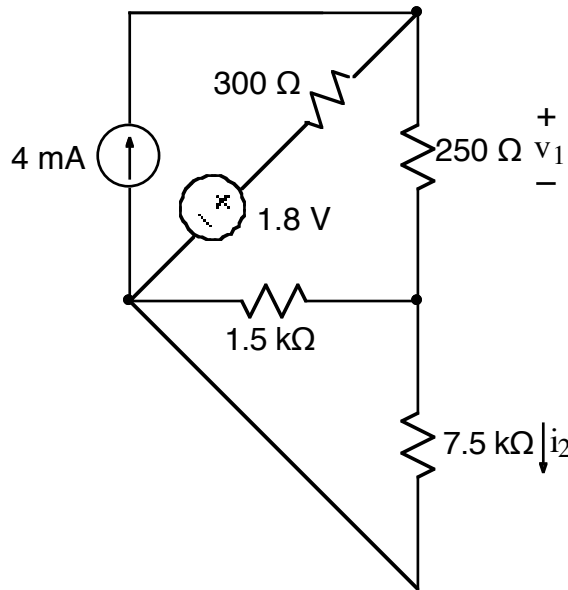



Ex:



- Use the node-voltage method to calculate  $v_1$  and  $i_2$ .
- Calculate the power in the  $1.5 \text{ k}\Omega$  resistor.

sol'n: a) We first assign a reference node. The node on the left is convenient since it is connected to the - of the 1.8V supply.

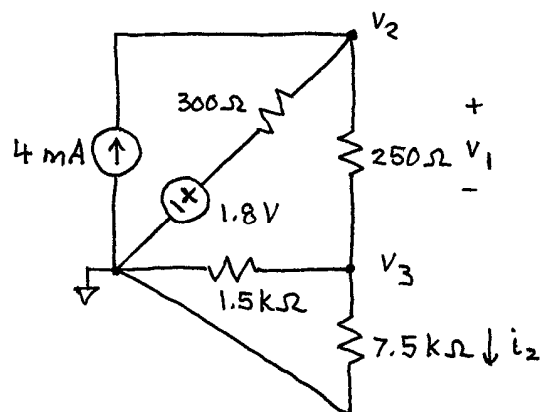We assign node voltages  $v_2$  and  $v_3$  on the right side of the circuit, (since  $v_1$  is already used).



---

We check for dependent sources and super nodes, but neither is present in this circuit.

Now we write current summation eq'ns for each node.

$$v_2 \text{ node: } -4 \text{ mA} + \frac{v_2 - 1.8 \text{ V}}{300 \Omega} + \frac{v_2 - v_3}{250 \Omega} = 0 \text{ A}$$

$$v_3 \text{ node: } \frac{v_3 - v_2}{250 \Omega} + \frac{v_3 - 0 \text{ V}}{1.5 \text{ k}\Omega} + \frac{v_3 - 0 \text{ V}}{7.5 \text{ k}\Omega} = 0 \text{ A}$$

We solve these eq'ns for  $v_2$  and  $v_3$ .

Grouping terms multiplying  $v_2$  and  $v_3$  and putting constant terms on the right side of the eq'n keeps things organized.

$$v_2 \left( \frac{1}{300 \Omega} + \frac{1}{250 \Omega} \right) + v_3 \left( \frac{-1}{250 \Omega} \right) = 4 \text{ mA} + \frac{1.8 \text{ V}}{300 \Omega}$$

$$v_2 \left( \frac{-1}{250 \Omega} \right) + v_3 \left( \frac{1}{250 \Omega} + \frac{1}{1.5 \text{ k}\Omega} + \frac{1}{7.5 \text{ k}\Omega} \right) = 0 \text{ A}$$

Multiplying both sides by  $7.5 \text{ k}\Omega$  clears the denominators.

$$v_2 (25 + 30) + v_3 (-30) = 30 \text{ V} + 1.8 \text{ V} (25)$$

$$v_2 (-30) + v_3 (30 + 5 + 1) = 0 \text{ V}$$

The 2nd eq'n is easier to solve. (We may solve for either  $v_2$  or  $v_3$ .)

$$v_2 = v_3 \frac{36}{30} = v_3 \cdot \frac{6}{5}$$

Substituting into the 1st eq'n, we have

$$v_3 \cdot \frac{6}{5} (55) + v_3 (-30) = 30V + 45V = 75V$$

$$\text{or } v_3 \cdot (66 - 30) = 75V$$


$$\text{or } v_3 \cdot 36 = 75V$$

$$\text{or } v_3 = \frac{75}{36} V = \frac{25}{12} V$$

Using our earlier eq'n for  $v_2$ , we have

$$v_2 = v_3 \cdot \frac{6}{5} = \frac{25}{12} V \cdot \frac{6}{5} = \frac{5}{2} V$$

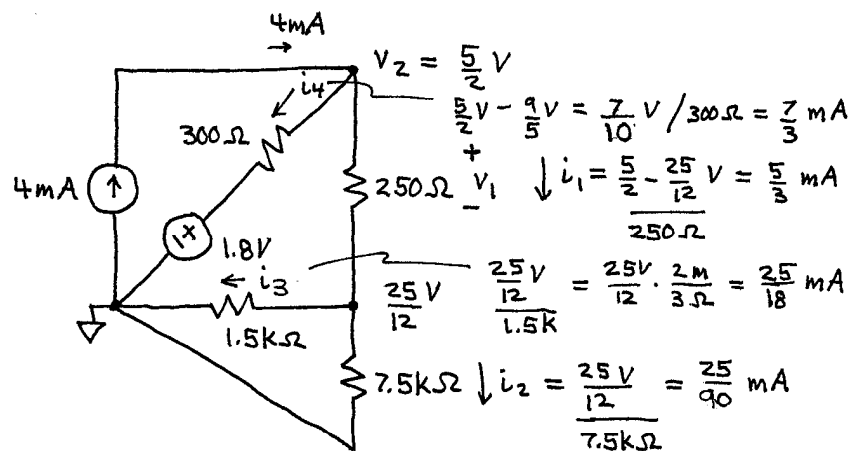Before going further we perform a consistency check on the currents to verify that they sum to zero at each node:



$$\text{Check: } -4 \text{ mA} + \frac{7}{3} \text{ mA} + \frac{5}{3} \text{ mA} = 0 \text{ mA} \checkmark$$

$$-\frac{5}{3} \text{ mA} + \frac{25}{18} \text{ mA} + \frac{25}{90} \text{ mA} = 0 \text{ mA} \checkmark$$

---

For  $v_1$  we have  $v_1 = v_2 - v_3 = \frac{5}{2} - \frac{25}{12} \text{ V}$

or  $v_1 = \frac{30}{12} - \frac{25}{12} \text{ V} = \frac{5}{12} \text{ V}$

For  $i_2$  we have  $i_2 = \frac{v_3}{7.5 \text{ k}\Omega} = \frac{25/12}{7.5} \text{ mA}$

$$i_2 = \frac{25}{12} \cdot \frac{10}{75} = \frac{5}{18} \text{ mA}$$

(Note:  $v_1$  and  $i_2$  we actually found earlier in the consistency check.)

b) The power in the  $300 \Omega$  resistor is

$$\begin{aligned} p &= v \cdot i = (v_2 - 1.8 \text{ V}) \cdot \frac{(v_2 - 1.8 \text{ V})}{300 \Omega} \\ &= \frac{(2.5 \text{ V} - 1.8 \text{ V})^2}{300 \Omega} = \frac{(0.7)^2}{300} \text{ W} \end{aligned}$$

$$p \doteq 1.63 \text{ mW}$$

The power in the  $1.5 \text{ k}\Omega$  resistor is

$$p = v \cdot i = \frac{(v_2 - v_1)^2}{1.5 \text{ k}\Omega} = \frac{\left(\frac{5}{2} - \frac{5}{12}\right)^2}{1.5 \text{ k}\Omega} = \frac{\left(\frac{25}{12}\right)^2}{1.5 \text{ k}\Omega} = 2.89 \text{ mW}$$