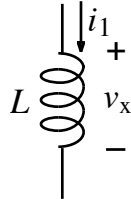


**Ex:** In (a)-(c), the current  $i_L(t)$  flowing into a  $2 \mu\text{H}$  inductor is listed. Find the voltage,  $v_L(t)$ , across the inductor in each case as a function of time:



- a)  $i_L(t) = 3 \text{ mA}$
- b)  $i_L(t) = 10t \text{ MA/s}$
- c)  $i_L(t) = 8 \cos(2\pi \cdot 10\text{k} \cdot t) \mu\text{A}$

**SOL'N:** We use the defining equation for an inductor in each case:

$$v_L = L \frac{di_L}{dt}$$

a)

$$v_L = L \frac{d}{dt} 3 \text{ mA} = L \cdot 0 \text{ A/s} = 0 \text{ V}$$

b)

$$v_L = L \frac{d}{dt} 10t \text{ MA/s} = 2 \mu\text{H} \cdot 10 \text{ MA/s} = 20 \text{ V}$$

c)

$$v_L = L \frac{d}{dt} 8 \cos(2\pi \cdot 10\text{k} \cdot t) \mu\text{A} = 2 \mu\text{H} \cdot (-8 \sin(2\pi \cdot 10\text{k} \cdot t) 20\text{k}\pi \mu\text{A/s})$$

$$v_L = -320\pi \sin(2\pi \cdot 10\text{k} \cdot t) \text{ nV}$$