
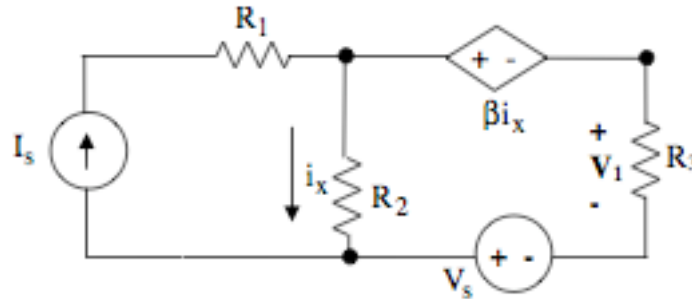


Ex:

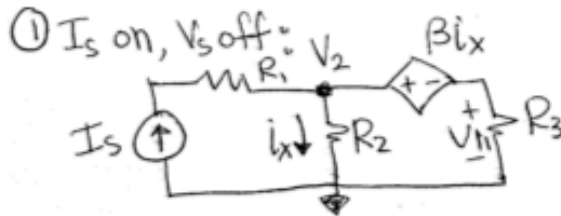

Using superposition, derive an expression for  $v_1$  that contains no circuit quantities other than  $i_s$ ,  $v_s$ ,  $R_1$ ,  $R_2$ ,  $R_3$ , and  $\beta$ , where  $\beta < 0$ .

SOL'N:



node-V:

$$-I_s + \frac{V_2}{R_2} + \frac{V_2 - \beta i_x}{R_3} = 0$$

$$i_x = \frac{V_2}{R_2}$$


$$-I_s + \frac{V_2}{R_2} + \frac{V_2}{R_3} - \frac{\beta \cdot V_2}{R_3 \cdot R_2} = 0$$

$$V_2 \left( \frac{1}{R_2} + \frac{1}{R_3} - \frac{\beta}{R_2 R_3} \right) = I_s$$

$$V_2 = \frac{I_s (R_2 R_3)}{R_2 + R_3 - \beta} \Rightarrow +V_2 - \beta \left( \frac{V_2}{R_2} \right) - V_1 = 0$$

$$V_1 = \left( 1 - \frac{\beta}{R_2} \right) \left( \frac{I_s R_2 R_3}{R_2 + R_3 - \beta} \right)$$

②  $I_s$  off,  $V_s$  on:

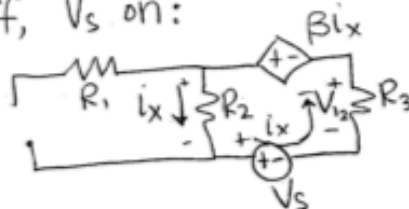

V-loop:  $-i_x R_3 + \beta i_x - i_x R_2 - V_s = 0$

$$i_x = \frac{-V_s}{R_2 + R_3 - \beta} \Rightarrow V_2 = -i_x R_3$$

$$\therefore V_1 = \frac{+V_s R_3}{R_2 + R_3 - \beta}$$

$$V_1 = V_1 + V_2 = \left( 1 - \frac{\beta}{R_2} \right) \left( \frac{I_s R_2 R_3}{R_2 + R_3 - \beta} \right) + \frac{V_s R_3}{R_2 + R_3 - \beta}$$