
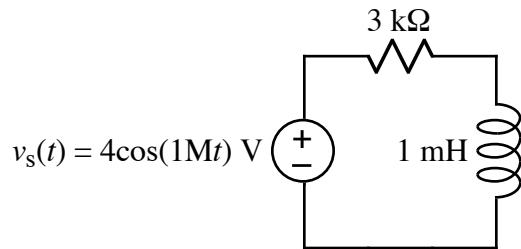


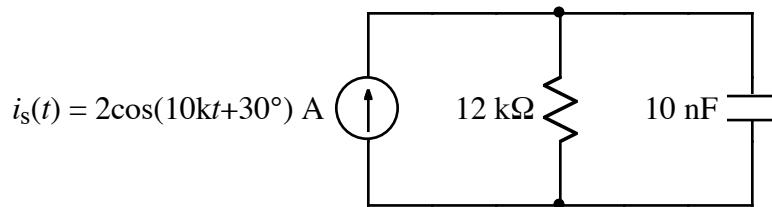

Ex:




- a) Find time-domain expressions for the waveforms of the voltages across the R and L in the above circuit.



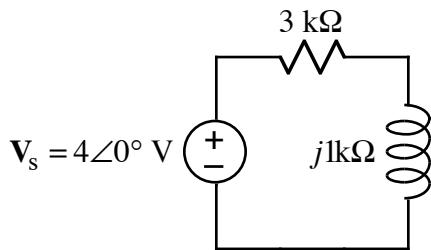- b) Find time-domain expressions for the waveforms of the currents through the R and C in the above circuit.

SOL'N: a) First, we transform the circuit to the frequency-domain.

$$j\omega L = j1M \cdot 1m \Omega = j1 \text{ k}\Omega$$



Second, we use a voltage-divider formula to find the voltage across the R and L .

$$\mathbf{V}_R = 4\angle 0^\circ \frac{3\text{k}\Omega}{3\text{k}\Omega + j1\text{k}\Omega} = 4V \frac{3}{3+j1} = 4V \frac{3}{3+j} \frac{3-j}{3-j}$$

or

$$\mathbf{V}_R = 12V \frac{3-j}{10} = 1.2V \cdot \sqrt{3^2 + 1^2} \angle \tan^{-1}\left(\frac{-1}{3}\right) = 1.2\sqrt{10} \angle -18.4^\circ \text{ V}$$

or

$$\mathbf{V}_R = 3.79 \angle -18.4^\circ \text{ V}$$

The calculation for the inductor voltage is similar to the above.

$$\mathbf{V}_L = 4 \angle 0^\circ \text{ V} \frac{j1\text{k}\Omega}{3\text{k}\Omega + j1\text{k}\Omega} = 4\text{V} \frac{j1}{3+j1} = 4\text{V} \frac{j}{3+j} \frac{3-j}{3-j}$$

or

$$\mathbf{V}_L = 4\text{V} \frac{1+j3}{10} = 0.4\text{V} \cdot \sqrt{1^2+3^2} \angle \tan^{-1}\left(\frac{3}{1}\right) = 0.4\sqrt{10} \angle 71.6^\circ \text{ V}$$

or

$$\mathbf{V}_L = 1.26 \angle 71.6^\circ \text{ V}$$


Third, we take the inverse phasor.

$$v_R(t) = 1.2\sqrt{10} \cos(1Mt - 18.4^\circ) \text{ V}$$

$$v_L(t) = 0.4\sqrt{10} \cos(1Mt + 71.6^\circ) \text{ V}$$

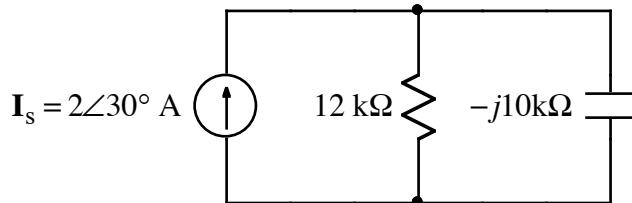b) First, we transform the circuit to the frequency-domain.

$$\frac{1}{j\omega C} = \frac{1}{j10\text{k} \cdot 10\text{n}} \Omega = -j10\text{k}\Omega$$



Second, we use a current-divider formula to find the current through the R and C .

$$I_R = 2 \angle 30^\circ \text{ A} \frac{-j10\text{k}\Omega}{12\text{k}\Omega - j10\text{k}\Omega} = 2 \angle 30^\circ \text{ A} \frac{10 \angle -90^\circ}{\sqrt{12^2 + 10^2}} \angle \tan^{-1}\left(\frac{-10}{12}\right) \text{ A}$$

or

$$I_R = \frac{10}{\sqrt{61}} \angle 30^\circ - 90^\circ - \tan^{-1}\left(\frac{-10}{12}\right) \text{ A} = \frac{10}{\sqrt{61}} \angle -20.2^\circ \text{ A}$$

The calculation for the capacitor current is similar to the above.

$$I_C = 2\angle 30^\circ A \frac{12k\Omega}{12k\Omega - j10k\Omega} = 2\angle 30^\circ A \frac{12}{\sqrt{12^2 + 10^2}} \angle \tan^{-1}\left(\frac{-10}{12}\right) A$$

or

$$I_C = \frac{12}{\sqrt{61}} \angle 30^\circ - \tan^{-1}\left(\frac{-10}{12}\right) A = \frac{10}{\sqrt{61}} \angle 69.8^\circ A$$

Third, we take the inverse phasor.

$$i_R(t) = \frac{10}{\sqrt{61}} \cos(10kt - 20.2^\circ) A$$

$$i_C(t) = \frac{12}{\sqrt{61}} \cos(10kt + 69.8^\circ) A$$