
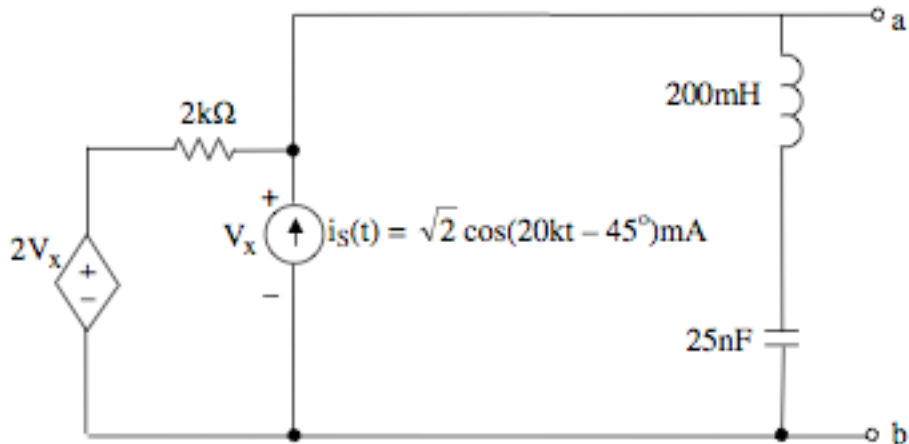


Ex:

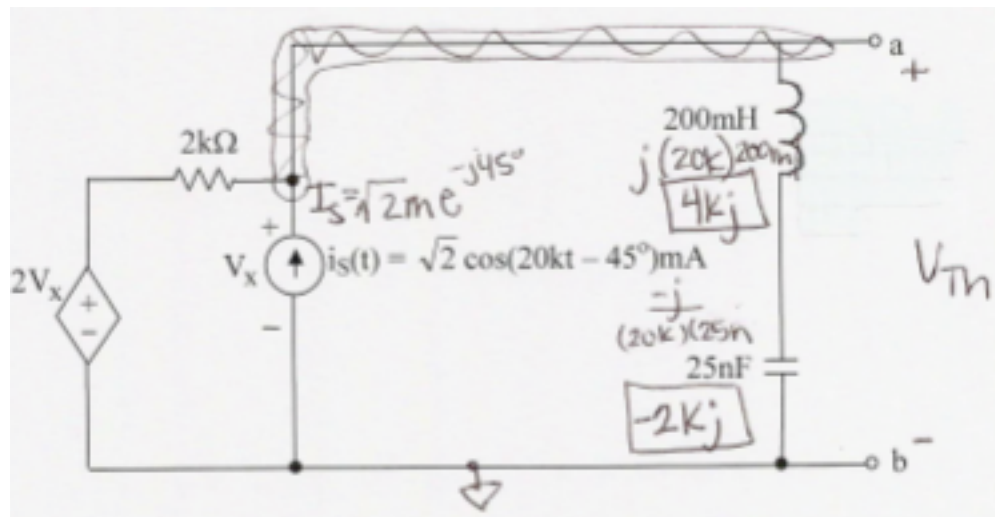

- Draw a frequency-domain equivalent of the above circuit. Show a numerical phasor value for $i_s(t)$, and show numerical impedance values for R , L , and C . Label the dependent source appropriately.
- Find the Thevenin equivalent (in the frequency domain) for the above circuit. Give the numerical phasor value for V_{Th} and the numerical value for the impedance value of z_{Th} .

SOL'N:



① Find V_{Th} :

$$V_{Th} = V_x$$

Using node-voltage:


$$V_{Th} \frac{-2V_{Th}}{2k} + \frac{V_{Th}}{(4kj-2kj)} - \sqrt{2}me^{-j45^\circ} = 0$$

$$V_{Th} \left(\frac{j}{2kj} - \frac{2j}{2kj} + \frac{1}{2kj} \right) = \sqrt{2}me^{-j45^\circ}$$

$$V_{Th} \left(\frac{1-j}{2kj} \right) = \frac{\sqrt{2}me^{-j45^\circ} \cdot (2ke^{j90^\circ})}{(1-j)} = \frac{\sqrt{2}m(2k)e^{j45^\circ}}{\sqrt{2}e^{j45^\circ}}$$

$$\boxed{V_{Th} = 2e^{j90^\circ}}$$

② Find Z_{Th} :

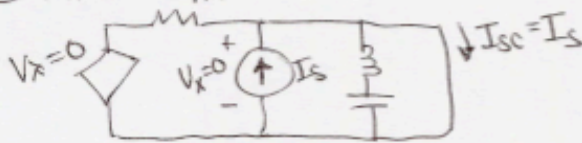

$$\therefore Z_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{2e^{j90^\circ}}{\sqrt{2}me^{-j45^\circ}}$$

$$\boxed{Z_{Th} = \frac{2k}{\sqrt{2}}e^{j135^\circ}}$$