
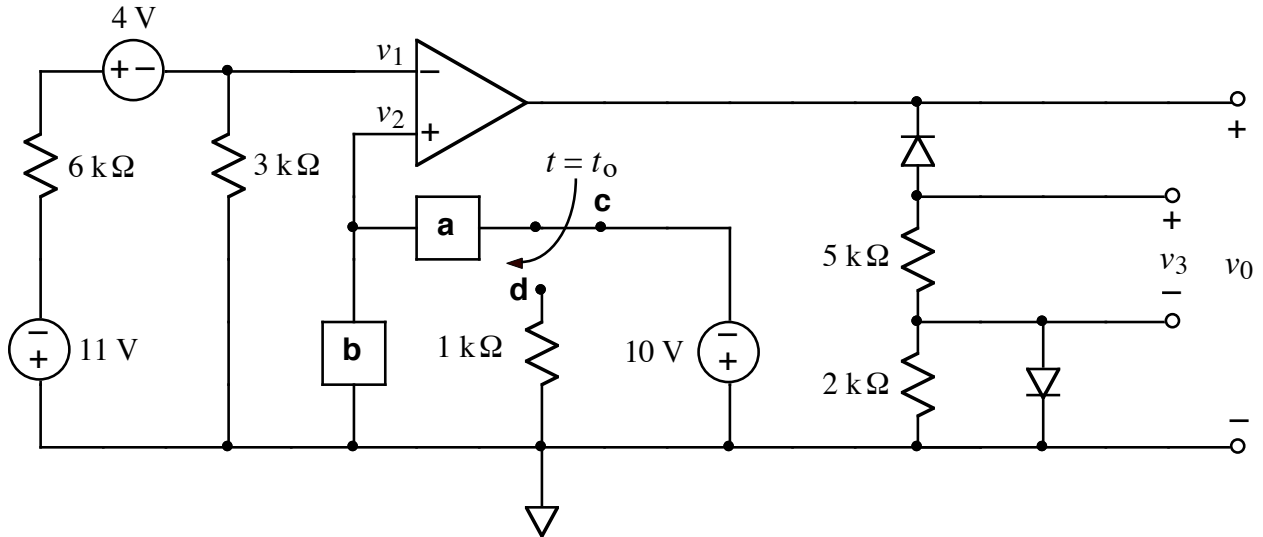


Ex:

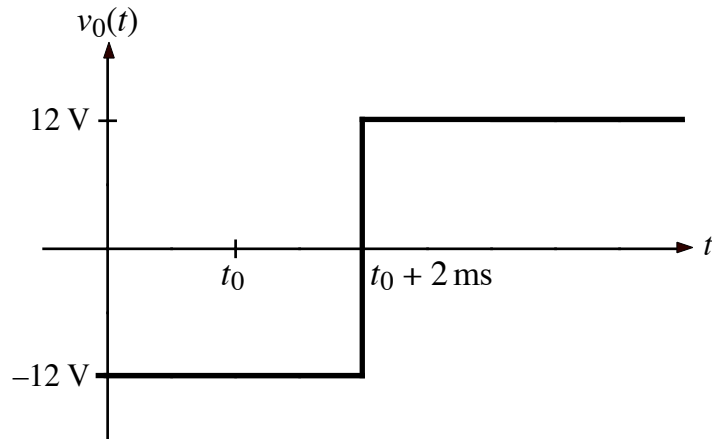

After being in position **c** for a long time, the switch moves from **c** to **d** at $t = t_0$.

Rail voltages = ± 12 V



- Choose either an R or C to go in box **a** and either an R or C to go in box **b** to produce the $v_0(t)$ shown above. (Note that v_0 stays high forever after $t_0 + 2$ ms.) Specify which element goes in each box and its value.
- Sketch $v_1(t)$, showing numerical values appropriately.
- Sketch $v_2(t)$, showing numerical values appropriately.
- Sketch $v_3(t)$. Show numerical values for $t < t_0$, for $t_0 < t < t_0 + 2$ ms, and for $t_0 + 2$ ms $< t$. Use the ideal model of the diode: when forward biased, its resistance is zero; when reverse biased, its resistance is infinite.

sol'n: a) For v_o to be low, (i.e., $-12V$), we must have $v_2 < v_1$.

To find v_1 , we slide the $4V$ source through the $6k\Omega$ resistor and find that we have the equivalent of a $-15V$ source and a voltage divider formed by the $3k\Omega$ and $6k\Omega$ resistors.

$$v_1 = -15V \cdot \frac{3k\Omega}{3k\Omega + 6k\Omega} = -5V$$

At $t=0^-$, we must have $v_2 < -5V$.

$a=R$
 $b=C$ [This is possible only if box **a** contains a resistor and box **b** contains a capacitor. If **a** is an **R** and **b** is a **C**, then the **C** will charge until $v_2 = -10V < v_1$.

When the switch moves from **c** to **d**, the capacitor voltage start charging toward $0V$, but it will still be $-10V$ initially. This gives the desired waveform for $v_o(t)$: v_o will go high when $v_2 = v_1 = -5V$.


Note: The reasons why other components in boxes **a** and **b** fail to yield the desired $v_o(t)$ are as follows:

$a = R$ and $b = R$ cannot give a waveform that changes after a delay. v_o would have to change instantly at $t = t_0$.

$a = C$ and $b = R$ would result in C charging until no current flows in R . This means $v_2 = 0V$, or $v_2 > v_1$, causing v_o to be high before $t = t_0$.

$a = C$ and $b = C$ would result in an arbitrary voltage at v_2 . The total voltage drop across the two C 's would be $10V$. When the switch changes from c to d , the capacitors would charge until the total voltage drop across them was $0V$. The same current would flow in both C 's, causing a voltage change that would be inversely proportional to the C values. The waveform shown for $v_o(t)$ could be produced, but there is a lack of control over the initial value of v_2 . This would make the timing of the $v_o(t)$ waveform uncertain. Thus, we reject this solution.

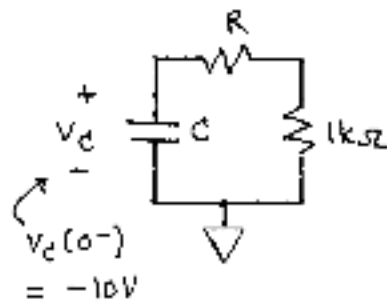Now we find possible values for R and C . We have the following circuit model for $t > t_0$:



$$v_c(t > t_0) = v_c(t \rightarrow \infty) + \left[v_c(t_0^+) - v_c(t \rightarrow \infty) \right] e^{-t/\tau}$$

\parallel \parallel \parallel
 $0V$ $-10V$ $0V$

$$v_c(t > t_0) = -10 e^{-t/\tau} \text{ V (where we take } t_0 = 0)$$

$$\text{where } \tau = (R + 1k\Omega) C$$

$$\text{We want } v_c(t = 2ms) = v_1 = -5V$$

$$\text{or } -10 e^{-2ms/\tau} = -5V$$


$$e^{-2ms/\tau} = \frac{1}{2}$$

$$-2ms = \tau \ln \frac{1}{2}$$


$$\tau = \frac{2ms}{\ln 2} \approx 2.9ms$$

One sol'n is $R = 1.9k\Omega$ and $C = 1\mu F$.
 Note: $R = 0\Omega$ is min R , $C = 2.9\mu F$ is max C .


b) $v_1(t) = -5V$ as shown earlier.

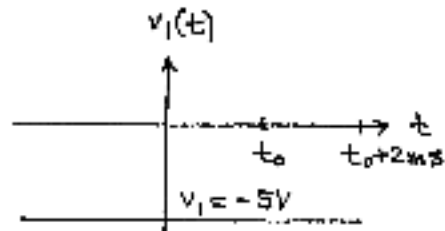

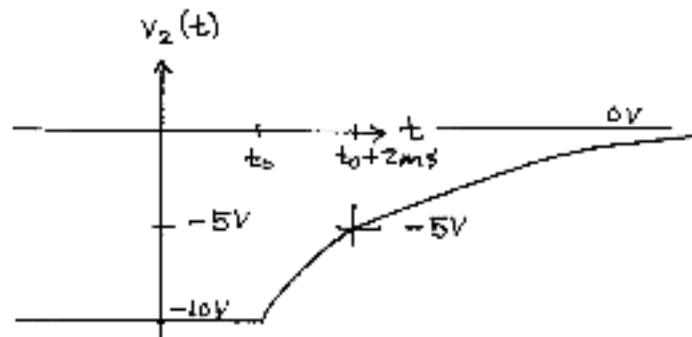c) $v_2 = v_c(t > 0) = -10V e^{-t/2.9ms}$ from (a)



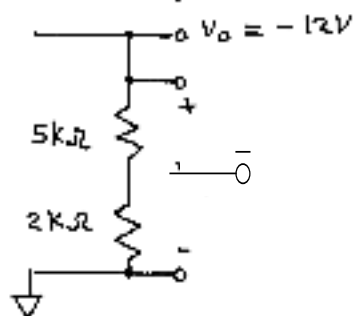d) When v_0 is low, the top diode will act like a wire and the bottom diode will act like an open circuit.



We have a voltage divider: $v_3 = -12V \cdot \frac{5k\Omega}{2k\Omega + 5k\Omega} = -\frac{60}{7}V$.

When v_0 is high, the top diode will act like an open circuit, leaving the bottom part of the circuit disconnected from v_0 , (or any other power source).

Thus $v_3 = 0V$ when v_0 is high.

