
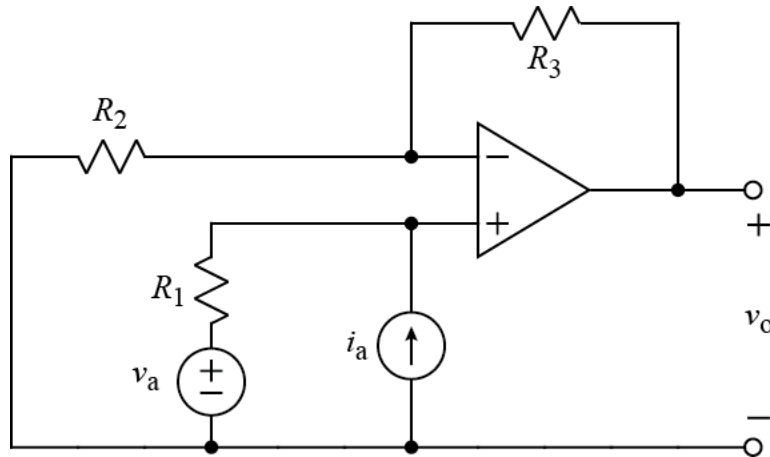


Ex:

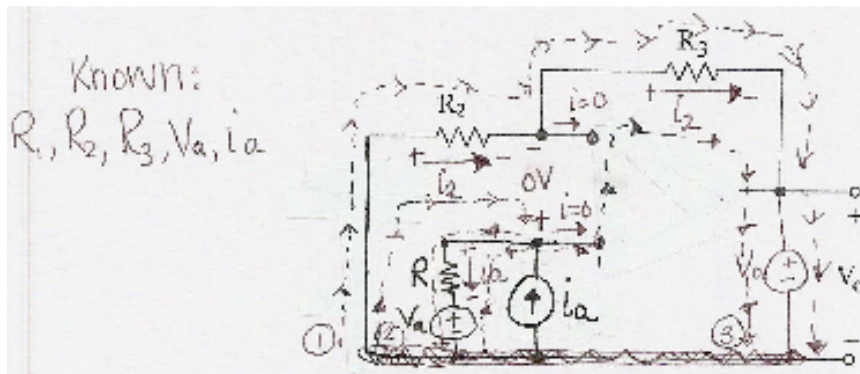

The op-amp operates in the linear mode. Using an appropriate model of the op-amp, derive an expression for v_o in terms of not more than v_a , i_a , R_1 , R_2 , and R_3 .

SOL'N:



KNOWN:
 R_1, R_2, R_3, v_a, i_a

V-loop: ① $-i_2 R_2 - i_2 R_3 - v_o = 0$
 ② $-i_2 R_2 - i_a R_1 + v_a = 0$
 ③ $+v_a + i_a R_1 - i_2 R_3 - v_o = 0$

① $v_o = -i_2 (R_2 + R_3)$

② $i_2 = -\frac{(v_a + i_a R_1)}{R_2}$

plug ② into ①

$$v_o = \frac{(v_a + i_a R_1)(R_2 + R_3)}{R_2} = \left(1 + \frac{R_3}{R_2}\right)(v_a + i_a R_1)$$