
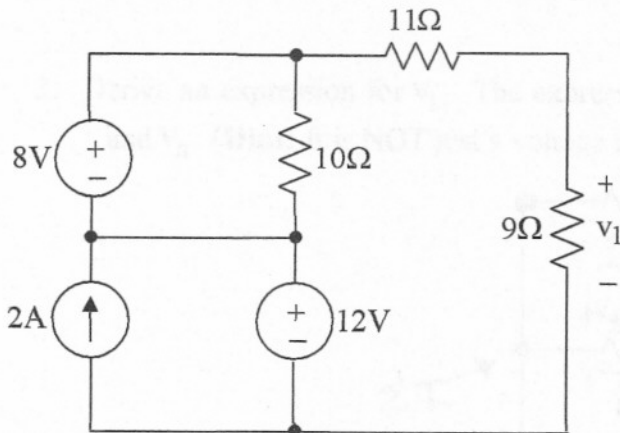


1. Calculate V_1 .

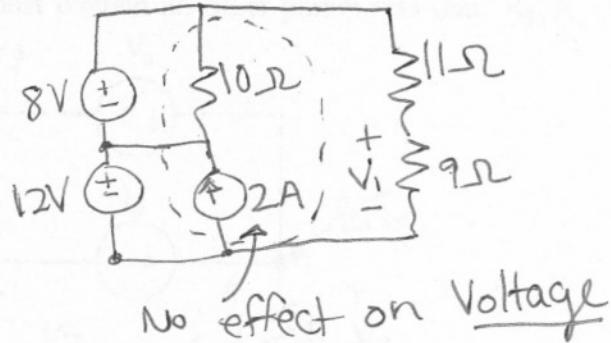

Notice that it can be redrawn as




No effect on Voltage


\therefore V-divider :

$$V_1 = \frac{(12+8)9}{9+11} = \frac{20(9)}{20} = \boxed{9V}$$

2. Calculate i_1 .

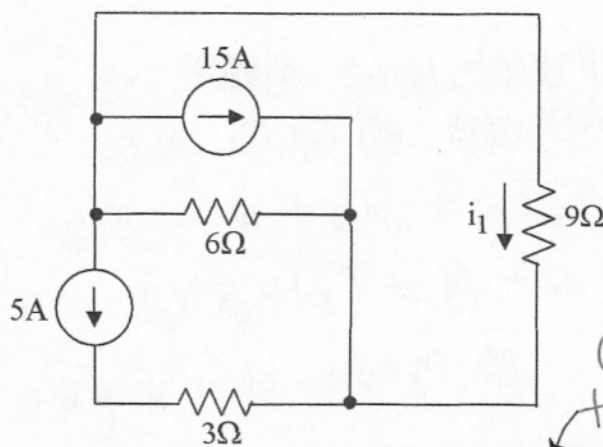

Can be redrawn:

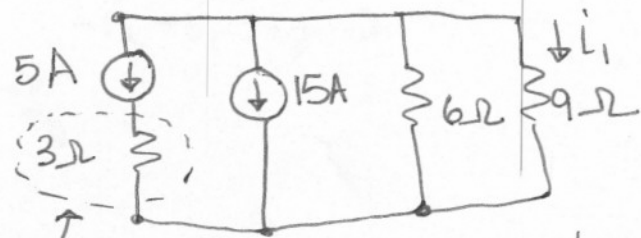

This will change Voltage, no change in current. 5A fixes branch current


Can add both current sources together.

$$i_1 = \frac{-(5+15)(6)}{6+9} = \frac{-20(6)}{15} = \frac{-4(2)}{1} = \boxed{-8A}$$

$$i_1 = i_3 - i_a = \frac{(i_a R_1 - V_a)}{(R_1 + R_2 + R_3)} - i_a$$

$$i_1 = \frac{i_a(R_2 + R_3) - V_a}{(R_1 + R_2 + R_3)}$$


3. (30 points)

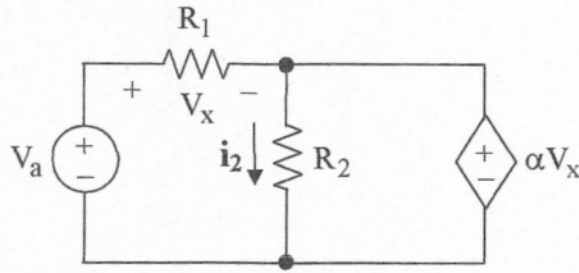

20 pts a) Drive the expression for i_2 containing not more than circuit parameters α , R_1 , R_2 , and V_a .

10 pts b) State the symbolic expression for power in the resistor, R_2 . Use only α , R_1 , R_2 , and V_a in the expression.

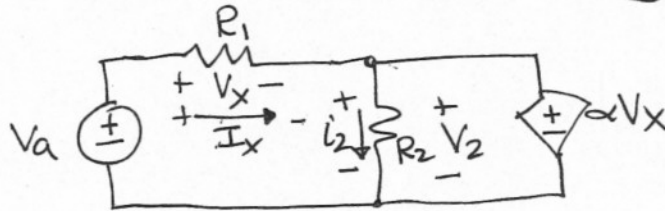a) ① Label all currents and voltages \Rightarrow



② Ohm's Law \Rightarrow

$$V_x = I_x R_x$$

$$V_2 = i_2 R_2$$

③ V loop \Rightarrow

$$+V_a - V_x - V_2 = 0$$

$$-V_2 + \alpha V_x = 0 \Rightarrow V_2 = \alpha V_x = \frac{\alpha V_a}{(1+\alpha)}$$

$$(*) +V_a - V_x - \alpha V_x = 0$$

$$V_a - V_x(1+\alpha) = 0$$


$$\frac{V_a}{1+\alpha} = V_x$$

$$i_2 = \frac{V_2}{R_2} = \frac{\alpha V_a}{(1+\alpha) R_2}$$

b) power = $V_2 \cdot i_2 = \frac{\alpha^2 V_a^2}{(1+\alpha)^2 R_2}$

If $(\alpha, V_a, R_2) > 0$ than absorbs power

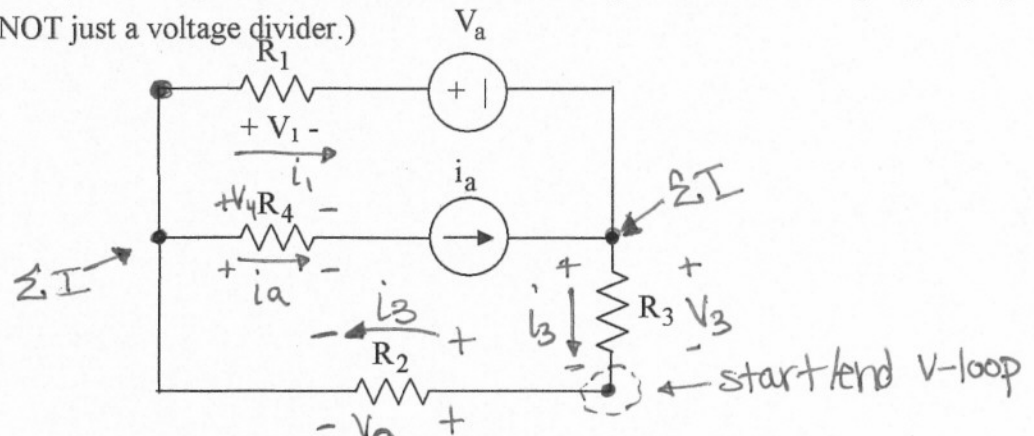3. Derive an expression for V_1 . The expression must contain no other parameters than R_1, R_2, R_3, i_a, R_4 and V_a . (Hint: It is NOT just a voltage divider.)



Step 1: Label a I and V through every R . Label polarity

Step 2: a. Ohm's Laws:

- ① $V_1 = i_1 R_1$
- ② $V_2 = i_3 R_2$
- ③ $V_3 = i_3 R_3$
- ④ $V_4 = i_a R_4$

b. V-loop: (avoid taking loop through I src.)

$$\textcircled{5} +V_3 + V_a + V_1 + V_2 = 0$$

c. $\sum I$:

$$\textcircled{6} +i_a + i_1 - i_3 = 0$$

$$-i_a - i_1 + i_3 = 0$$

Step 3: Solve simultaneous eq.

plug ①, ②, ③ into ⑤

$$i_3 R_3 + V_a + i_1 R_1 + i_3 R_2 = 0$$

$$i_3 (R_2 + R_3) + i_1 R_1 + V_a = 0$$

plug i_1 into above eq.

$$i_3 (R_2 + R_3) + (i_3 - i_a) R_1 + V_a = 0$$

$$i_3 (R_1 + R_2 + R_3) - i_a R_1 + V_a = 0$$

$$\therefore i_3 = \frac{(i_a R_1 - V_a)}{R_1 + R_2 + R_3}$$

$$i_1 = i_3 - i_a = \frac{(i_a R_1 - V_a)}{(R_1 + R_2 + R_3)} - i_a$$


$$i_1 = \frac{i_a (R_2 + R_3) - V_a}{(R_1 + R_2 + R_3)}$$

← eq. with i_1 & i_3 unknown
 ⑥ also has i_1 & i_3 "
 \therefore solve ⑥ for i_1 as function
 of $i_3 \Rightarrow i_1 = (i_3 - i_a)$


$$V_1 = i_1 R_1$$

$$\therefore V_1 = \frac{i_a R_1 (R_2 + R_3) - V_a R_1}{(R_1 + R_2 + R_3)}$$

4. (30 points)

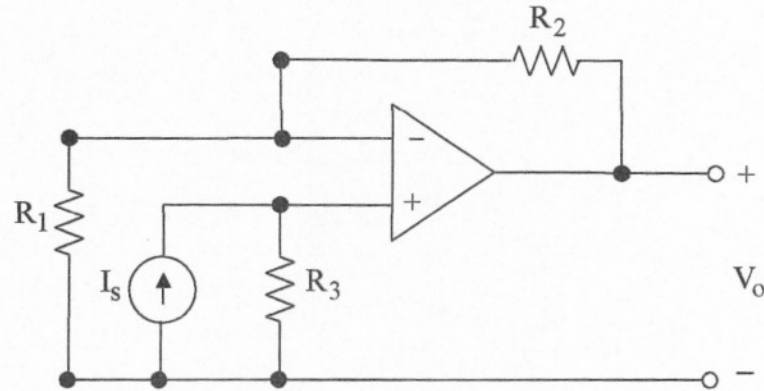

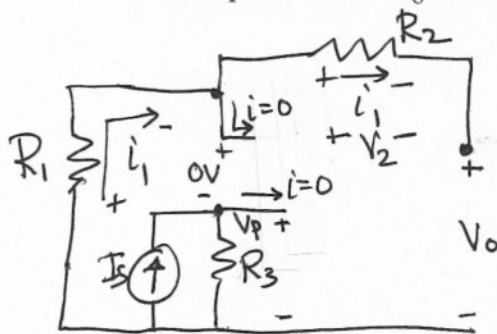The op-amp operates in the linear mode. Using an appropriate model of the op-amp, derive an expression for V_o in terms of not more than I_s , R_1 , R_2 , and R_3 .



$$V_p = +I_s(R_3)$$

$$\textcircled{1} +I_s(R_3) - V_2 - V_o = 0$$

$$V_2 = (i_1 \cdot R_2)$$


$$+I_s(R_3) - i_1 R_2 - V_o = 0$$

$$+i_1 R_1 + I_s R_3 = 0$$


$$i_1 = -\frac{I_s R_3}{R_1}$$

$$\text{From } \textcircled{1} : I_s R_3 + \frac{I_s R_3 R_2}{R_1} = V_o$$

$$\therefore V_o = \frac{I_s R_3 (R_1 + R_2)}{R_1}$$

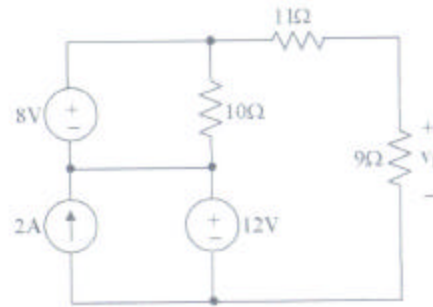1. Calculate V_1 .

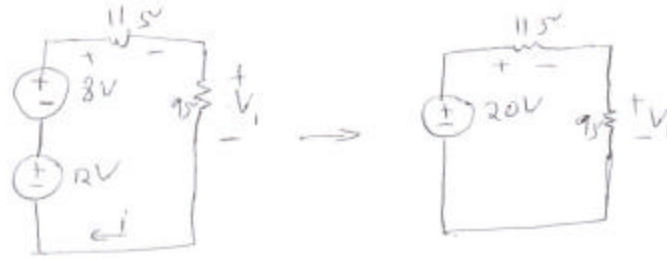
1) The voltage across the 10Ω resistor is equal to $8V$ (parallel to the voltage source). We can redraw the right loop as follows



Then, it is a voltage divider

$$V_1 = 20 \times \frac{9}{9+11} = 20 \times \frac{9}{20} = 9V$$

2. Calculate i_1 .

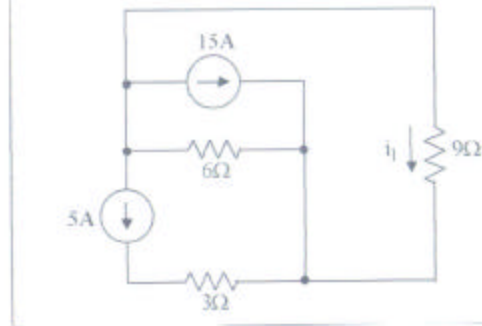

2.) We can redraw the circuit as follows



Since the two current sources contribute currents at the same direction to ~~node~~ node 1, and since we do not care about the voltage across the 3Ω resistor, we can again draw the circuit as follows.




then using current divider :-


$$i = -20 \times \frac{6}{9+6} = -20 \times \frac{4}{15} = -8A$$

The negative sign is because i is in the opposite direction of the actual current

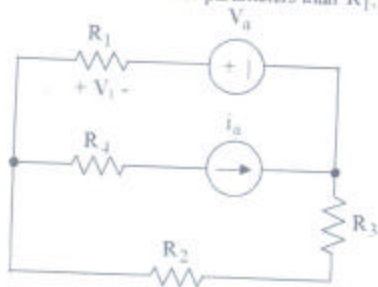3. Derive an expression for V_1 . The expression must contain no other parameters than R_1, R_2, R_3, i_a , and V_a .
 (Hint: It is NOT just a voltage divider.)



3. Name the voltages and currents...

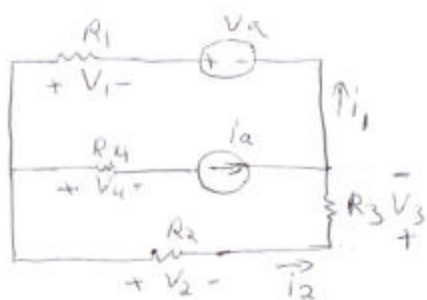

V-loop:- take the outer loop because we don't know the voltage across the current source.

$$V_a + V_1 - V_3 - V_2 = 0 \rightarrow 1$$

we need V_3 and V_2 in terms of R_3, R_2

$$\text{Ohm's: } V_3 = R_3 i_2, V_2 = R_2 i_2 \rightarrow 2$$

Now, we need i_2 in terms of i_a & i_1

$$i_2 + i_a - i_1 = 0 \Rightarrow i_2 = i_1 - i_a \rightarrow 3$$

We still need i_1 in terms of V_1 and R_1

$$i_1 = \frac{-V_1}{R_1}$$

substituting in 3

$$i_2 = \frac{-V_1}{R_1} - i_a$$

substituting for i_2 in 2

$$V_3 = R_3 \left(\frac{-V_1}{R_1} - ia \right), \quad V_2 = R_2 \left(\frac{-V_1}{R_1} - ia \right)$$

substituting for V_3 and V_2 in 1, we get

$$V_a + V_1 - R_3 \left(\frac{-V_1}{R_1} - ia \right) - R_2 \left(\frac{-V_1}{R_1} - ia \right) = 0$$


$$\Rightarrow V_1 - (R_3 + R_2) \left(\frac{-V_1}{R_1} - ia \right) = -V_a$$

$$\Rightarrow V_1 + \frac{V_1 (R_3 + R_2)}{R_1} + ia(R_3 + R_2) = -V_a$$

$$\Rightarrow V_1 \left(1 + \frac{R_3 + R_2}{R_1} \right) = -V_a - ia(R_3 + R_2)$$

$$\Rightarrow V_1 \left(\frac{R_1 + R_2 + R_3}{R_1} \right) = -V_a - ia(R_2 + R_3)$$
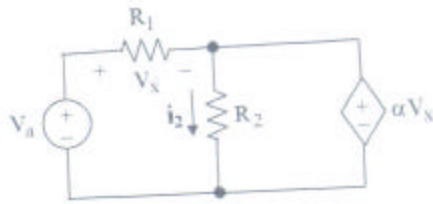
$$\Rightarrow V_1 = \frac{-R_1 (V_a + ia(R_2 + R_3))}{R_1 + R_2 + R_3}$$



- Derive the expression for i_2 containing not more than circuit parameters α , R_1 , R_2 , and V_a .
- State the symbolic expression for power in the resistor, R_2 . Use only α , R_1 , R_2 , and V_a in the expression.

4. a) The voltage across R_2 is αV_x because they are in parallel.

Using the outer V-loop

$$V_a - V_x - \alpha V_x = 0$$

$$\Rightarrow -V_x - \alpha V_x = -V_a$$

$$\Rightarrow V_x(1 + \alpha) = V_a$$

$$\Rightarrow V_x = \frac{V_a}{1 + \alpha} \rightarrow \text{①}$$


Ohm's law:- $i_2 = \frac{V_2}{R_2}$, $V_2 = \alpha V_x$

$$i_2 = \frac{\alpha V_x}{R_2} \quad \text{using ①, we get}$$

$$i_2 = \frac{\alpha V_a}{R_2(1 + \alpha)}$$

$$b) P_{R_2} = i_2 V_2 = \frac{\alpha V_a}{R_2(1 + \alpha)} \times \alpha V_x$$
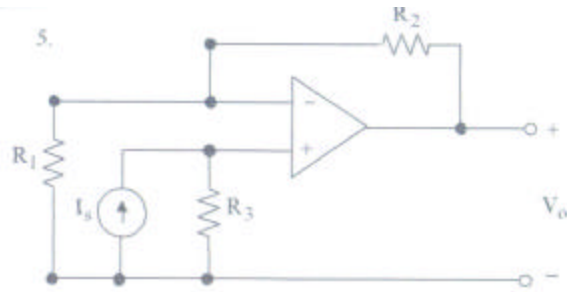
$$= \frac{\alpha V_a}{R_2(1 + \alpha)} \times \frac{\alpha V_a}{(1 + \alpha)} = \left(\frac{\alpha V_a}{1 + \alpha} \right)^2 / R_2$$



The op-amp operates in the linear mode. Using an appropriate model of the op-amp, derive an expression for V_o in terms of not more than I_s , R_1 , R_2 , and R_3 .

$$5. \quad V_1 = V_2 = I_s R_3 \quad \text{--- (1)}$$

$$V_1 = V_o \times \frac{R_1}{R_1 + R_2} \quad (\text{voltage divider})$$

$$\Rightarrow V_o = \frac{V_1 (R_1 + R_2)}{R_1}$$

using (1) and substituting for V_1

$$V_o = \frac{I_s R_3 (R_1 + R_2)}{R_1}$$