


UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1270

HOMEWORK #3

Spring 2008

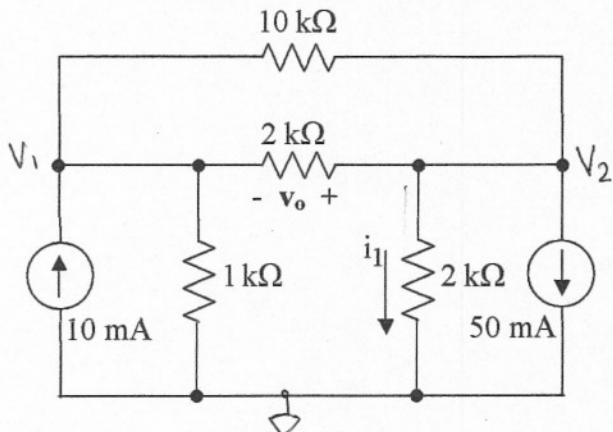1. Use node-voltage method to find i_1 and v_o .



$$V_o = (V_2 - V_1) = -52.86 + 13.6 = \boxed{-39.26 \text{ V}}$$

$$i_1 = \frac{V_2}{2k} = -\frac{52.86}{2k} = \boxed{-26.4 \text{ mA}}$$

$$-10 \text{ mA} + \frac{V_1}{1k} + \frac{(V_1 - V_2)}{2k} + \frac{(V_1 - V_2)}{10k} = 0$$

$$V_1 \left(\frac{1}{1k} + \frac{1}{2k} + \frac{1}{10k} \right) - V_2 \left(\frac{1}{2k} + \frac{1}{10k} \right) - 10 \text{ m} = 0$$

$$V_1 \left(\frac{10}{10k} + \frac{5}{10k} + \frac{1}{10k} \right) - V_2 \left(\frac{5}{10k} + \frac{1}{10k} \right) - 10 \text{ m} = 0$$

$$V_1 \left(\frac{16}{10k} \right) - V_2 \left(\frac{6}{10k} \right) - 10 \text{ m} = 0 \Rightarrow V_1 = \frac{[10 \text{ m} + V_2 \left(\frac{6}{10k} \right)] 10k}{16} = \boxed{-13.6}$$

$$+ 50 \text{ m} + \frac{V_2}{2k} + \frac{(V_2 - V_1)}{2k} + \frac{(V_2 - V_1)}{10k} = 0$$

$$+ 50 \text{ m} + V_2 \left(\frac{1}{2k} + \frac{1}{2k} + \frac{1}{10k} \right) - V_1 \left(\frac{1}{2k} + \frac{1}{10k} \right) = 0$$

$$+ 50 \text{ m} + V_2 \left(\frac{5}{10k} + \frac{5}{10k} + \frac{1}{10k} \right) - V_1 \left(\frac{5}{10k} + \frac{1}{10k} \right) = 0$$

$$+ 50 \text{ m} + V_2 \left(\frac{11}{10k} \right) - V_1 \left(\frac{6}{10k} \right) = 0$$


$$+ 50 \text{ m} + V_2 \left(\frac{11}{10k} \right) - \frac{100}{16} \left(\frac{6}{10k} \right) - V_2 \left(\frac{6}{16} \cdot \frac{6}{10k} \right) = 0$$

$$V_2 \left(\frac{11(16)}{10k(16)} - \frac{6 \cdot 6}{(16)10k} \right) = -50 \text{ m} + \frac{100}{16} \left(\frac{6}{10k} \right)$$

$$V_2 \left(\frac{176 - 36}{16 \cdot 10k} \right) = -50 \text{ m} + \frac{(600)}{16(10k)}$$

$$V_2 = \frac{-0.04625}{8.75 \times 10^{-4}} = -52.86$$

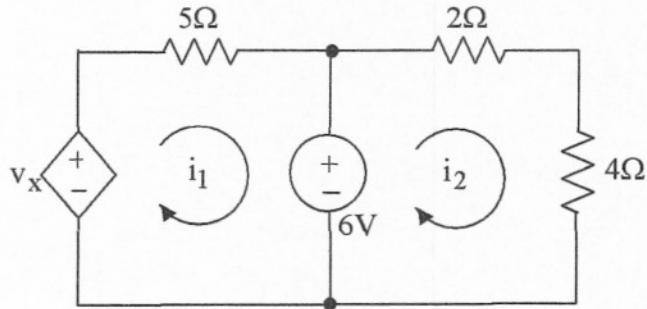4. a. Use the mesh-current method to find i_1 and i_2 . Use $V_x = 0.5i_2$.
 b. Find the power dissipated by the dependent current source.



$$+v_x - i_1(5) - 6 = 0$$

$$0.5i_2 - 5i_1 - 6 = 0$$

$$i_2 = \frac{5i_1 + 6}{0.5} = 10i_1 + 12$$

$$+6 - i_2(2) - i_2(4) = 0$$

$$i_2(6) = 6$$

$$\boxed{i_2 = 1A}$$

$$1 = 10i_1 + 12$$

$$1 - 12 = 10i_1$$

$$\boxed{-\frac{11}{10} = i_1}$$

$$\text{power} = v_x(-i_1) = 0.5i_2(-i_1)$$

$$= 0.5(1)(-\frac{11}{10}) = \boxed{0.55W}$$

absorbing power