


UNIVERSITY OF UTAH
ELECTRICAL AND COMPUTER ENGINEERING DEPARTMENT

ECE 1270


HOMEWORK #5

Spring 2008

1.

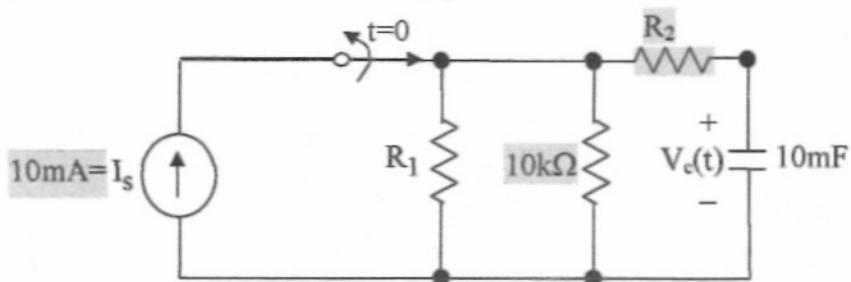

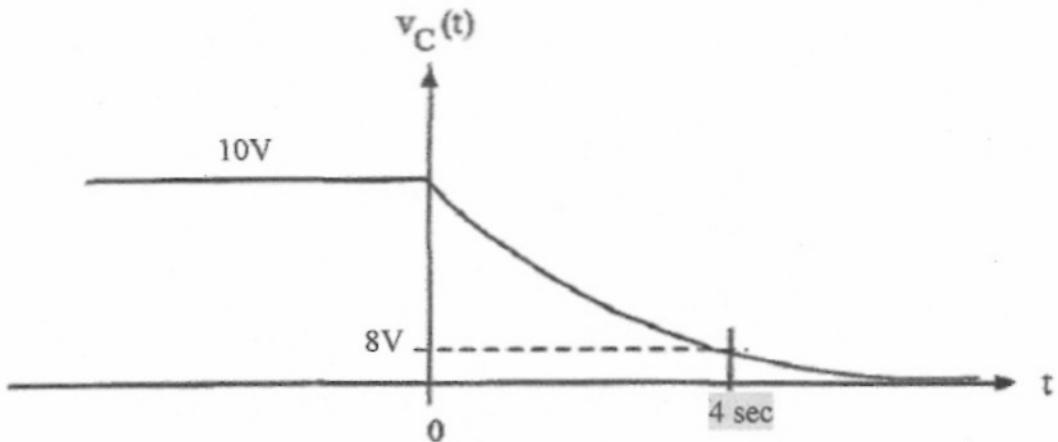
After being closed for a long time, the switch becomes open at $t=0$. Find R_1 and R_2 that give the following plot for $V_c(t)$:



Step 1. a. Draw circuit when switch is before $t=0$. This time is $t=0^-$.

$$V_{C1} = \frac{10m(10k)}{R_1 + 10k} = 10V$$

\uparrow from graph

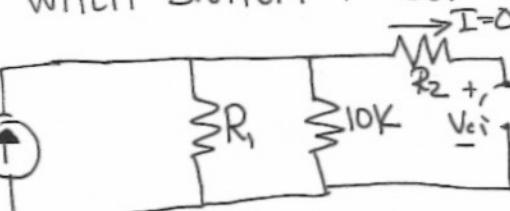


$$100 R_1 = R_1(10) + 10k(10)$$

$$R_1(100 - 10) = 10k(10) \Rightarrow R_1 \approx 1.11k\Omega$$

\cap is open because switch has been at this position for a long time.
 $\therefore i = C \left(\frac{dv}{dt} \right) = 0$
 $\therefore i = 0$ (looks like an open)

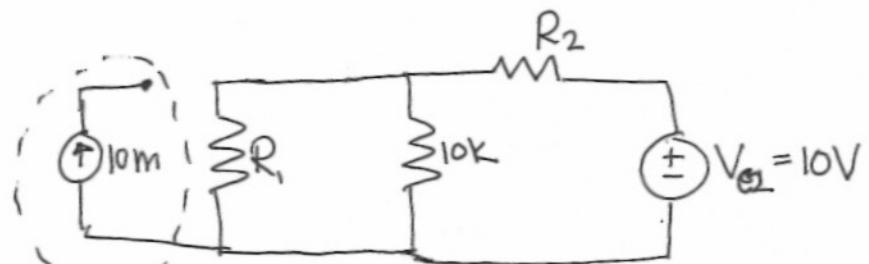Step 1. b. Draw circuit when switch just changes at $t=0$.
 This time is $t=0^+$. Find INITIAL CONDITION at this time.



voltage on capacitor
can not change
instantaneously!

- Irrelevant part of circuit

$$V_{c2} = V_{c1} = +10V$$

Step 2. Draw circuit when switch has changed. Time is $t=\infty$. Find FINAL VALUE. cap open again



because switch has been at
that position for a long
time $\Rightarrow i = C \frac{dy}{dt} = 0$

(no change in voltage over time)

$$V_{c3} = 0$$

$$Y = R_{eq} \cdot C = [R_2 + (1.11k \parallel 10k)]C = [R_2 + 999] \cdot C$$

Step 3. General equation \Rightarrow


$$V_c(t) = 10 e^{-t/(R_2+999)10m}$$

$$\text{From graph } \Rightarrow 8 = 10 e^{-4(R_210m+9.99)}$$

$$\ln \frac{8}{10} = \frac{-4}{(R_210m+9.99)}$$


$$R_210m + 9.99 = \left[\frac{-4}{\ln(\frac{8}{10})} - 9.99 \right] = \boxed{794 \Omega}$$

2.

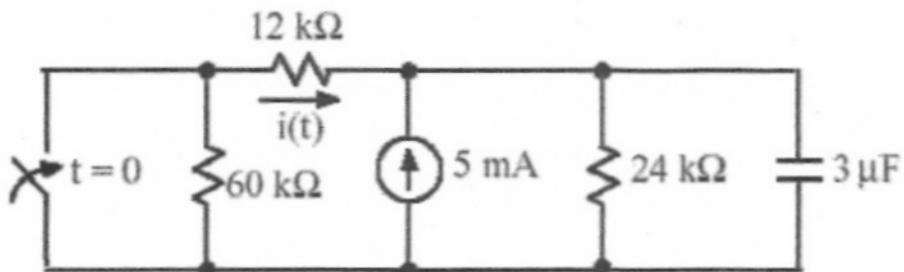


Step 1: After being open for a long time, the switch becomes closed at $t=0$. Find $i(t)$ for $t > 0$.

a. ($t=0^-$)

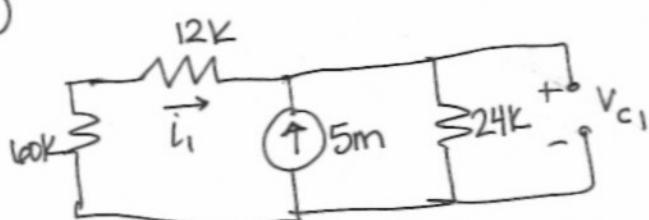

$$V_{C1} = \left[\frac{5m(72k)}{72k+24k} \right] 24k = 90V$$

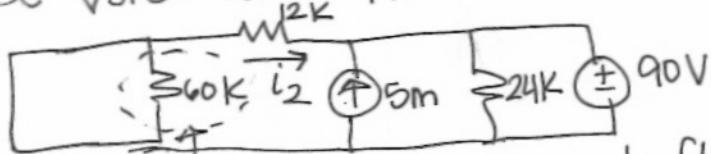b. ($t=0^+$) \leftarrow Find Initial Value at this time. (switch just changed, use V_{src} for cap) \Rightarrow




irrelevant: 0 current flow, 0 volts

Use Ohm's Law: polarity is opposite +90V supply

$$90 = -i_2(12k)$$

$$\therefore i_2 = -\frac{90}{12k} = 7.5mA \text{ (Initial condition)}$$

Step 2: ($t=\infty$)

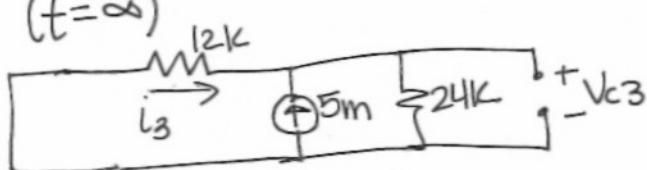

$$V_{C3} = \left[\frac{5m(12k)}{12k+24k} \right] 24k = 40V$$


$$i_3 = -\frac{5m(24k)}{3k} = -3.33mA \text{ Final}$$

$$\gamma = (24k||12k) \cdot 3\mu \approx 24m$$

$$t > 0, \quad i(t) = -3.33m + [7.5m - (-3.33m)] e^{-t/24m} \quad A$$


$$i(t) = -3.33m + 10.83m e^{-t/24m} \quad A$$

3.

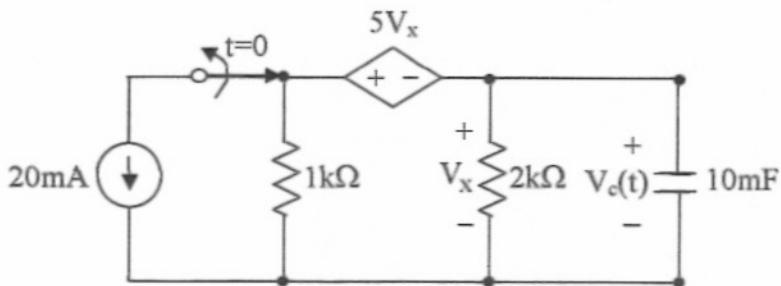

After the switch has been closed for a long time, it opens at $t=0$. Find $V_c(t)$ for $t > 0$.

Step 1a. ($t=0^-$)

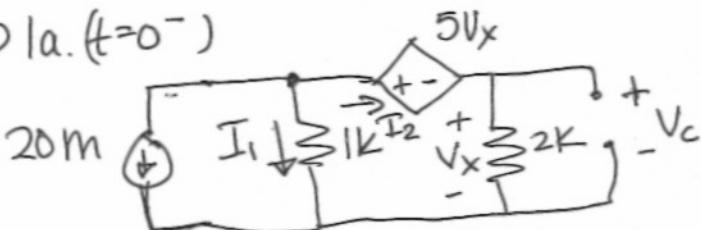

$$\Sigma I: +20m + I_1 + I_2 = 0 \Rightarrow I_1 = (-I_2 - 20m)$$


$$\text{V-loop: } +I_1(1K) - 5(I_2)(2K) - I_2(2K) = 0$$

$$-(I_2 1K) - 20m(1K) - 10K I_2 - I_2(2K) = 0$$

$$I_2(-13K) = 20 \Rightarrow I_2 = \frac{-20}{13K}$$

$$V_c = I_2(2K) = -\frac{40}{13}$$

Step 1b.

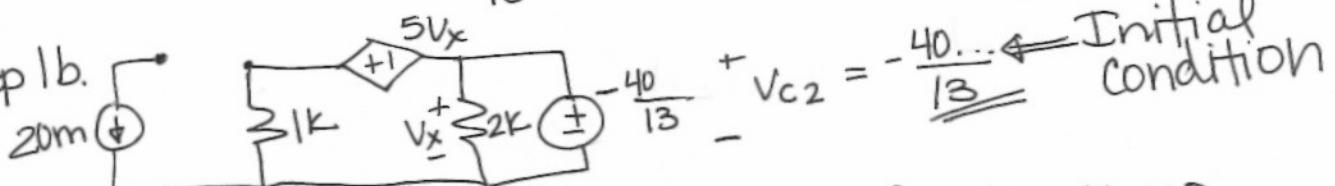

Step 2:




$\gamma \Rightarrow$ since $V_{c3}=0$, need to use test source

$$-I_1(1K) - 5V_x - V_x = 0$$

$$-I_1(1K) - 6(I_1(2K)) = 0$$

$$I_1 = 0 \quad \therefore V_{c3} = 0$$

Final value

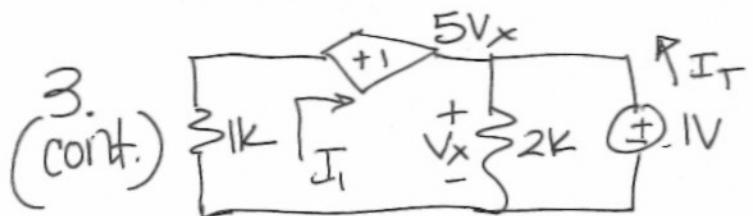

$$V_x = 1V$$

$$-I_1(1k) - 5(1) - 1 = 0$$

$$I_1 = \frac{-6}{1k} = -6mA$$

$$-I_1 + \frac{1}{2k} - I_T = 0$$

$$I_T = \frac{1}{2k} - (-6m) = 6.5m$$

$$R_{Th} = \frac{1V}{I_T} = \frac{1V}{6.5m} = 154\Omega$$


$$\gamma = (154)(10m) = 1.54$$

Step 3:

general eq: $t > 0, V_c(t) = 0 + \left[-\frac{40}{13} - 0 \right] e^{-t/1.54} V$


$t > 0, V_c(t) = -\frac{40}{13} e^{-t/1.54} V$

4.

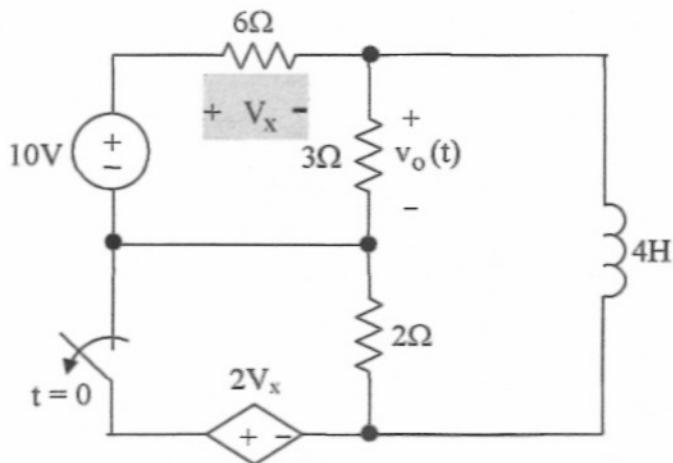

After the switch has been closed for a long time, it opens at $t=0$. Find the output voltage $v_o(t)$ for $t > 0$.

Step 1a. ($t=0^-$)

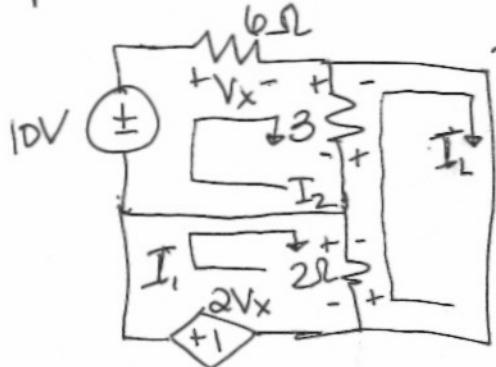

$$\textcircled{1} +2(I_2)(6) - I_1(2) + I_L(2) = 0$$

$$\textcircled{2} 2(I_1 - I_L) + 3(I_2 - I_L) = 0$$

$$\textcircled{3} +10 - I_2(6) + 3(I_L - I_2) = 0$$

Solve $\textcircled{3}$ for I_2 :

$$10 - 6I_2 - 3I_2 + 3I_L = 0$$

$$10 - 9I_2 + 3I_L = 0$$

$$\textcircled{4} I_2 = \frac{10 + 3I_L}{9}$$

plug $\textcircled{4}$ into $\textcircled{1}$

$$12\left(\frac{10}{9}\right) + 12\left(\frac{I_L}{3}\right) - I_1 2 + 2I_L = 0$$

$$6I_L + \frac{120}{9} = 2I_1$$

$$3I_L + \frac{60}{9} = I_1 \quad \textcircled{5}$$

plug $\textcircled{5}$ into $\textcircled{2}$


$$2\left(3I_L + \frac{60}{9}\right) - 2I_L + 3\left(\frac{10}{9}\right) + 3\left(\frac{3I_L}{9}\right) - 3I_L = 0$$

$$I_L\left(6 - 2 + 1 - 3\right) = -\frac{120}{9} - \frac{30}{9} = -\frac{150}{9}$$

$$I_L = \frac{-150}{9(2)} = -\frac{25}{3} \text{ A}$$

4. (cont.)

Step 1b. ($t=0^+$)

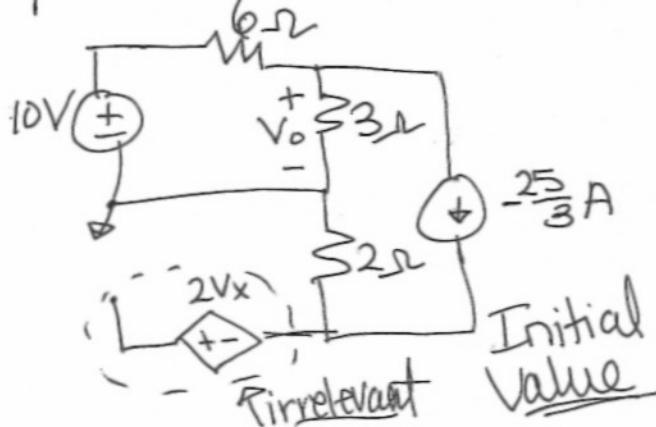

$$\frac{V_o}{6} + \frac{V_o}{3} + \left(-\frac{25}{3}\right) = 0$$


$$V_o \left(\frac{1}{6} + \frac{2}{3}\right) = \frac{25}{3} + \frac{5}{3} = \frac{30}{3}$$

$$V_o = \frac{30}{3} \cdot \frac{6}{3} = \frac{180}{9} V$$

$$V_o = 20 V$$

Initial Value

Step 2: ($t=\infty$)

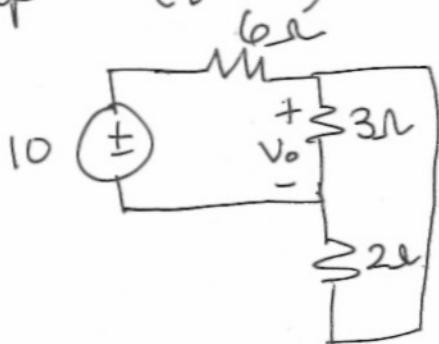

$$V_o = \frac{10(3||2)}{(3||2)+6} = \frac{5}{3} V \quad \text{Final Value}$$

$\gamma \Rightarrow$



$$R_{eq} = (3||6) + 2 = \frac{3(6)}{9} + 2$$

$$R_{eq} = 4 \Omega$$

$$\tau = R_{eq} = \frac{4}{4} = 1$$

$$t > 0, V_o(t) = \frac{5}{3} + [20 - \frac{5}{3}] e^{-t/1} V$$

$$V_o(t) = \frac{5}{3} + \frac{55}{3} e^{-t} V$$