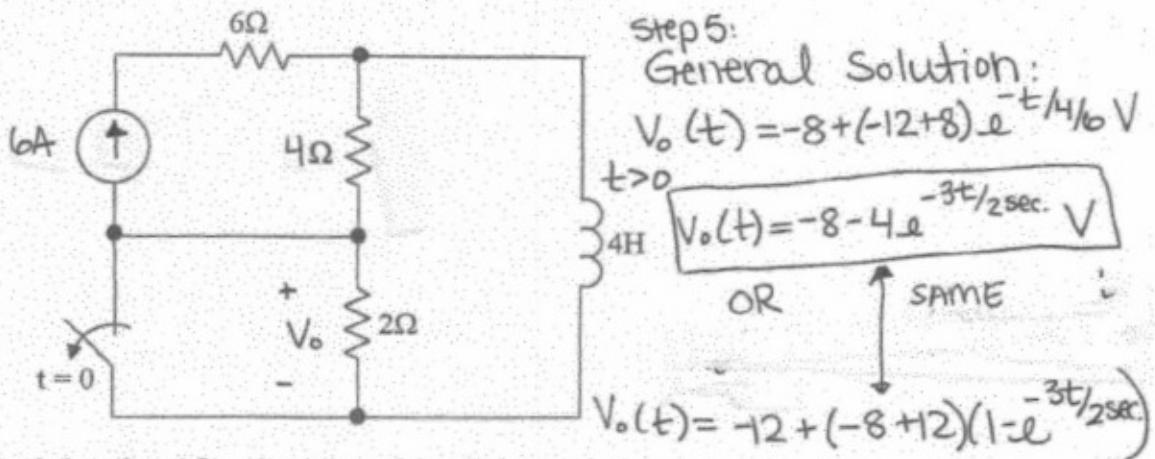


HW 6 Solution

Spring 2008




After being closed for a long time, the switch opens at $t = 0$.

1. Calculate the energy stored on the inductor as $t \rightarrow \infty$.

2. Write a numerical expression for $v_o(t)$ for $t > 0$.

(2) $t \rightarrow \infty$

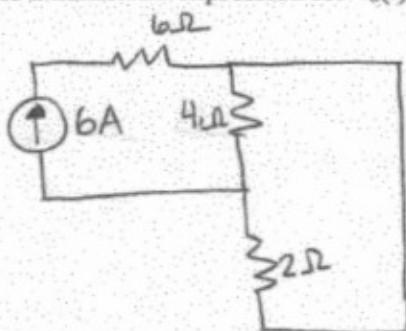


$$\textcircled{1} \quad i_L = \frac{6(4)}{(4+2)} = \frac{24}{6} = 4 \text{ A}$$

$$\cdot \text{energy} = \frac{1}{2} L i_L^2$$


$$w_L(t \rightarrow \infty) = \frac{1}{2}(4)(4)^2$$

$$= 32 \text{ J}$$


Step 1:
 $(t=0^-)$

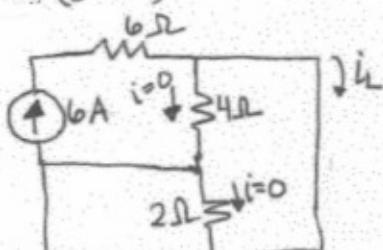


Step 2:
 $(t=0^+)$

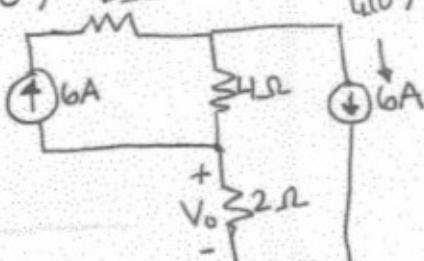


Step 3:

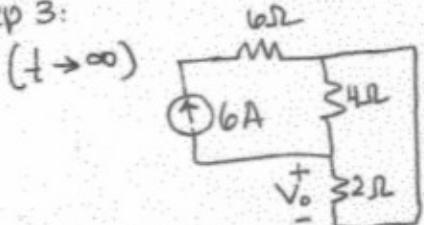

Step 4:

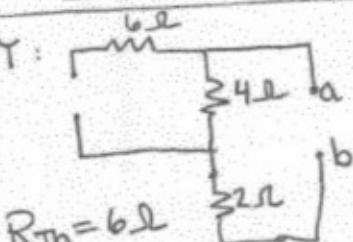


3.

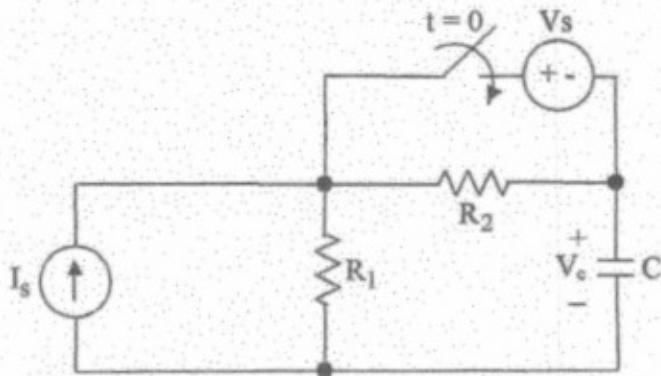


After being open for a long time, the switch closes at $t = 0$.

- Write an expression for $V_c(t = 0^+)$
- Write an expression for $V_c(t > 0)$ in terms of R_1 , R_2 , V_s , I_s , and C .

a. $(t = 0^-)$

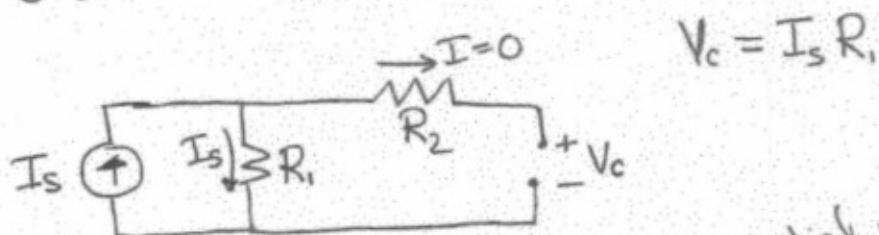
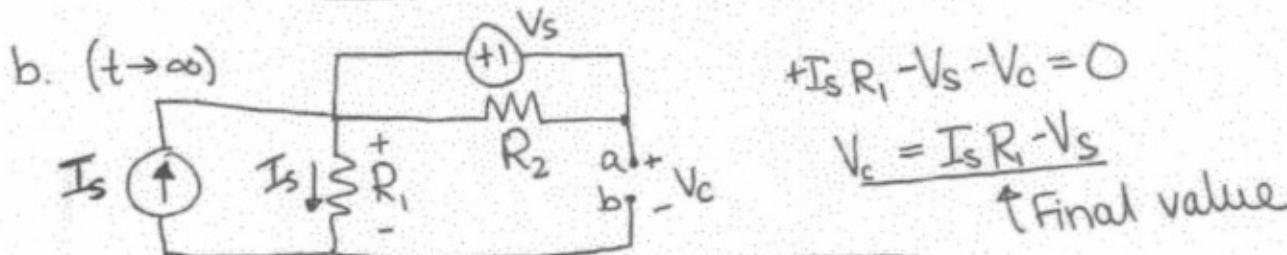
$$V_c(t = 0^-) = V_c(t = 0^+) = I_s R_1 \quad \text{Initial value}$$




$$+I_s R_1 - V_s - V_c = 0$$

$$V_c = I_s R_1 - V_s$$

Final value

$$\therefore R_{th} = R_1$$

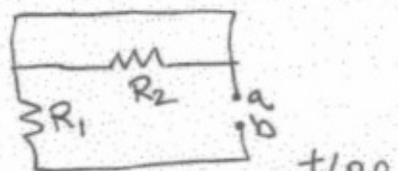


$$V_c(t > 0) = I_s R_1 - V_s + (I_s R_1 - I_s R_1 + V_s) e^{-t/R_{th}}$$

$$V_c(t > 0) = I_s R_1 - V_s + V_s e^{-t/R_{th}}$$


$$\text{OR } V_c(t > 0) = (I_s R_1) + [I_s R_1 - V_s - I_s R_1] (1 - e^{-t/R_{th}})$$

4.

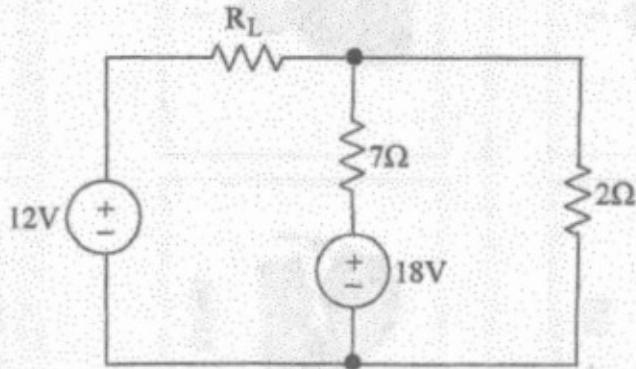

- a) Calculate the value of R_L that would absorb maximum power.
 b) Calculate that value of maximum power R_L could absorb.

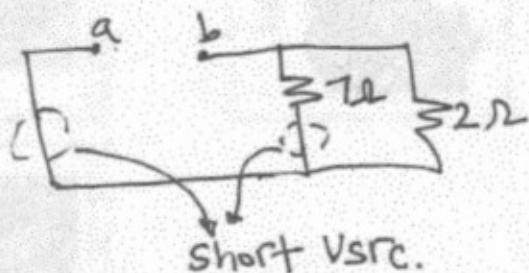
a. Maximum power achieved when $R_L = R_{Th}$



$$R_{Th} = R_L = 7\Omega \parallel 2\Omega$$

$$R_L = \frac{7(2)}{9} = \boxed{\frac{14}{9}\Omega}$$

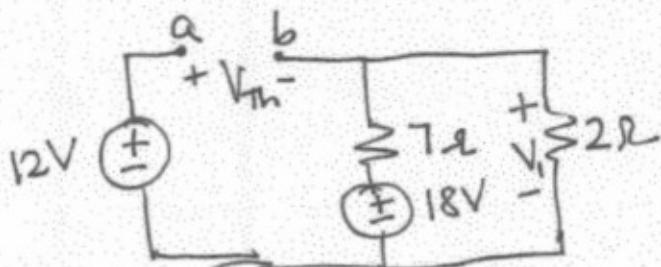b. maximum power = $\frac{V_{Th}^2}{4R_{Th}}$




$$V_1 = \frac{18(2)}{9} = 4V$$

$$+12 - V_{Th} - V_1 = 0$$

$$V_{Th} = 12 - 4 = 8V$$


$$\frac{V_{Th}^2}{4R_{Th}} = \frac{(8)^2}{4(\frac{14}{9})} \approx \boxed{10.3W}$$

5.

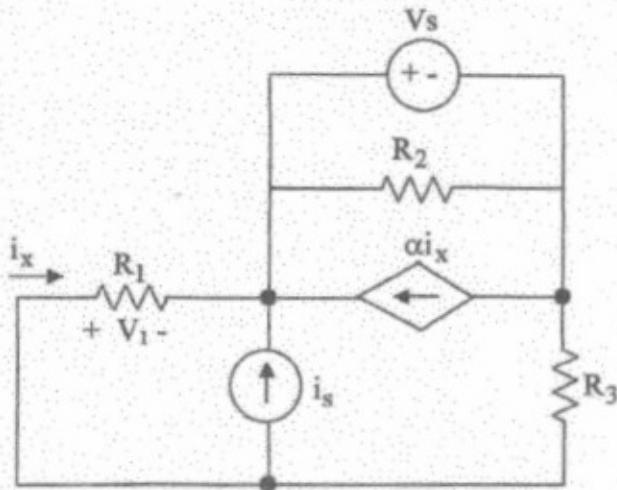

Using superposition, derive an expression for V_1 that contains no circuit quantities other than i_s , V_s , R_1 , R_2 , R_3 , and α , where $\alpha > 0$.


Case I: V_s on, i_s off ($i_s=0$)

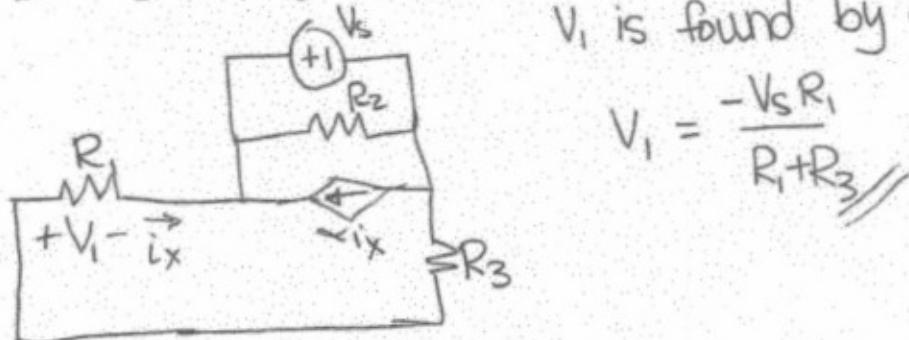

V_1 is found by a V-divider:

$$V_1 = \frac{-V_s R_1}{R_1 + R_3} //$$

Case II: V_s off ($V_s=0$), i_s ON

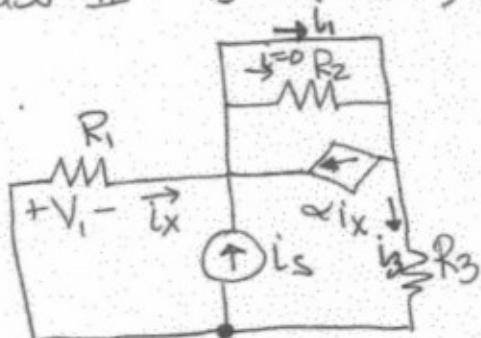

$$\begin{aligned} V_1 &= i_x R_1 \\ -i_3 + i_s + i_x &= 0 \\ i_3 &= (i_s + i_x) \end{aligned}$$

$$\begin{aligned} \text{V-loop: } -i_x R_1 - i_3 R_3 &= 0 \\ -i_x R_1 - i_s R_3 - i_x R_3 &= 0 \end{aligned}$$

$$i_x = -\frac{i_s R_3}{R_1 + R_3} \quad [\text{I-divider}]$$

Total = sum both cases

$$V_1 = \frac{-V_s R_1}{(R_1 + R_3)} + \frac{-i_s R_1 R_3}{R_1 + R_3}$$

$$\therefore V_1 = -\frac{i_s R_1 R_3}{R_1 + R_3}$$