

1. Solve the following simultaneous equations for i_1 , i_2 , and i_3 :

$$\text{Eq. 1} \quad 2(i_1 + i_2) - 10 + (3i_2 - i_1 - 4i_3) = 0$$

$$\text{Eq. 2} \quad -3(i_1 + i_2) + 2(i_1 + 3i_3) = 0$$

$$\text{Eq. 3} \quad i_1 - 5 - i_2 = 0$$

Solving Eq. 3 for $i_1 \Rightarrow$

$$i_1 = 5 + i_2$$

Plugging this result into Eq. 2 \Rightarrow

$$-3(5 + i_2) - 3i_2 + 2(5 + i_2) + 6i_3 = 0$$

$$-15 - 3i_2 - 3i_2 + 10 + 2i_2 + 6i_3 = 0$$

$$-5 - 4i_2 + 6i_3 = 0$$

{Solving for $i_3 \Rightarrow$ }

$$i_3 = \frac{+5+4i_2}{6}$$

Plugging this result into Eq. 1 \Rightarrow

$$2(5 + i_2) + 2i_2 - 10 + 3i_2 - 5 - i_2 - 4\left(\frac{+5+4i_2}{6}\right) = 0$$

$$+6\left(\frac{6}{6}\right)i_2 - 5\left(\frac{6}{6}\right) - \left(\frac{+20+16i_2}{6}\right) = 0$$

$$\left(\frac{20}{6}\right)i_2 - \left(\frac{+50}{6}\right) = 0$$

$$i_2 = \left(\frac{50}{6}\right)\left(\frac{6}{20}\right) = \boxed{2.5A}$$

$$i_3 = \frac{+5 + 4(2.5)}{6} = \boxed{2.5A}$$






$$i_3 = 5 + 2.5 = \boxed{7.5A}$$

2. Perform the following calculations. Write the answers with appropriate prefixes (such as μ , m , k etc.) for engineering units:

a) $P = 7.2 \text{ mA} \times 6 \text{ kV}$ (Note: $V^*A=W$) $= 7.2 \times 10^{-3} \times 6 \times 10^3 = \boxed{43.2W}$

b) $R = 3.3 \text{ k}\Omega + 1.6 \mu\Omega = 3300 + 0.0000016 = \boxed{3,300.0000016\Omega}$

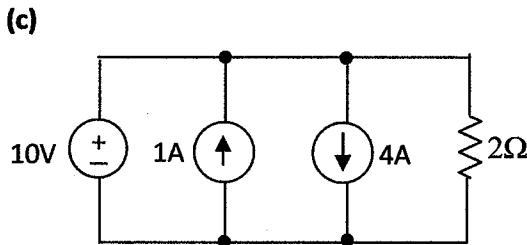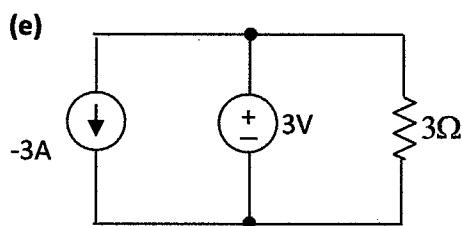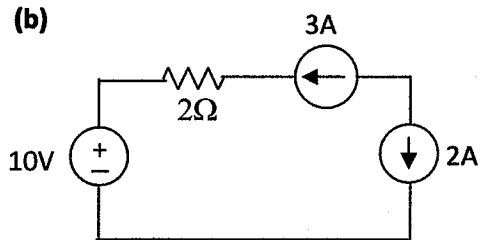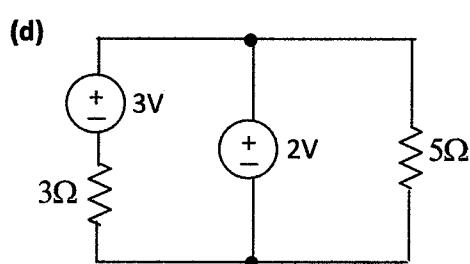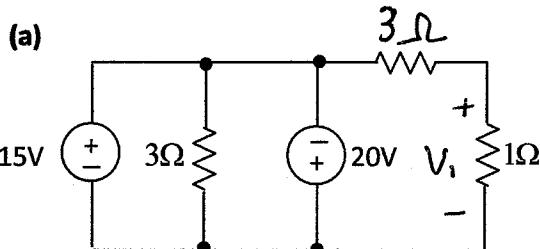3. Determine whether each of the following circuits is valid or invalid.



(a) This circuit is INVALID. By Kirchhoff's laws, components in parallel must have the same voltage drop across them. Here, the two voltage sources disagree across the 3Ω resistor.


(b) This circuit is INVALID. By Kirchhoff's laws components in series must carry the same current. The current sources disagree on the current and will try to force the current to have two different values: 3 A and 2 A.

(c) This circuit is VALID. Current sources in parallel sum. The voltage across both current sources and the 2Ω is 10V. Here, the current flowing through the 2Ω is $10/2=5A$. Summing the current will result in $-I_1-10V-1+4+5=0 \Rightarrow I_1+10V=8A$ flowing upward through the 10V voltage source. Note that current sources will produce whatever voltage is necessary to force a specified current flow in a circuit.

(d) This circuit is VALID. By Kirchhoff's laws, components in parallel must have the same voltage drop across them. Here, this is possible.

(e) This circuit is VALID. The 3Ω has $3/3=1A$ flowing downward through it. This means $+(-3)-I_1-3V+1=0$ gives $I_1-3V=-2A$ flowing through the voltage source (2A is flowing downward through the voltage source.)


4. Find I_x in the circuit below.

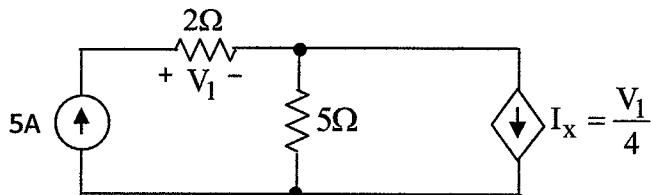

$$V_1 = 5A \cdot 2\Omega = 10V$$


$$I_x = V_1/4 = 10/4 = \boxed{2.5A}$$

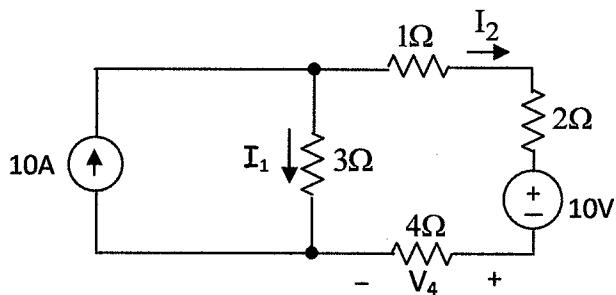5. Find I_2 in the circuit below if $V_4=8V$.



$$V_4 = 8V = I_2 \cdot 4\Omega \Rightarrow I_2 = 8/4\Omega = \boxed{2A}$$

Using a current summation at the top node: $-10 + I_1 + I_2 = 0 \Rightarrow I_1 = 10 - 2 = 8A$

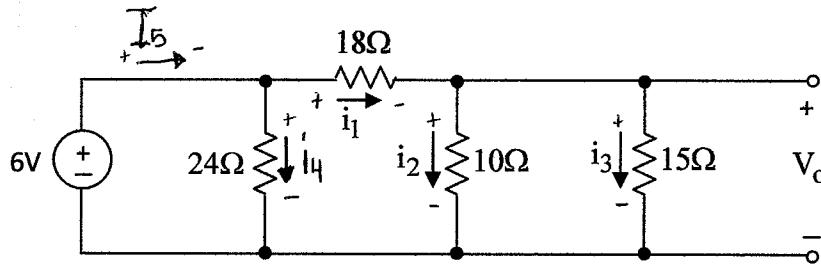9. (a) Find i_1 , i_2 , i_3 , and v_o .(b) Find the power dissipated in the 24Ω resistor and the power supply.

$$\text{KVL: } +6 - i_4(24) = 0 \Rightarrow i_4 = \frac{6}{24} = 250 \text{ mA}$$

$$+6 - i_1(18) - i_2(10) = 0$$

$$\textcircled{1} +6 - i_1(18) - i_3(15) = 0$$

$$+i_2(10) - i_3(15) = 0$$

$$+i_2(10) - V_o = 0$$

$$+i_3(15) - V_o = 0$$

$$+i_4(24) - i_1(18) - i_2(10) = 0$$

$$+i_4(24) - i_1(18) - i_3(15) = 0$$

$$\therefore V_o = i_2(10) \text{ or } V_o = i_3(15)$$

$$i_2(10) = i_3(15)$$

$$i_2 = i_3 \left(\frac{3}{2}\right)$$

Using $\textcircled{1}$ and $\textcircled{2}$:

$$+6 - i_3 \left(\frac{5}{2}\right) 18 - i_3(15) = 0$$

$$+6 = \left[\frac{18(5) + 30}{2} \right] i_3$$

$$\frac{12}{120} = \begin{cases} i_3 = 100 \text{ mA} \\ i_1 = \frac{5}{2}(100 \text{ mA}) = 250 \text{ mA} \\ i_2 = \frac{3}{2}(100 \text{ mA}) = 150 \text{ mA} \\ V_o = i_2(10) = 1.5 \text{ V} \end{cases}$$

KCL:

$$-i_1 + i_2 + i_3 = 0$$

$$-i_1 + i_3 \left(\frac{3}{2}\right) + i_3 \left(\frac{3}{2}\right) = 0$$

$$\textcircled{2} i_1 = \frac{5}{2} i_3$$

(b) 24Ω power:

$$P = I \cdot V = I^2 R$$

$$I_{24\Omega} = i_4 = 250 \text{ mA}$$

$$\therefore P_{24\Omega} = (250 \text{ mA})^2 \cdot 24$$

$$P_{24\Omega} = 1.5 \text{ W}$$

power supply power:

$$\begin{matrix} \oplus 6V & I_5 \\ \text{---} & \text{---} \end{matrix} \quad P = (-) I \cdot V$$

signs are opposite


$$-I_5 + i_4 + i_1 = 0$$

$$I_5 = 250 \text{ mA} + 250 \text{ mA} = 500 \text{ mA}$$

$$P_{6V} = -500 \text{ mA} (6) = \boxed{-3 \text{ W}}$$


Summer 2009
(Dr. Cotter)

7.

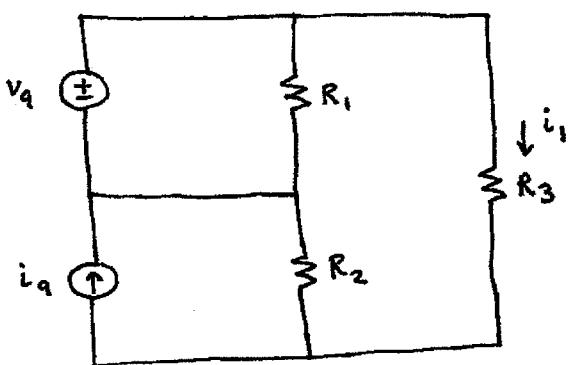

Derive expression for i_1 . Expression must contain no other parameters than V_a , i_a , R_1 , R_2 , R_3 .

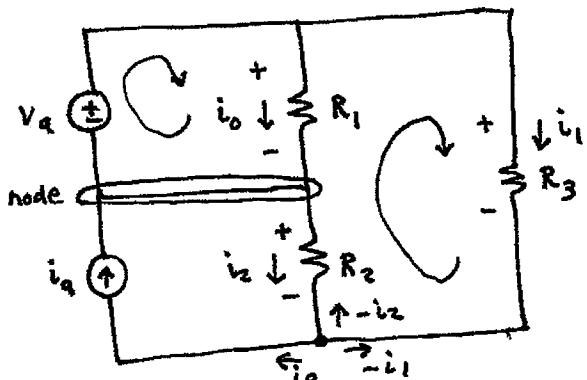sol'n: Use Kirchhoff's Laws. Label resistors.



We'll use Ohm's Law as we go by writing voltages for R 's as $v = iR$.

voltage loops:

$$\text{Upper left loop } +V_a - i_0 R_1 = 0V$$

$$\text{We can solve this. } i_0 = \frac{V_a}{R_1}$$

$$\text{Right side loop } +i_2 R_2 + i_0 R_1 - i_1 R_3 = 0V \quad (1)$$

These are the only v -loops that are allowed, (i.e., no v needed for i src), and are not redundant, (i.e., are not bigger loops equivalent in content to several smaller loops).

Summer 2009
(Dr. Cotter)

sol'n

Sol'n: cont.

current sums at nodes:

The only node where we can sum currents (without having to define a current for a voltage source) is the bottom node.

$$\text{Bottom node } i_q - i_2 - i_1 = 0 \text{ A} \quad (2)$$

Now we have the last two eqns in two unknowns that we can solve for i_1 .

Solve eqn (1) for i_2 so we can eliminate it.

$$i_2 = \frac{i_1 R_3 - i_q R_1}{R_2} = i_1 R_3 - \frac{i_q R_1}{R_2}$$

$$\text{or } i_2 = \frac{i_1 R_3 - V_q}{R_2}$$

Substitute this into eqn (2); solve for i_1 .

$$i_1 = i_q - i_2 = i_q - \frac{i_1 R_3 - V_q}{R_2}$$

$$i_1 + i_1 \frac{R_3}{R_2} = i_q + \frac{V_q}{R_2}$$

$$i_1 \left(1 + \frac{R_3}{R_2}\right) = i_q + \frac{V_q}{R_2}$$

$$i_1 \frac{R_2 + R_3}{R_2} = i_q + \frac{V_q}{R_2}$$


$$i_1 = \left(i_q + \frac{V_q}{R_2}\right) \frac{R_2}{R_2 + R_3}$$

$$i_1 = \frac{i_q R_2 + V_q}{R_2 + R_3}$$

Summer 2009
(Dr. Cotter)

8.

sol'n

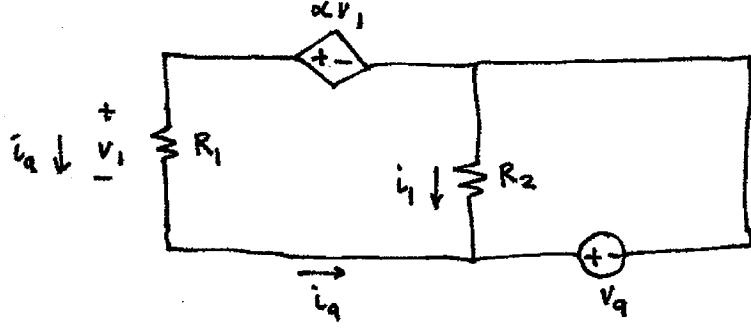

- a. Derive expression for i_a containing not more than circuit parameters α, V_a, R_1, R_2 .

sol'n: a) Use Kirchhoff's Laws. We can save effort by observing that V_a is across two circuits that we may solve separately: R_2 is the first circuit, and R_1 and αV_1 src are the other circuit.

We may thus ignore R_2 , and we may use an outer V -loop.

(We use $i_q R_1$ to replace v_1 everywhere.)

$$+i_q R_1 - \alpha(i_q R_1) + v_q = 0V$$

$\underbrace{v_1}_{V_1}$

$$\text{or } i_q (R_1 - \alpha R_1) = -V_q$$

or

$$i_q = \frac{-V_q}{(1-\alpha) R_1}$$

Summer 2009
(Dr. Cotter)

sol'n

sol'n: 8. (Example) A consistency check means we pick values for components that make the circuit so simple that we can solve it by inspection. We then check our answer to (a) against the simple sol'n.

Many checks are possible. This is only one possible check.

Let $\alpha=0$ so dependent v-src becomes OR (or wire).

Then $-v_q$ is across R_1 . Thus, $i_q = \frac{-v_q}{R_1}$.

We let $R_1 = 1\Omega$, $R_2 = 2\Omega$, $v_q = 12V$.

Then $i_q = \frac{-12V}{1\Omega} = -12A$.


Now we see if our formula from (a) gives this answer.

$$i_q = \frac{-v_q}{(1-\kappa) R_1} = \frac{-12V}{(1-0) 1\Omega} = -12A \checkmark$$

Agrees with answer from simplified circuit.


Note: this check can catch a problem although it doesn't guarantee correctness if the sol'n to (a) passes the test.

9.

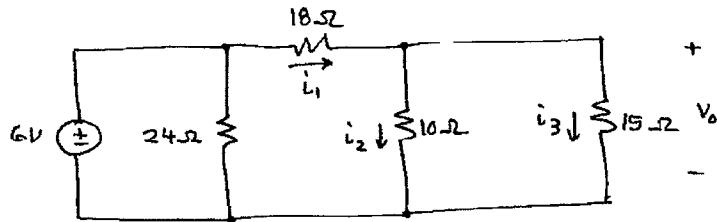


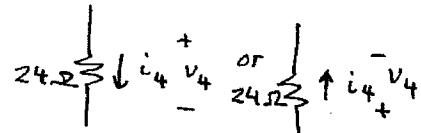- a. Calculate i_1, i_2, i_3, V_o .
 b. Find power dissipated in the 24Ω resistor and the 6V supply.

sol'n: a) using passive sign convention, label all currents and voltage drops. Note that we have two choices for the labeling of the 24Ω resistor:



I'll use the first labeling:

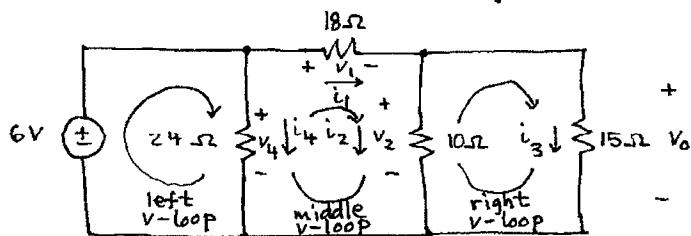

Write eqns for voltage loops for inner loops
(unless that would force us to define a voltage for a current source).

$$\text{Left } v\text{-loop: } +6V - V_4 = 0V \Rightarrow V_4 = 6V$$

Makes sense since 24Ω resistor is across 6V source (battery).

$$\text{Ohm's Law: } i_4 = \frac{V_4}{24\Omega} = \frac{6V}{24\Omega} = \frac{1}{4} A \text{ or } 250 \text{ mA}$$

$$\text{Middle } v\text{-loop: } +V_4 - V_1 - V_2 = 0V$$

of course, $V_4 = 6V$. So

$$V_1 + V_2 = V_4 = 6V$$

sol'n: 9.a) cont.

$$\text{Right } V\text{-loop: } +v_2 - v_0 = 0V \Rightarrow v_0 = v_2$$

Now write eqns for current sums at nodes.

We do all but one node, (one is always redundant), unless we would have to define a current for a voltage source. In that case, we can skip that node.

Here, we observe that we can skip the node to left of the 18Ω resistor. (We don't want to define a current for the $6V$ source.)

For the node to the right of the 18Ω resistor, we sum currents measured in a direction away from the node:

$$-i_1 + i_2 + i_3 = 0A$$

We leave out one node, and I usually leave out the bottom rail. By the way, the two bottom nodes are connected by a wire so they are really just one node. (Redraw circuit so everything is connected to one point on the bottom.)

We are done with Kirchhoff's Laws. Now use Ohm's Law for all resistors: (already did 24Ω)

$v_1 = i_1 \cdot 18\Omega$
$v_2 = i_2 \cdot 10\Omega$
$v_0 = i_3 \cdot 15\Omega$

We have 6 eqns in 6 unknowns, (boxed eqns).

sol'n: 9.a) cont.

One way to proceed is to replace all v's with i·R's:

$$i_1 \cdot 18\Omega + i_2 \cdot 10\Omega = 6V \quad \text{eq'n \#1}$$

$$i_3 \cdot 15\Omega = i_2 \cdot 10\Omega \quad \text{eq'n \#2}$$

$$-i_1 + i_2 + i_3 = 0A \quad \text{eq'n \#3}$$

Solve the simultaneous eq'n's. I use the simplest eq'n first to isolate one variable in terms of others. Eq'n (2) tells us what to substitute for i_3 : $i_3 = i_2 \cdot \frac{10\Omega}{15\Omega} = \frac{2}{3} i_2$

Using this for i_3 in eq'n's (1) and (3) gives

$$i_1 \cdot 18\Omega + i_2 \cdot 10\Omega = 6V$$

$$-i_1 + i_2 + \frac{2}{3} i_2 = 0A \quad \text{or} \quad -i_1 + i_2 \left(1 + \frac{2}{3}\right) = 0A$$

From this new eq'n (2) we have $i_1 = i_2 \left(1 + \frac{2}{3}\right) = \frac{5}{3} i_2$.

Eq'n (1) becomes $\frac{5}{3} i_2 \cdot 18\Omega + i_2 \cdot 10\Omega = 6V$

$$\text{or} \quad i_2 \cdot \left(\frac{5}{3} \cdot 18 + 10\right)\Omega = 6V$$

$$i_2 \cdot 40\Omega = 6V$$

$$i_2 = \frac{6V}{40\Omega} = \frac{6V}{40\Omega \cdot 25} = \frac{150}{1k} \frac{V}{\Omega}$$

$$i_2 = 150 \text{ mA}$$

Substitute back into eq'n (1) to get

$$i_1 \cdot 18\Omega + 150 \text{ mA} \cdot 10\Omega = 6V$$

$$i_1 \cdot 18\Omega + 1.5V = 6V$$

$$i_1 \cdot 18\Omega = 4.5V$$

$$i_1 = \frac{4.5V}{18\Omega} = \frac{1}{4} A \text{ or } 250 \text{ mA}$$

sol'n: 9.a) cont. Using eq'n (2), we have $i_3 \cdot 15\Omega = 150\text{mA} \cdot 10\Omega$.

$$i_3 = \frac{1.5V}{15\Omega} = \frac{1}{10} A \text{ or } 100 \text{ mA}$$

By Ohm's Law, $v_o = i_3 \cdot 15\Omega = 100 \text{mA} \cdot 15\Omega = 1.5V$.

Summary:	$i_1 = 250 \text{ mA}$	$i_4 = 250 \text{ mA}$
	$i_2 = 150 \text{ mA}$	
	$i_3 = 100 \text{ mA}$	
	$v_o = 1.5V$	

Consistency checks:

Outer v-loop correct?

$$+6V - V_1 - V_o \stackrel{?}{=} 0$$

$$+6V - 250\text{mA} \cdot 18\Omega - 100\text{mA} \cdot 15\Omega \stackrel{?}{=} 0$$

$$+6V - 4.5V - 1.5V = 0 \checkmark \text{ works!}$$

Current flowing into upper right node equals current flowing out of upper right node?

$$\text{Current flowing in} = i_1 = 250 \text{ mA}$$

$$\begin{aligned} \text{Current flowing out} &= i_2 + i_3 = 150\text{mA} + 100\text{mA} \\ &= 250 \text{ mA} \checkmark \text{ works!} \end{aligned}$$

b) $P = i \cdot v$ (value > 0 means power dissipated
value > 0 " " generated or sourced)

For resistors, $P = i \cdot v = i \cdot iR = i^2 R$ by Ohm's Law
 $= \frac{v}{R} \cdot v = \frac{v^2}{R}$ " " "

Thus, we can find P as $i^2 R$ or $\frac{v^2}{R}$ for R's.

$$P_{24\Omega} = i_4^2 \cdot 24\Omega = (\frac{1}{4}A)^2 \cdot 24\Omega = \frac{1}{16} \cdot 24 \text{ W} = 1.5 \text{ W}$$

$$P_{18\Omega} = i_1^2 \cdot 18\Omega = (\frac{1}{4}A)^2 \cdot 18\Omega = \frac{1}{16} \cdot 18 \text{ W} = 1.125 \text{ W}$$

$$P_{10\Omega} = i_2^2 \cdot 10\Omega = (\frac{1.5}{10}A)^2 \cdot 10\Omega = \frac{2.25}{100} \cdot 10 \text{ W} = 225 \text{ mW}$$

$$P_{15\Omega} = i_3^2 \cdot 15\Omega = (\frac{1}{10}A)^2 \cdot 15\Omega = \frac{100}{15} \text{ W} = 150 \text{ mW}$$

sol'n: q. 6) cont. Now we need the current for the 6V source:

$$6V \text{ } \oplus \downarrow i \quad P = i \cdot 6V$$

we avoided defining i earlier. Now that we have found all the other i 's and v 's, we can find i .

use a current sum at the node to the left of the 18Ω: $i + i_4 + i_1 = 0A$

$$i + 250\text{mA} + 250\text{mA} = 0A$$

$$i = -500\text{mA} \text{ or } -\frac{1}{2}A$$


$$P_{6V} = i \cdot 6V = -\frac{1}{2}A \cdot 6V = -3W \quad (\text{negative means pwr source})$$

Consistency check:

Total pwr for all components should be zero:

$$-3W + 1.5W + 1.125W + 225\text{mW} + 150\text{mW} = 0W \checkmark \text{ works!}$$

10.

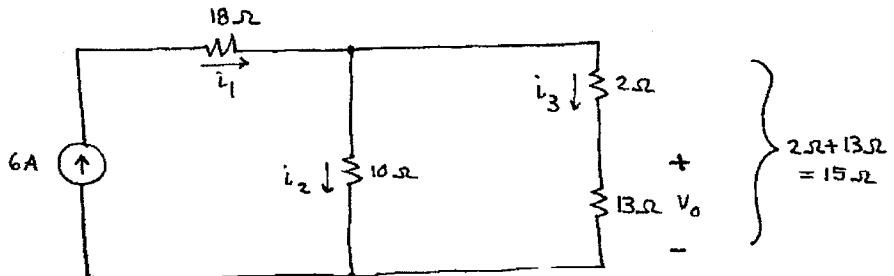Find i_1 , i_2 , i_3 , and V_0 .

sol'n: Since 18Ω in series with $6A$ source, we must have $i_1 = 6A$. This is total i for right side.

Now we can use i -divider formula for the two branches on right:

$$i_2 = i_1 \cdot \frac{15\Omega}{10\Omega + 15\Omega} = i_1 \cdot \frac{3}{5} = 6A \cdot \frac{3}{5} = 3.6A$$

$$i_3 = i_1 \cdot \frac{10\Omega}{10\Omega + 15\Omega} = i_1 \cdot \frac{2}{5} = 6A \cdot \frac{2}{5} = 2.4A$$

To find V_0 , we observe that i_3 flows thru 13Ω resistor. Thus, $V_0 = i_3 \cdot 13\Omega = 2.4A \cdot 13\Omega$
 $= \frac{12}{5}A \cdot 13\Omega = \frac{156}{5}V = 31.2V$

Summary: $i_1 = 6A$

$i_2 = 3.6A$

$i_3 = 2.4A$

$V_0 = 31.2V$

Consistency checks: $i_1 = ?$ $i_2 + i_3 = 6A = 3.6A + 2.4A$ ✓

$i_2 \cdot 10\Omega = ?$ $i_3 \cdot 15\Omega = 3.6A \cdot 10\Omega = 2.4A \cdot 15\Omega$ ✓

$$\underbrace{i_3 \cdot 13\Omega}_{V_0} + i_3 \cdot 2\Omega = ?$$

$$31.2V + 2.4A \cdot 2\Omega = ?$$

$$31.2V + 4.8V = 36V$$