

1. Solve the following simultaneous equations for i_1 , i_2 , and i_3 :

$$5(i_1 + i_2) + (2i_2 - i_3 - 4i_3) - 20 = 0$$

$$-3(i_1 + i_2) + 2(3i_3) = 0$$






$$-5 + i_1 - 2i_2 = 0$$

2. Perform the following calculations. Write the answers with appropriate prefixes (such as μ , m, k etc.) for engineering units:


a) $P = 5 \mu\text{A} \times 6 \text{GV}$ (Note: $V \cdot A = W$)

b) $R = 5.1 \text{k}\Omega + 160\Omega$

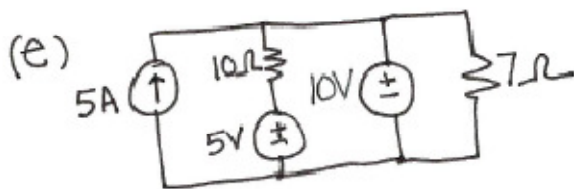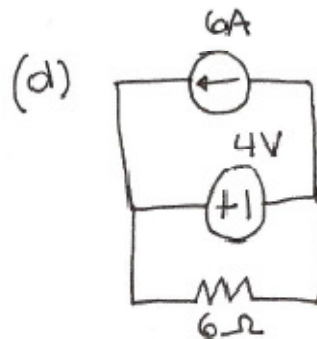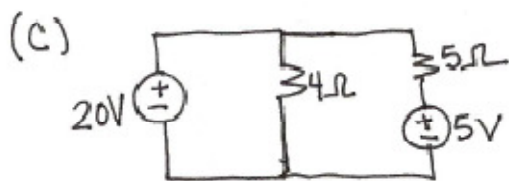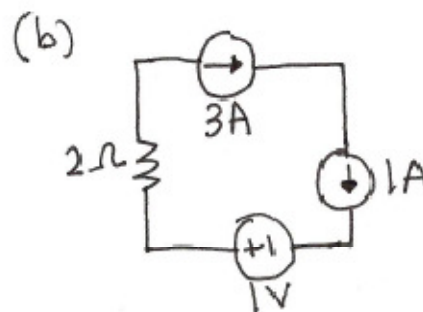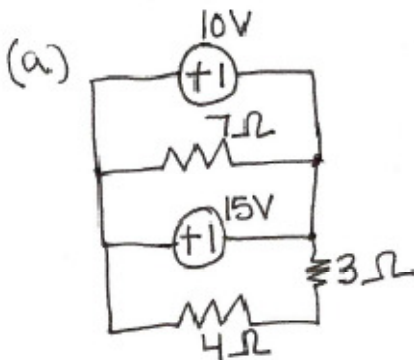
3. Determine whether each of the following circuits is valid or invalid.



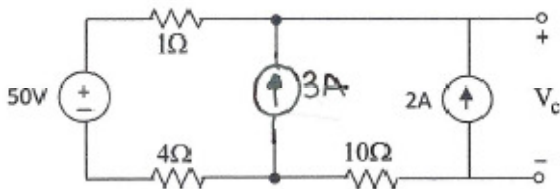
4. Use Kirchoff's laws and Ohm's Law to find the value of V_c . Note that it is also the voltage across the **2A** current source.



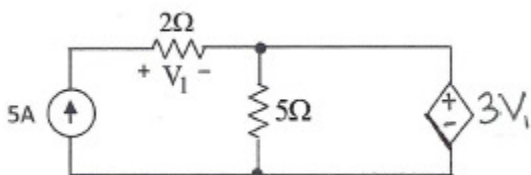
5. Use Kirchoff's laws and Ohm's Law to find the current through the 5Ω resistor. The current source is not ideal and so will have a voltage drop across it.



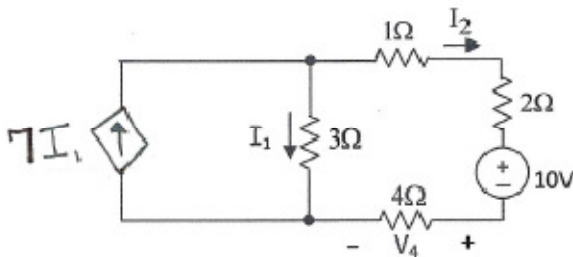
6. Use Kirchoff's laws and Ohm's Law to find I_2 and V_4 in the circuit below.



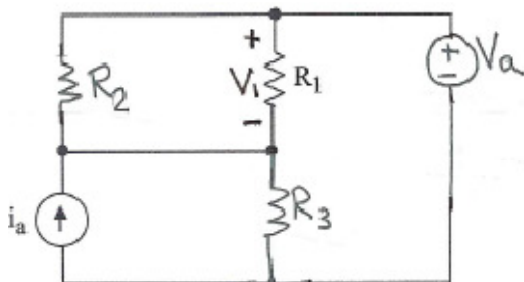
7. Use Kirchoff's laws and Ohm's Law to find the expression for V_1 . The expression can contain no other parameters than V_a , i_a , R_1 , R_2 , and/or R_3 .



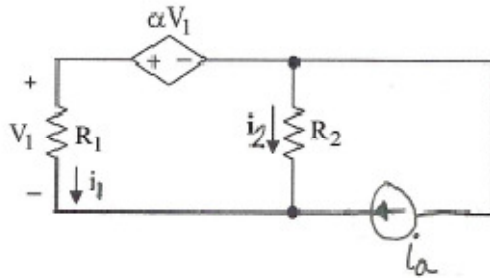8. Use Kirchoff's laws and Ohm's Law to find the expression for i_1 . The expression can contain no other parameters than i_a , α , R_1 , and/or R_2 . (Hint: Eliminate V_1 from the expression)



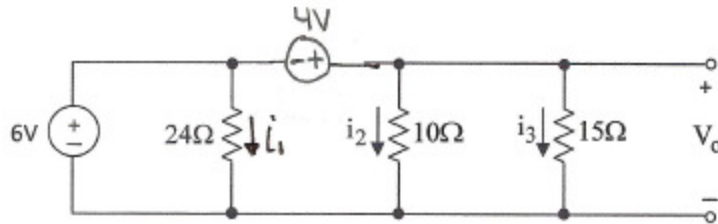9. (a) Find i_1 , i_2 , i_3 , and v_o .
 (b) Find the power dissipated in the 24Ω resistor and the power supply.



10. Find i_1 , i_2 , i_3 , and v_o .

