

1. Solve the following simultaneous equations for  $i_1$ ,  $i_2$ , and  $i_3$ :

$$\textcircled{1} \quad 5(i_1 + i_2) + (2i_2 - i_3 - 4i_3) - 20 = 0$$

$$\textcircled{2} \quad -3(i_1 + i_2) + 2(3i_3) = 0$$

$$\textcircled{3} \quad -5 + i_1 - 2i_2 = 0$$

Rearranging  $\textcircled{1}$ :

$$5i_1 + 5i_2 + 2i_2 - i_3 - 4i_3 - 20 = 0$$

$$5i_1 + 7i_2 - 5i_3 - 20 = 0$$

Solving  $\textcircled{2}$  for  $i_2$ :

$$-3i_1 - 3i_2 + 6i_3 = 0$$

$$3i_2 = \frac{(-3i_1 + 6i_3)}{3} \Rightarrow i_2 = -i_1 + 2i_3 \textcircled{2}$$

Solving  $\textcircled{3}$  for  $i_1$  and plugging into  $\textcircled{2}$ :

$$-5 + i_1 - 2i_2 \Rightarrow i_1 = 2i_2 + 5 \textcircled{3}$$

into  $\textcircled{2}$ :

$$i_2 = -2i_2 - 5 + 2i_3 \Rightarrow 3i_2 = \frac{(-5 + 2i_3)}{3} \textcircled{4} \quad \{\textcircled{4} \rightarrow \textcircled{3}\}$$

$$\therefore i_1 = -\frac{10}{3} + \frac{4}{3}i_3 + 5 \textcircled{5}$$

[Now eq.  $\textcircled{4}$  gives  $i_2$  in terms of  $i_3$  &  $\textcircled{5}$  gives  $i_1$  in terms of  $i_3$ ]  $\rightarrow$  usually try to put eq. in terms of 1 unknown  
plug  $\textcircled{4}$ ,  $\textcircled{5}$  into  $\textcircled{1}$

$$5\left(-\frac{10}{3} + \frac{4}{3}i_3 + 5\right) + 7\left(-\frac{5}{3} + \frac{2}{3}i_3\right) - 5i_3 - 20 = 0$$

$$i_3\left(\frac{20}{3} + \frac{14}{3} - \frac{15}{3}\right) = \frac{60}{3} + \frac{35}{3} - \frac{25(3)}{3} + \frac{50}{3}$$

problem #1 (cont.)

$$i_3 \left( \frac{34-15}{3} \right) = \frac{(60+35-75+50)}{3}$$

$$i_3 \left( \frac{19}{3} \right) = \left( \frac{70}{3} \right) \Rightarrow i_3 = \left( \frac{70}{3} \times \frac{3}{19} \right) = \boxed{\frac{70}{19} \text{ A}} \approx (3.7)$$

use in (4):

$$i_2 = -\frac{5}{3} + \frac{2}{3} \left( \frac{70}{19} \right) = \frac{\overbrace{-5(19)}^{-95} + 2(70)}{3(19)} = \boxed{\frac{45}{57} \text{ A}} \approx (0.8)$$

use in (5):

$$i_1 = -\frac{10}{3} + \frac{4}{3} \left( \frac{70}{19} \right) + \frac{15}{3} = \frac{\overbrace{5(19)}^{95} + \overbrace{4(70)}^{280}}{3(19)} = \boxed{\frac{375}{57} \text{ A}} \approx (6.6)$$

check:

$$\text{eq. (3)} \quad -5 + 6.6 - 1.6 = 0 \quad \checkmark$$

$$\text{eq. (2)} \quad -3(6.6 + 0.8) + 6(3.7) = 0 \\ -22.2 + 22.2 = 0 \quad \checkmark$$






$$\text{eq. (1)} \quad 5(6.6 + 0.8) + (2(8) - 3.7 - 4(3.7)) - 20 = 0 \\ 37 + 1.6 - 3.7 - 14.8 - 20 = 0 \quad \checkmark$$

2. Perform the following calculations. Write the answers with appropriate prefixes (such as  $\mu$ , m, k etc.) for engineering units:


a)  $P = 5 \mu\text{A} \times 6 \text{GV}$  (Note:  $V \cdot A = W$ ) =  $5 \times 10^{-6} \cdot 6 \times 10^9 = \boxed{30 \text{KW}}$

b)  $R = 5.1 \text{k}\Omega + 160 \Omega = 5,100 + 160 = \boxed{5,260 \Omega \text{ or } 5.26 \text{k}\Omega}$

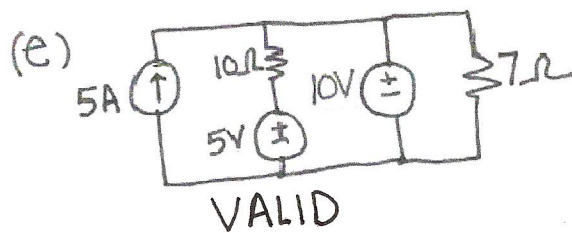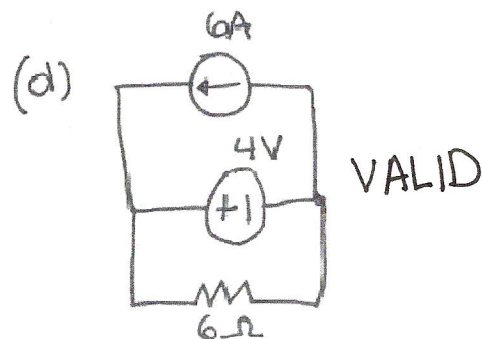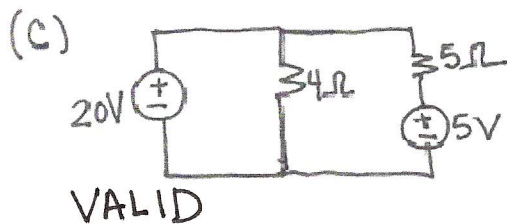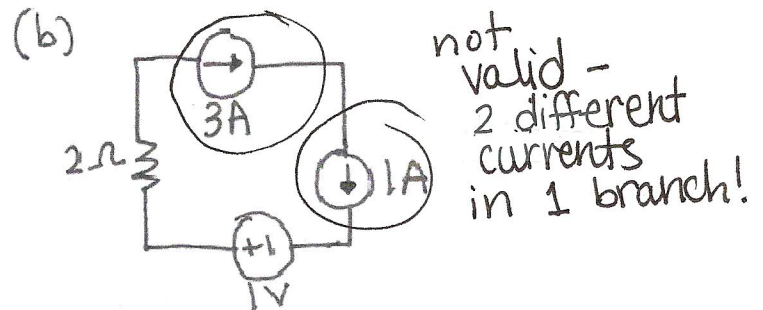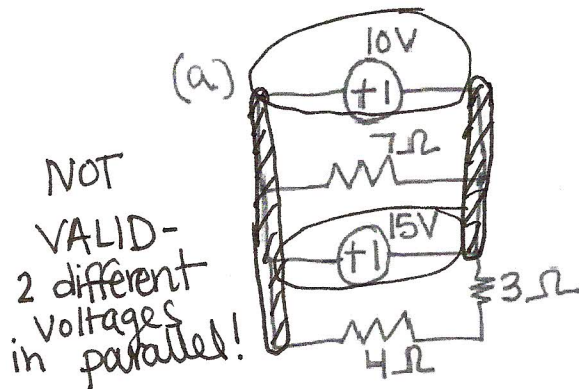3. Determine whether each of the following circuits is valid or invalid.



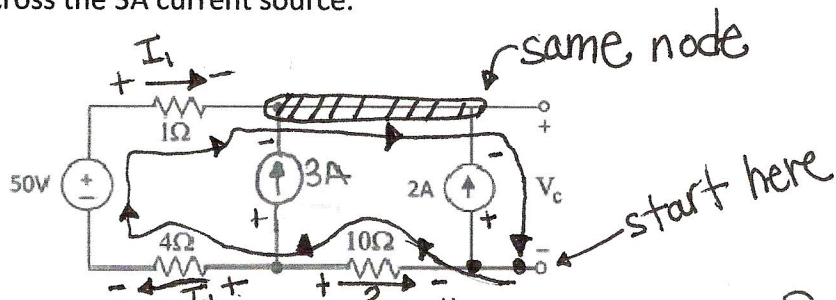4. Use Kirchoff's laws and Ohm's Law to find the value of  $V_c$ . Note that it is also the voltage across the 3A current source.



1. Label a current through every R.

2. Take a current summation at top node:

$$-I_1 - 3 - 2 = 0$$


$$I_1 = -5A$$

3. Take a voltage loop (note:

$$+2(10) - 4(I_1) + 50 - \underbrace{I_1(1)}_{\text{across } 1\Omega} - V_c = 0$$

$$\therefore V_c = 20 - 20 + 50 + 5 = \boxed{55V}$$

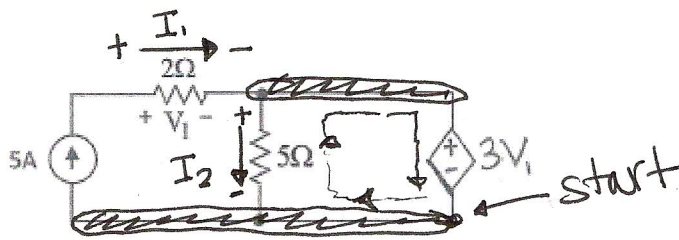5. Use Kirchoff's laws and Ohm's Law to find the current through the  $5\Omega$  resistor. The current source is not ideal and so will have a voltage drop across it.



For dependent sources, always try to write an equation for unknown variable ( $V_1$  in this case).

$$V_1 = I_1(2) \text{ where } I_1 = 5A$$


$$\therefore V_1 = 10V$$

$$+I_2(5) - 3V_1 = 0 \text{ (v loop)}$$

$$I_2 = +\frac{30}{5} = \boxed{6A}$$

6. Use Kirchoff's laws and Ohm's Law to find  $I_2$  and  $V_4$  in the circuit below.

take current sum here.

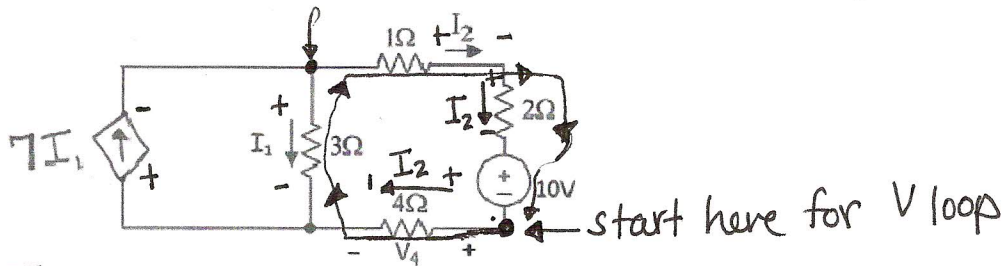

$\sum I:$

$$-7I_1 + I_1 + I_2 = 0 \rightarrow I_2 = +6I_1$$

V-loop:

$$-I_2(4) + I_1(3) - I_2(1) - I_2(2) - 10 = 0$$

$$-4I_2 + 18$$


$$-24I_1 + 3I_1 - 18I_1 - 10 = 0$$

$$I_1 = \frac{+10}{-39}$$

$$I_2 = -\frac{60}{39} \text{ A}$$

$$V_4 = I_2(4) = -\frac{240}{39} \text{ V}$$

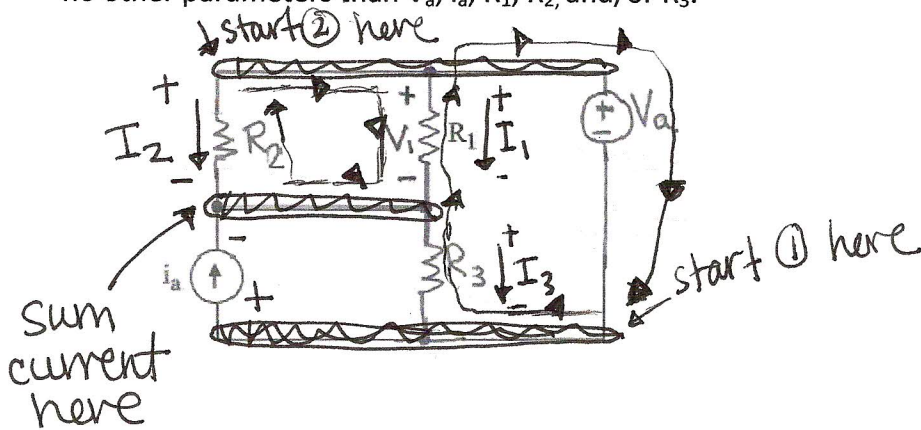7. Use Kirchoff's laws and Ohm's Law to find the expression for  $V_1$ . The expression can contain no other parameters than  $V_a$ ,  $i_a$ ,  $R_1$ ,  $R_2$ , and/or  $R_3$ .



$$-i_a - I_2 - I_1 + I_3 = 0 \rightarrow I_3 = i_a + I_1 + I_2$$

V-loop:

$$\textcircled{1} +I_3 R_3 + I_1 R_1 - V_a = 0$$

$$\textcircled{2} -I_1 R_1 + I_2 R_2 = 0$$

$$I_1 = \frac{I_2 R_2}{R_1} \quad I_2 = \frac{I_1 R_1}{R_2}$$

$$\text{plug into } I_3 \text{ eq: } I_3 = i_a + \frac{I_2 R_2}{R_1} + I_2 \frac{R_1}{R_1} = i_a + \frac{(R_1 + R_2)}{R_1} I_2$$

$$I_3 = i_a + I_1 + I_1 \frac{R_1}{R_2} = i_a + \frac{(R_1 + R_2)}{R_2} \cdot I_1$$


plug into  $\textcircled{1}$

$$i_a R_3 + \frac{(R_1 + R_2) R_3}{R_2} \cdot I_1 + I_1 R_1 - V_a = 0$$

$$I_1 \left[ \frac{(R_1 + R_2) R_3 + R_1 R_2}{R_2} \right] = V_a - i_a R_3$$

$$V_1 = I_1 R_1 = \frac{(V_a - i_a R_3) R_1 \cdot R_2}{(R_1 + R_2) R_3 + R_1 R_2}$$

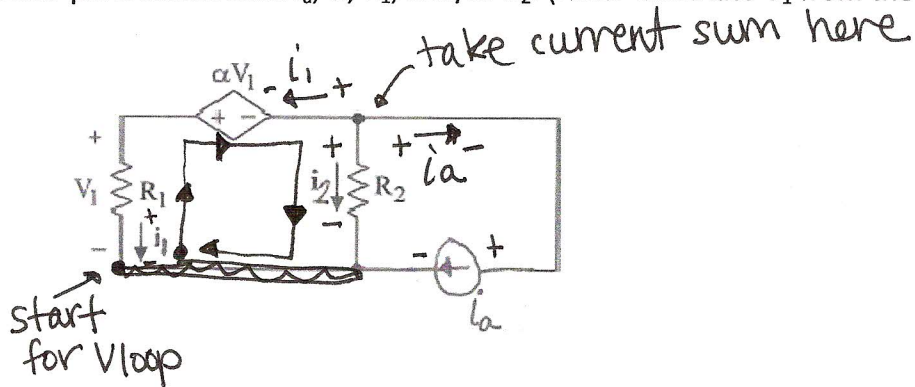8. Use Kirchoff's laws and Ohm's Law to find the expression for  $i_1$ . The expression can contain no other parameters than  $i_a$ ,  $\alpha$ ,  $R_1$ , and/or  $R_2$ . (Hint: Eliminate  $V_1$  from the expression)



Current sum:

$$+i_1 + i_2 + i_a = 0 \rightarrow i_2 = -i_a - i_1$$

V-loop:

$$+i_1 R_1 - \alpha V_1 - i_2 R_2 = 0$$


where  $V_1 = i_1 R_1$

$$\therefore i_1 R_1 - \alpha i_1 R_1 - i_2 R_2 = 0$$

$$i_1 (R_1 (1 - \alpha)) + i_a R_2 + i_1 R_2 = 0$$
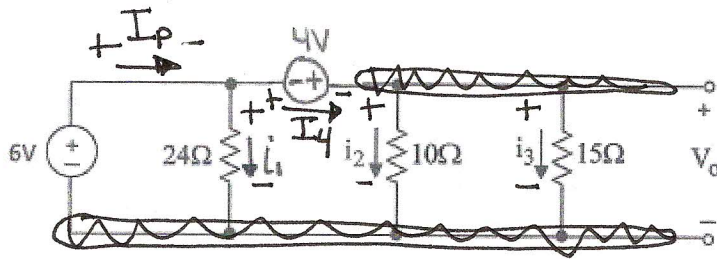
$$i_1 = \frac{i_a R_2}{R_1 (1 - \alpha) + R_2}$$



9. (a) Find  $i_1$ ,  $i_2$ ,  $i_3$ , and  $v_o$ .(b) Find the power dissipated in the  $24\Omega$  resistor and the power supply.

$$+6 - i_1(24) = 0$$

$$i_1 = \frac{6}{24} = \boxed{\frac{1}{4} \text{ A}}$$

$$+i_1(24) + 4 - i_2(10) = 0$$

$$\frac{1}{4}(24) + 4 - i_2(10) = 0$$

$$\therefore i_2 = \frac{10}{10} = \boxed{1 \text{ A}}$$

$$+i_2(10) - i_3(15) = 0$$

$$i_3 = \frac{i_2(10)}{15} = 1 \cdot \frac{10}{15} = \boxed{\frac{2}{3} \text{ A}}$$

$$v_o = i_3(15) \text{ or } i_2(10) = \frac{2}{3}(15) = \boxed{10 \text{ V}}$$

power in  $24\text{-}\Omega$  R:

$$P = i_1^2 R = \left(\frac{1}{4}\right)^2 \cdot 24 = \frac{24}{16} \cdot \frac{1}{4} = \boxed{\frac{3}{2} \text{ W}}$$

$$\sum I: -I_p + i_1 + I_4 = 0$$

$$-I_4 + i_2 + i_3 = 0 \rightarrow I_4 = i_2 + i_3$$

$$-I_p + i_1 + i_2 + i_3 = 0$$

$$I_p = i_1 + i_2 + i_3 = \frac{1(3)}{4(3)} + \frac{4(3)}{4(3)} + \frac{2(4)}{4(3)} = \frac{3+12+8}{12} = \frac{23}{12}$$

$$P_{6V \text{ supply}} = -\frac{23}{12} \cdot 6 = \boxed{-\frac{23}{2}}$$