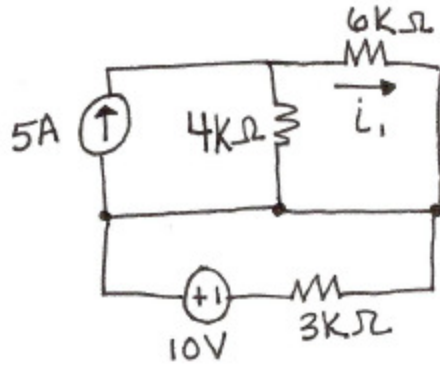
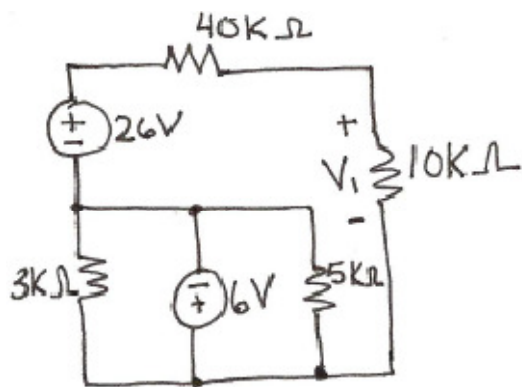




1.

Calculate i_1 .


2.

Calculate V_1 .

3. Find the total resistance between terminals a and b.

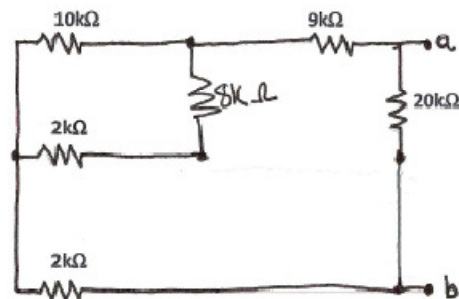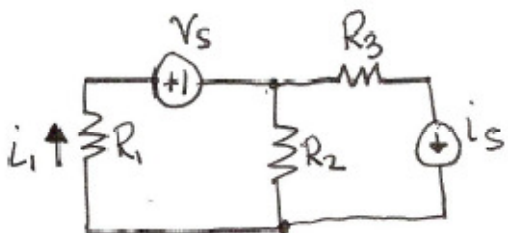4. Derive an expression for i_1 in the circuit below containing not more than circuit parameters R_1 , R_2 , R_3 , V_s , and/or i_s .


5.

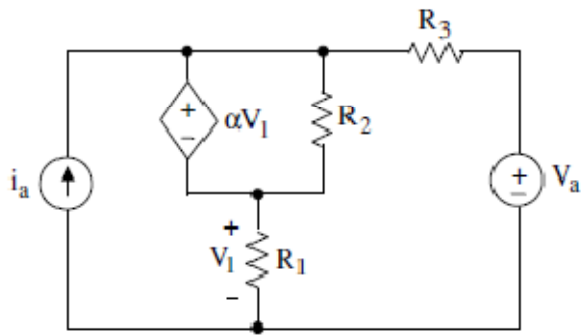


Derive the expression for V_1 containing not more than circuit parameters α , R_1 , R_2 , R_3 , V_a , and i_a .

6. Using the circuit shown in Problem #5, derive an expression for the power through R_2 . The known values are α , i_a , V_a , R_1 , R_2 and R_3 .

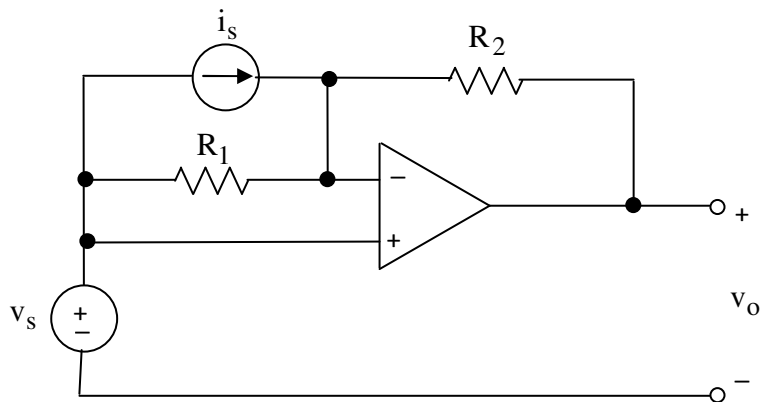
7. The op-amp operates in the linear mode. Using an appropriate model of the op amp, derive an expression for v_o in terms of not more than V_s , i_s , R_1 , and/or R_2 . Note that the current source is **not** ideal and has a voltage drop across it.



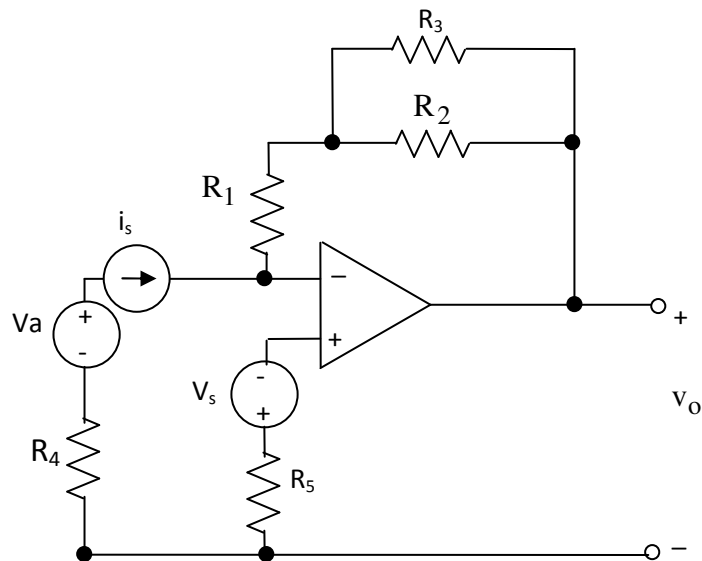8. The op-amp operates in the linear mode. Using an appropriate model of the op amp, derive an expression for v_o in terms of not more than V_a , V_s , i_s , R_1 , R_2 , R_3 , R_4 and R_5 . Note that the current source is **not** ideal and has a voltage drop across it.



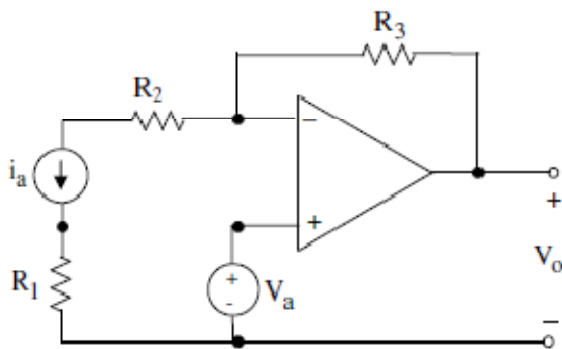9. The op-amp operates in the linear mode. Using an appropriate model of the op-amp, derive an expression for V_o in terms of not more than i_a , R_1 , R_2 , R_3 , and/or V_a . Note that the current source is **not** ideal and has a voltage drop across it.



10. The op-amp operates in the linear mode. Using an appropriate model of the op-amp, derive an expression for V_o in terms of not more than i_a , R_1 , R_2 , R_3 , and/or V_a . Note that the current source is **not** ideal and has a voltage drop across it. (*updated figure*)

