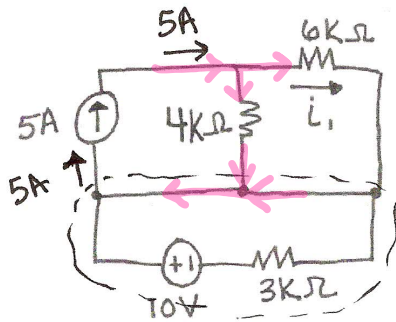
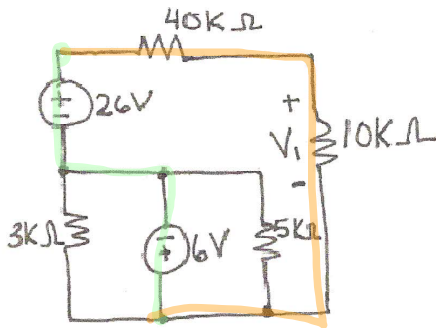
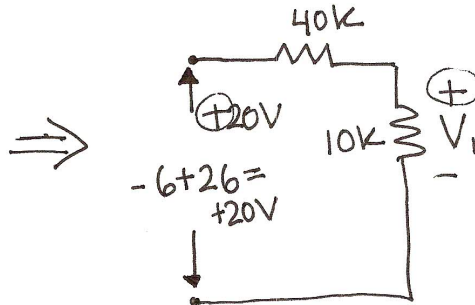


1.

Calculate  $i_1$ .

all of this  
combines current  
which then goes out -  
so 5A into parallel R's  
so splits current by  
divider:  $i_1 = \frac{5(4k)}{10k} = 2A$   
(current in)  
(opposite  
branch R)  
total R  
in both branches


2.

Calculate  $V_1$ .

Voltage divider:  
voltage across  
R's in series  
· signs closest are  
the same so +  
answer

$$V_1 = \frac{20(10k)}{50k} = 4V$$

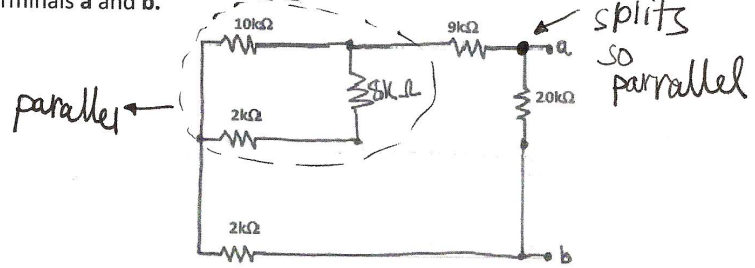3. Find the total resistance between terminals a and b.




$$R_{eq} = [9k + (8k + 2k) \parallel 10k + 2k] \parallel 20k$$

$$R_{eq} = [9k + \frac{1}{\frac{1}{10k} + \frac{1}{10k}} + 2k] \parallel 20k = [11k + 5k] \parallel 20k$$

$$R_{eq} = 16k \parallel 20k = \frac{1}{\frac{(20k)}{(20k)16k} + \frac{1}{20k(16k)}} = \frac{16k(20k)}{20k + 16k}$$

$$R_{eq} \cong \boxed{8.9k \Omega}$$

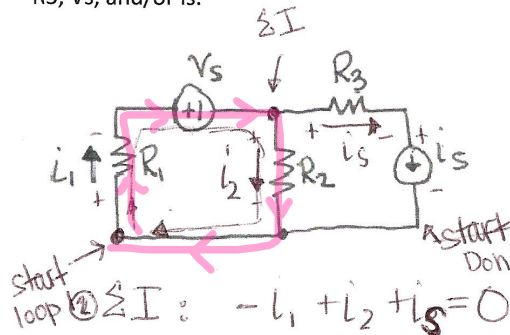4. Derive an expression for  $i_1$  in the circuit below containing not more than circuit parameters  $R_1$ ,  $R_2$ ,  $R_3$ ,  $V_s$ , and/or  $i_s$ .



Known values:

$$R_1, R_2, R_3, V_s, i_s$$

start loop 1  $\Sigma I: -i_1 + i_2 + i_s = 0$   
 start loop 2 Don't want to take a v-loop across  $i$  source.

$$\textcircled{1} \text{ V-loop: } -i_1 R_1 - V_s - i_2 R_2 = 0$$

$\textcircled{2}$

from  $\textcircled{2}$   $i_1 = i_2 + i_s$  plug into  $\textcircled{1}$

$$-(i_2 + i_s) R_1 - V_s - i_2 R_2 = 0$$


$$-i_2 (R_1 + R_2) = i_s R_1 + V_s$$

$$i_2 = -\frac{(i_s R_1 + V_s)}{R_1 + R_2}$$

$$\therefore i_1 = \frac{-(i_s R_1 + V_s)}{(R_1 + R_2)} + \frac{i_s (R_1 + R_2)}{R_1 + R_2}$$

$$i_1 = \frac{i_s R_2 - V_s}{(R_1 + R_2)}$$

5.

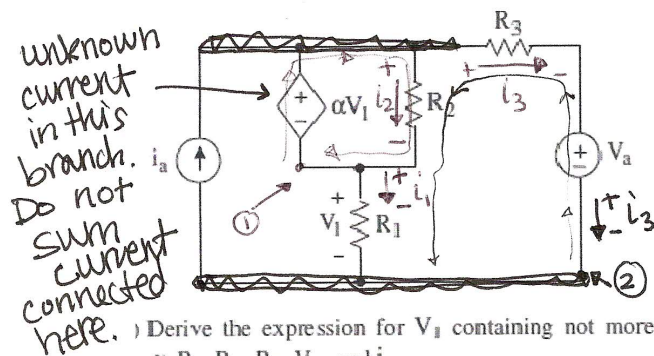

Derive the expression for  $V_1$  containing not more than circuit parameters  $\alpha$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $V_a$ , and  $i_a$ .

6. Using the circuit shown in Problem #5, derive an expression for the power through  $R_2$ . The known values are  $\alpha$ ,  $i_a$ ,  $V_a$ ,  $R_1$ ,  $R_2$  and  $R_3$ .

First write an equation for unknown  $V_1$ .

$$V_1 = i_1 R_1$$

$$\textcircled{1} +\alpha V_1 - i_2 R_2 = 0 \rightarrow i_2 = \frac{\alpha V_1}{R_2}$$

$$\textcircled{2} +V_a + i_3 R_3 - \alpha V_1 - i_1 R_1 = 0$$

$$+V_a + i_3 R_3 - \alpha (i_1 R_1) - i_1 R_1 = 0 \rightarrow i_3 = \frac{-V_a + i_1 R_1 (1 + \alpha)}{R_3}$$

$\sum I$  at  $\textcircled{2}$ :

$$+i_a - i_1 - i_3 = 0$$

$$i_3 = i_a - i_1 \text{ (set equal to )}$$


$$(i_a - i_1) = \frac{[-V_a + i_1 R_1 (1 + \alpha)]}{R_3}$$

$$(i_a + \frac{V_a}{R_3}) = i_1 \frac{R_1}{R_3} (1 + \alpha) + i_1 = i_1 \left[ 1 + \frac{R_1}{R_3} (1 + \alpha) \right]$$


$$V_1 = \frac{[R_3 i_a + V_a]}{[R_3 + R_1 (1 + \alpha)]} \cdot R_1$$

$$P_{i_2} = i_2^2 \cdot R_2 = \left[ \frac{\alpha (R_3 i_a + V_a) R_1}{[R_3 + R_1 (1 + \alpha)] R_2} \right]^2 \cdot R_2$$

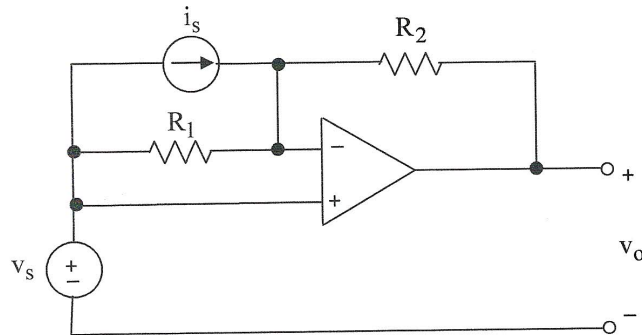7. The op-amp operates in the linear mode. Using an appropriate model of the op amp, derive an expression for  $v_o$  in terms of not more than  $V_s$ ,  $i_s$ ,  $R_1$ , and/or  $R_2$ . Note that the current source is **not** ideal and has a voltage drop across it.



Redraw:

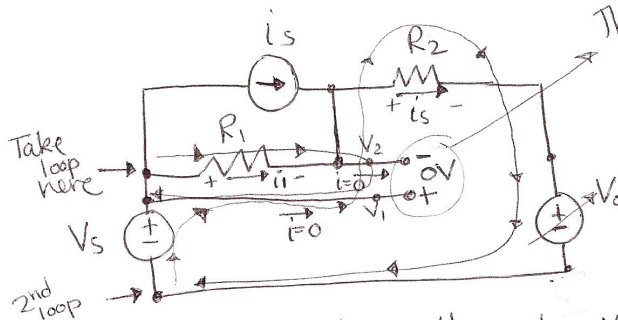

This is a "virtual" short that means 0V drop so  $V_1 = V_2$ . Also means no current from  $V_1$  to  $V_2$ .

• Taking a loop through  $V_2$  to  $V_1$ ,


$$-i_1 R_1 + 0 = 0 \quad \therefore \underline{i_1 = 0}$$

$\therefore i_s$  flows through  $R_2$ .


$$+V_s - 0 - i_s R_2 - V_o = 0$$

$$\boxed{V_o = V_s - i_s R_2}$$

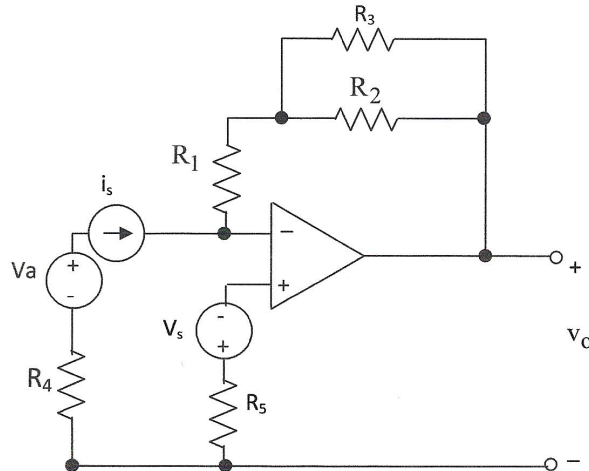8. The op-amp operates in the linear mode. Using an appropriate model of the op amp, derive an expression for  $v_o$  in terms of not more than  $V_a$ ,  $V_s$ ,  $i_s$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$  and  $R_5$ . Note that the current source is **not** ideal and has a voltage drop across it.



Redraw:

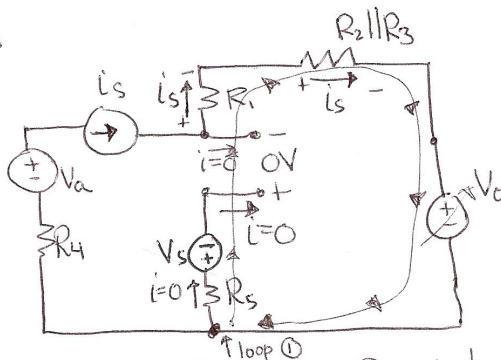


$i_s$  flows through  $R_1$  and  $R_2 \parallel R_3$  because  $i=0$  into op-amp.

$$\textcircled{1} -0 - V_s - 0 - i_s R_1 - i_s R_2 \parallel R_3 - V_o = 0$$


↑  
0 V drop across  $R_5$

$$\therefore V_o = -V_s - i_s R_1 - \frac{i_s R_2 R_3}{(R_2 + R_3)}$$

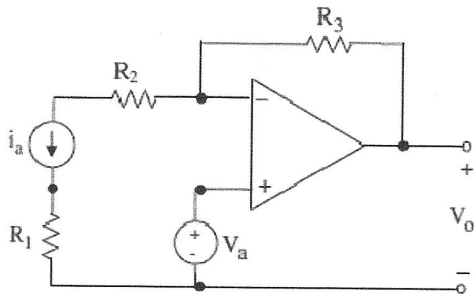9. The op-amp operates in the linear mode. Using an appropriate model of the op-amp, derive an expression for  $V_o$  in terms of not more than  $i_a$ ,  $R_1$ ,  $R_2$ ,  $R_3$ , and/or  $V_a$ . Note that the current source is **not** ideal and has a voltage drop across it.



Redraw:


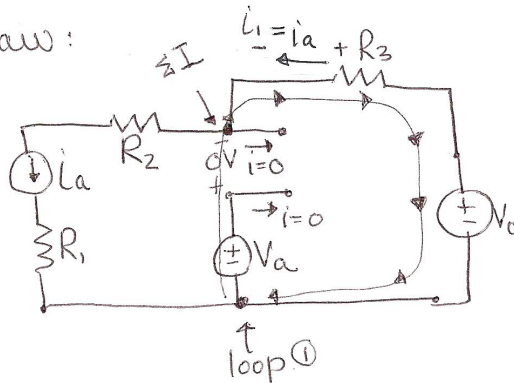


$$\sum I : +i_a + 0 - i_1 = 0 \quad \therefore i_1 = i_a$$

$$V\text{-loop} : +V_a - 0 + i_a R_3 - V_o = 0$$

$$\boxed{V_o = V_a + i_a R_3}$$

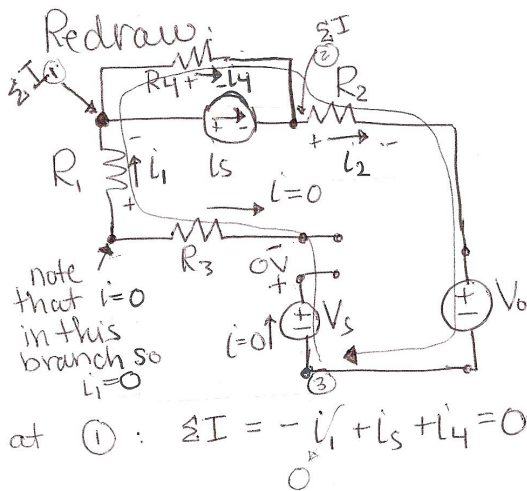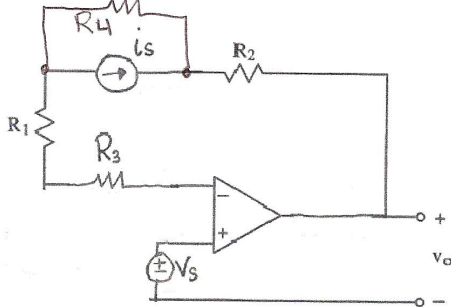10. The op-amp operates in the linear mode. Using an appropriate model of the op-amp, derive an expression for  $V_o$  in terms of not more than  $i_a$ ,  $R_1$ ,  $R_2$ ,  $R_3$ , and/or  $V_a$ . Note that the current source is **not** ideal and has a voltage drop across it.



at ②:  $\sum I \quad -i_s - i_4 + i_2 = 0$   
 $-i_s - (-i_s) + i_2 = 0 \quad \therefore i_2 = 0$

at ③ V-loop:  $+V_s - 0 + 0 - \frac{i_1}{0} R_1 - i_4 R_4 - \frac{i_2}{0} R_2 - V_o = 0$

$$\therefore \boxed{V_o = V_s + i_s R_4}$$