

1. a.  $v_1 = 0$   $\leftarrow -122 + 3 = -119V$



$v_2 \leftarrow +5 - 127 = -122V$




$v_3 \leftarrow -(-5) = +5$



Find the absolute voltages at all the labeled nodes in the circuit at the left. Hint: Start at the bottom (which is 0V) and work upwards.

b.

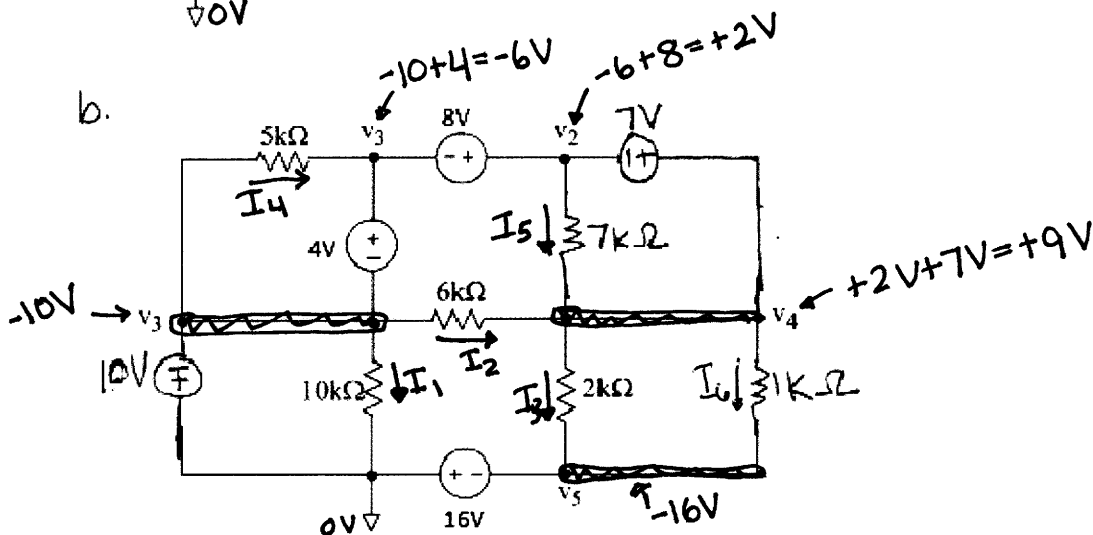

Find the absolute voltages at all the labeled nodes in the above circuit. Hint: This may be done by inspection.

c. Using Ohm's law and the node voltages found in part b, find the currents for all the resistors in part b.

$$I_1 = \frac{-10}{10k} = -1mA$$

$$I_6 = \frac{+9 - (-16)}{1k} = -7mA$$


$$I_2 = \frac{-10 - (+9)}{6k} = -\frac{19}{6}mA$$

$$I_3 = \frac{+9 - (-16)}{2k} = \frac{+25}{2}mA$$

$$I_4 = \frac{-10 - (-6)}{5k} = -\frac{4}{5}mA$$

$$I_5 = \frac{2 - 9}{7k} = -1mA$$

4.

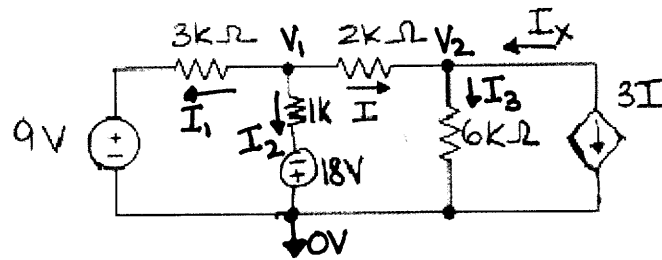

- a. Use the node-voltage method to determine  $I_x$ .
- b. Determine the amount of power in the dependent source.

$$I_1 = \frac{V_1 - 9}{3k}, \quad I_2 = \frac{V_1 - (-18)}{1k}, \quad I_3 = \frac{V_2}{6k}, \quad I = \frac{(V_1 - V_2)}{2k}$$

$$\textcircled{1} \text{ at } V_1: \frac{(V_1 - 9)}{3k} + \frac{V_1 - (-18)}{1k} + \frac{(V_1 - V_2)}{2k} = 0$$

$$\textcircled{2} \text{ at } V_2: -\frac{(V_1 - V_2)}{2k} + \frac{V_2}{6k} + 3 \cdot I = 0$$

$$\textcircled{1} V_1 \left( \underbrace{\frac{1}{3k} + \frac{1}{1k} + \frac{1}{2k}}_{1.83m} \right) - \frac{V_2}{2k} = -18m + 3m$$

$$\#4. \textcircled{1} V_1(1.83\text{m}) - \frac{V_2}{2\text{k}} = -15\text{m}$$

$$V_1 = \frac{V_2}{2\text{k} \cdot 1.83\text{m}} - \frac{15\text{m}}{1.83\text{m}} = 273\text{m} \cdot V_2 - 8.2$$

plug into  $\textcircled{2}$

$$-\frac{1}{2\text{k}} \cdot (273\text{m} \cdot V_2 - 8.2) + \frac{V_2}{2\text{k}} + \frac{V_2}{6\text{k}} + \frac{3 \cdot (273\text{m} \cdot V_2 - 8.2)}{2\text{k}} - \frac{3V_2}{2\text{k}} = 0$$

$$V_2(136.5\mu + 500\mu + 166.7\mu + 409.5\mu - 1.5\text{m}) = -4.1\text{m} + 12.3\text{m}$$


$$V_2 = \frac{8.2\text{m}}{-287.3\mu} = -28.5\text{V}$$

$$V_1 \hat{=} -16$$

$$I_x = -3I = -3 \frac{(V_1 - V_2)}{2\text{k}} = \frac{-3(-16 + 28.5)}{2\text{k}} = \boxed{-18.75\text{mA}}$$

$$\text{power} = 3 \cdot I \cdot V_2 = -I_x \cdot V_2 = 18.75\text{m} \cdot (-28.5) = \boxed{-534\text{mW}}$$

5.

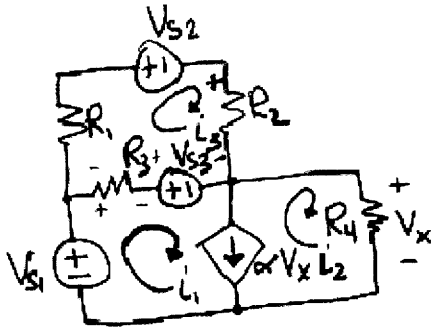

Use the mesh-current method to find  $i_1$  and  $i_2$ , and  $i_3$ .

$$\textcircled{1} \alpha V_x = i_1 - i_2$$

$$V_x = i_2 R_4$$

$$\textcircled{2} +V_{s1} + (i_3 - i_1)R_3 - V_{s3} - i_2 R_4 = 0$$

$$\textcircled{3} +V_{s3} + (i_1 - i_3)R_3 - i_3 R_1 - V_{s2} - i_3 R_2 = 0$$

$$\textcircled{1} i_1 = i_2 (\alpha R_4 + 1)$$

plug into  $\textcircled{2}$

$$V_{s1} + i_3 R_3 - i_2 R_3 (\alpha R_4 + 1) - V_{s3} - i_2 R_4 = 0$$

$$\textcircled{2} i_3 = \frac{V_{s3} - V_{s1} + i_2 [R_4 (\alpha R_3 + 1) + R_3]}{R_3}$$

plug  $\textcircled{1,2}$  into  $\textcircled{3}$

$$V_{s3} + i_2 R_3 (\alpha R_4 + 1) - V_{s2} + (-R_3 - R_1 - R_2) \frac{[V_{s3} - V_{s1} + i_2 [R_4 (\alpha R_3 + 1) + R_3]]}{R_3} = 0$$

#5. (cont.)

$$i_2 (R_3(\alpha R_4 + 1) - \frac{(R_1 + R_2 + R_3)}{R_3} [R_4(\alpha R_3 + 1) + R_3]) = -V_{s3} + V_{s2} + (R_1 + R_2 + R_3) \dots$$

$\dots \left[ \frac{V_{s3}}{R_3} - \frac{V_{s1}}{R_3} \right]$

$$i_2 = \frac{[-V_{s3} + V_{s2} + (R_1 + R_2 + R_3) \frac{V_{s3} - V_{s1}}{R_3}] \cdot R_3}{R_3(\alpha R_4 + 1)R_3 - (R_1 + R_2 + R_3)[R_4(\alpha R_3 + 1) + R_3]}$$


↓ reduced

$$i_2 = \frac{(-V_{s1} + V_{s2})R_3 + (R_1 + R_2)(V_{s3} - V_{s1})}{-R_4(R_1 + R_2 + R_3)}$$

$$i_1 = \frac{[(V_{s2} - V_{s1})R_3 + (V_{s3} - V_{s1})(R_1 + R_2)](\alpha R_4 + 1)}{-R_4(R_1 + R_2 + R_3)}$$

$$i_3 = \frac{V_{s3} - V_{s1}}{R_3} + \left[ \frac{(V_{s2} - V_{s1})R_3 + (R_1 + R_2)(V_{s3} - V_{s1})}{-R_4(R_1 + R_2 + R_3)} \right] \cdot \frac{[R_4(\alpha R_3 + 1) + R_3]}{R_3}$$

6.

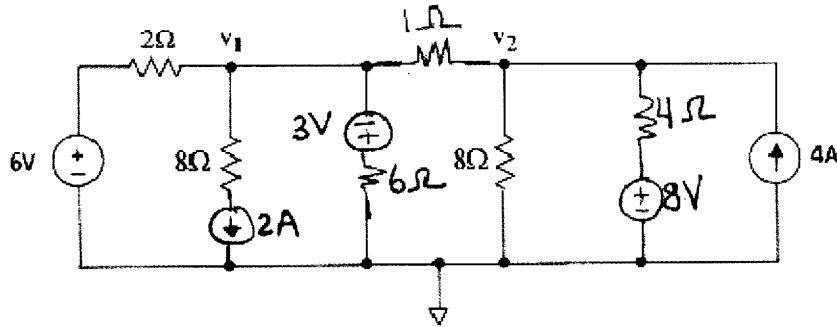

- Use the node-voltage method to find  $v_1$  and  $v_2$ .
- Determine the amount of power supplied by the 6V voltage source.

7. Use the mesh current method to solve Problem 6 to find  $v_1$  and  $v_2$ .

$$\textcircled{1} \frac{V_1 - 6}{2} + 2 + \frac{V_1 + 3}{6} + \frac{(V_1 - V_2)}{1} = 0$$

$$\textcircled{2} \frac{V_2 - V_1}{1} + \frac{V_2}{8} + \frac{(V_2 - 8)}{4} - 4 = 0$$

$$\text{From } \textcircled{1}: V_1 \left( \frac{1}{2} + \frac{1}{6} + 1 \right) = +3 - 2 + \frac{1}{2} + V_2$$

$$V_1 \left( \underbrace{\frac{3}{6} + \frac{1}{6} + \frac{6}{6}}_{\frac{10}{6}} \right) = \frac{6}{2} - \frac{4}{2} + \frac{1}{2} + V_2 = \frac{3}{2} + V_2$$

$$V_1 = \frac{3}{2} \cdot \frac{6}{10} + V_2 \cdot \frac{6}{10} = \frac{9}{10} + \frac{3}{5} \cdot V_2$$

plugging into  $\textcircled{2}$ :

$$V_2 \left( 1 + \frac{1}{8} + \frac{1}{4} \right) - \frac{9}{10} - \frac{3}{5} \cdot V_2 = +2 + 4$$

$$V_2 \left[ \frac{40}{40} + \frac{5}{40} + \frac{10}{40} - \frac{24}{40} \right] = \frac{9}{10} + \frac{20}{10} + \frac{40}{10}$$

$$V_2 \left( \frac{31}{40} \right) = \frac{69}{10} \cdot \frac{40}{31} = 8.9V$$

#6. (cont.)


$$V_2 = \boxed{8.9V}$$

$$V_1 = \frac{9}{10} + \frac{3}{5}(8.9) = \boxed{6.24V}$$

power in 6V supply:

$$\text{current} = \frac{V_1 - 6}{2} = \frac{6.24 - 6}{2} = -.120A$$

$$p = (+6)(-.120) = \boxed{-0.720W}$$

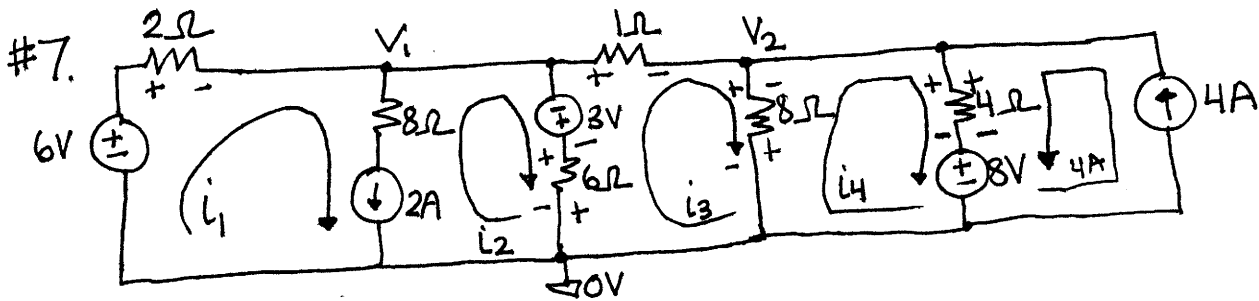

$$\textcircled{1} 2 = (i_1 - i_2)$$

$$\textcircled{2} +6 - i_1(2) + 3 - i_2(6) + i_3(6) = 0$$

$$\textcircled{3} (+i_3 - i_4)8 - (i_4 + 4)4 - 8 = 0$$

$$\textcircled{4} +6 - i_1(2) - i_3 - (i_4 + 4)4 - 8 = 0$$

From  $\textcircled{1}$   $i_1 = (2 + i_2)$ , plug into  $\textcircled{2}$ :  $6 - 2(2 + i_2) + 3 - 6i_2 + i_3(6) = 0$

$$+5 - 2i_2 - 6i_2 + 6i_3 = 0$$

$$+5 - 8i_2 + 6i_3 = 0 \rightarrow 6i_3 = \frac{8i_2 - 5}{6}$$

plug into  $\textcircled{3}$

$$\left(\frac{8i_2}{6} - \frac{5}{6}\right)8 - 4 \cdot 8 - 4i_4 - 16 - 8 = 0$$

$$i_4 = \frac{+24 + \frac{40}{6} - \frac{64i_2}{6}}{-12} = -2 - \frac{10}{6 \cdot 3} + \frac{64i_2}{6 \cdot 12}$$

plug all into  $\textcircled{4}$ :

#6. (cont.)

$$+6 - 2(2 + i_2) - \frac{8}{6} i_2 - \frac{5}{6} - 4\left(-2 - \frac{10}{18} + \frac{64i_2}{6 \cdot 12}\right) - 16 - 8 = 0$$

$$i_2\left(-2 - \frac{8}{6} - \frac{4(64)}{6 \cdot 12}\right) = -6 + 4 + \frac{5}{6} - 8 - \frac{40}{18} + 16 + 8$$

$$-i_2(3.3 + 3.556) = +14 + 0.833 - 2.22$$

$$i_2 = \frac{+12.61}{-6.856} = -1.84$$

$$i_1 = 2 + i_2 = +0.160$$

$$i_3 = \frac{8(-1.84) - 5}{6} = -3.3$$


$$i_4 = -2 - \frac{10}{18} + \frac{64(-1.84)}{6 \cdot 12} = -2 - 0.556 - 1.64 = -4.2$$

$$V_1 = +6 - 2(i_1) = \boxed{+5.68V}$$

$$V_2 = (+i_3 - i_4)8 = (-3.3 + 4.2)8 = \boxed{+7.2V}$$



8.

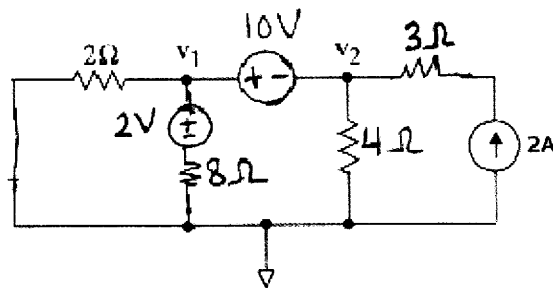

Use either the node-voltage method or current mesh method to find  $v_1$  and  $v_2$ .

$$\frac{V_1}{2} + \frac{(V_1 - 2)}{8} + \frac{V_2}{4} - 2 = 0$$

$$(+V_1 - V_2) = +10$$

$$V_1 = 10 + V_2$$

$$\frac{10}{2} + \frac{V_2}{2} + \frac{10}{8} + \frac{V_2}{8} - \frac{1}{4} + \frac{V_2}{4} - 2 = 0$$

$$V_2 \left( \frac{1}{2} + \frac{1}{8} + \frac{1}{4} \right) = -5 - \frac{10}{8} + \frac{1}{4} + 2$$


$$V_2 \left( \frac{4}{8} + \frac{1}{8} + \frac{2}{8} \right) = \frac{-40 - 10 + 2 + 16}{8} = \frac{-4(8)}{8}$$

$\underbrace{\hspace{1.5cm}}_{\frac{7}{8}}$

$$V_2 = -4.57V$$

$$V_1 = +5.43V$$

9.

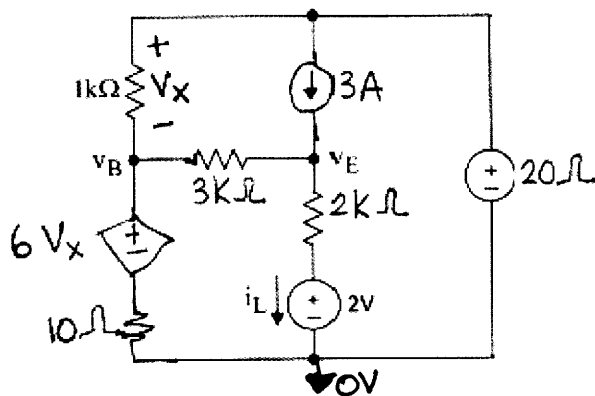

Use the node-voltage method to find  $v_1$  and  $v_2$ .

10. Solve Problem 9 using the mesh current method to find  $v_1$  and  $v_2$ .

$$\#9. \frac{(V_B - 6V_x)}{10} + \frac{(V_B - V_E)}{3k} + \frac{(V_B - 20)}{1k} = 0$$

$$(20 - V_B) = V_x$$

$$\textcircled{1} \frac{(V_B - 6(20 - V_B))}{10} + \frac{(V_B - V_E)}{3k} + \frac{(V_B - 20)}{1k} = 0$$

$$\textcircled{2} \frac{(V_E - V_B)}{3k} - 3 + \frac{(V_E - 2)}{2k} = 0$$

$$V_E \left( \frac{1}{3k} + \frac{1}{2k} \right) = \frac{V_B}{3k} + 3 + \frac{1}{1k}$$

$$V_E (333\mu + 500\mu) = 333\mu V_B + 3.001$$

$$V_E = 0.4V_B + 3.6k$$


$$\text{plug into } \textcircled{1}: \frac{V_B}{10} - \frac{120}{10} + \frac{6V_B}{10} + \frac{V_B}{3k} - \frac{0.4V_B}{3k} - \frac{3.6k}{3k} + \frac{V_B}{1k} - \frac{20}{1k} = 0$$

$$V_B \left( \frac{1}{10} + \frac{6}{10} + \frac{1}{3k} - \frac{0.4}{3k} + \frac{1}{1k} \right) = +12 + \frac{3.6k}{3k} + \frac{20}{1k}$$

$$V_B (0.7) = 13.22 \rightarrow \boxed{V_B = 18.9V}$$

$$\boxed{V_E \approx 3.6k}$$

9.

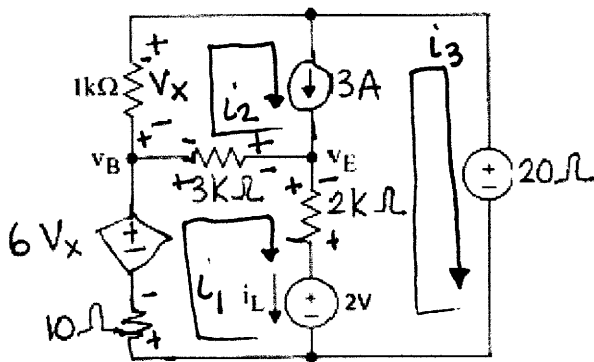

Use the node-voltage method to find  $v_1$  and  $v_2$ .

10. Solve Problem 9 using the mesh current method to find  $v_1$  and  $v_2$ .

$$\#10. \textcircled{1} 3 = i_2 - i_3 \rightarrow i_3 = (i_2 - 3)$$

$$V_x = -i_2(1k)$$

$$\textcircled{2} -i_1(10) + 6(-i_2(1k)) - i_2(1k) - 20 = 0$$

$$\textcircled{3} -i_1(10) + 6(-i_2(1k)) + 3k(i_2 - i_1) + 2k(+i_3 - i_1) - 2 = 0$$

plug  $\textcircled{1}$  into  $\textcircled{3}$ :

$$-i_1(10) - i_2(6k) + i_2(3k) - i_1(3k) + 2k(i_2 - 3) - i_1(2k) - 2 = 0$$

$$i_1(-10 - 3k - 2k) = +2 + i_2(-6k + 3k + 2k) + 6k$$

$$i_1 = \frac{6,002 + i_2(-1k)}{-5,010}$$

plug into  $\textcircled{2}$ :

$$\left[ \frac{-6,002 + i_2(-1k)}{-5,010} \right] \cdot 10 - 6k i_2 - 1k i_2 - 20 = 0$$

$$i_2 \left( +\frac{1k \cdot 10}{5,010} - 6k - 1k \right) = +20 + \frac{6,002 \cdot 10}{-5,010}$$

$$i_2(-7k) = 8.02 \Rightarrow i_2 = -1.1m, i_1 = 1.2mA, i_3 \approx -3$$

$$V_B = +20 + i_2(1k) = \boxed{+18.9V}$$