
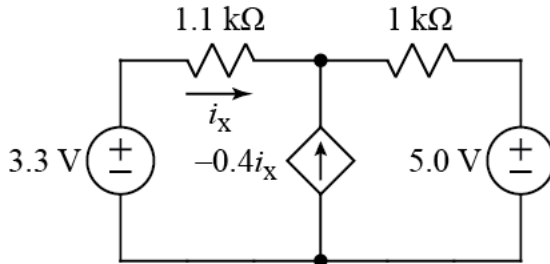


Ex:

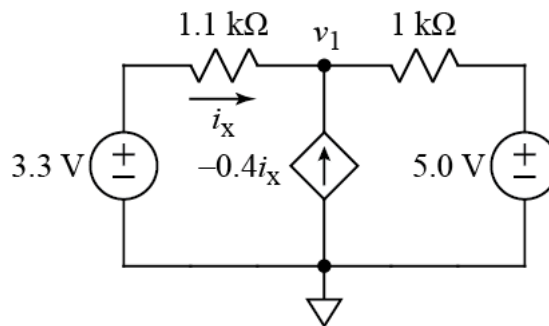

Calculate the power consumed (i.e., dissipated) by the 3.3 V source. **Note:** If a source supplies power, the power it consumes is negative.

SOL'N: Any valid method of solution may be used. Here, the node-voltage method is used. We define a reference node and a v_1 node.



We define the variable, i_x , for the dependent source in terms of the node-voltage.

$$i_x = \frac{3.3 \text{ V} - v_1}{1.1 \text{ k}\Omega}$$

Now we sum the current out of the v_1 node.

$$\frac{v_1 - 3.3 \text{ V}}{1.1 \text{ k}\Omega} - 0.4 \left(\frac{3.3 \text{ V} - v_1}{1.1 \text{ k}\Omega} \right) + \frac{v_1 - 5.0 \text{ V}}{1 \text{ k}\Omega} = 0 \text{ A}$$

or

$$v_1 \left(\frac{1}{1.1 \text{ k}\Omega} - 0.4 \frac{1}{1.1 \text{ k}\Omega} + \frac{1}{1 \text{ k}\Omega} \right) = \frac{3.3 \text{ V}}{1.1 \text{ k}\Omega} - 0.4 \frac{3.3 \text{ V}}{1.1 \text{ k}\Omega} + \frac{5.0 \text{ V}}{1 \text{ k}\Omega}$$

or, if we multiply both sides by 1.1 kΩ

$$v_1 (1 - 0.4 + 1.1) = 3.3 \text{ V} + 0.4(3.3 \text{ V}) + 5.5 \text{ V}$$

or

$$v_1(1.7) = 1.98 + 5.5 \text{ V} = 7.48 \text{ V}$$

or

$$v_1 = \frac{7.48 \text{ V}}{1.7} = 4.4 \text{ V}$$

The power in the 3.3 V source is $p = -i_x \cdot 3.3 \text{ V}$. We now calculate i_x .

$$i_x = \frac{3.3 \text{ V} - 4.4 \text{ V}}{1.1 \text{ k}\Omega} = -1 \text{ mA}$$

Finally, we calculate the power:

$$p = iv = -i_x 3.3 \text{ V} = 1 \text{ mA} \cdot 3.3 \text{ V} = 3.3 \text{ mW}$$