
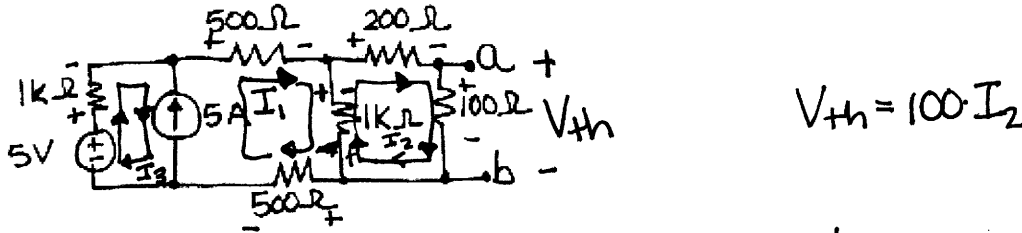


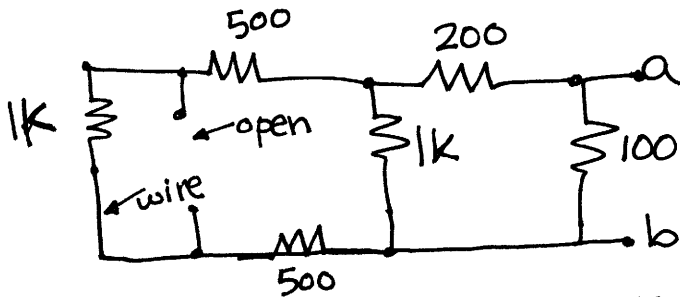1. Find the Thevenin equivalent circuit between terminals a-b.



Circuit contains only independent source.

(Short all independent sources: (V=0) becomes wire
(I=0) becomes open)



$$R_{th} = 100 \parallel \left[200 + \frac{2k \cdot 1k}{3k} \right] = 100 \parallel 867 = \frac{100(867)}{967} \approx \underline{\underline{89.6 \Omega}}$$

Using mesh current method:

$$\textcircled{1} +5 - I_3(1k) - 500I_1 - 200I_2 - 100I_2 - 500I_1 = 0$$

$$\textcircled{2} 5A = I_1 - I_3 \rightarrow I_3 = I_1 - 5A$$

$$\textcircled{3} +5 - I_3(1k) - 500I_1 - 1kI_1 + 1kI_2 - 500I_1 = 0$$

$$\textcircled{4} +1k(I_1) - 1k(I_2) - 200I_2 - 100I_2 = 0 \rightarrow \dots$$


$$I_2 = \frac{1kI_1}{1.3k}$$

use $\textcircled{2}, \textcircled{4}$ & plug into $\textcircled{3}$


$$+5 - 1k(I_1 - 5) - 500I_1 - 1.5kI_1 + 1k \left(\frac{1kI_1}{1.3k} \right) = 0$$

$$I_1 \left(1k + 500 + 1.5k - \frac{1k}{1.3} \right) = 5 + 5k \rightarrow I_1 = 2.24$$
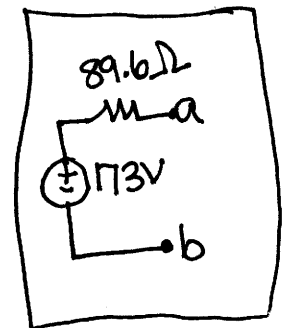
$$\therefore I_2 = 2.24 \left(\frac{1}{1.3} \right) = 1.73 \rightarrow V_{th} = 173V$$



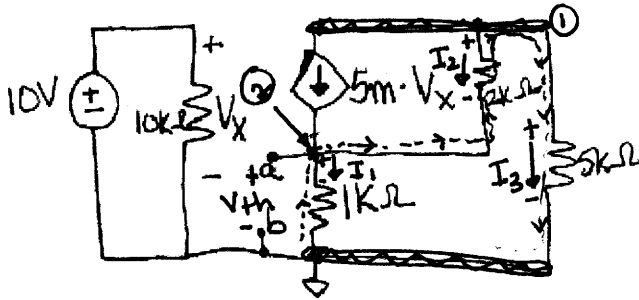2. Find the Thevenin equivalent circuit between terminals a-b.



$$V_x = 10V$$

$$V_{th} = I_1(1k)$$

$$V_{loop} = +I_1(1k) + I_2(2k) - I_3(5k) = 0$$

$$\text{at } \textcircled{1} \sum I: +5m + I_2 + I_3 = 0 \rightarrow I_3 = -I_2 - 50m$$

$$\text{at } \textcircled{2} \sum I: -5m + I_1 - I_2 = 0 \rightarrow I_1 = I_2 + 50m$$

$$1k(I_2 + 50m) + 2k(I_2) - 5k(-I_2 - 50m) = 0$$

$$I_2(1k + 2k + 5k) = -1k(50m) - 5k(50m)$$

$$I_2(8k) = -50 - 250 = -\frac{300}{8k} = -37.5mA$$



$$I_1 = -37.5m + 50m = +12.5mA$$

$$V_{th} = 12.5m(1k) = 12.5V$$


Using a test source:

$$I_{test} = \frac{1}{1k \parallel 7k}$$
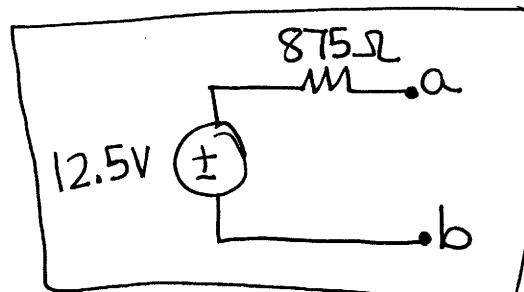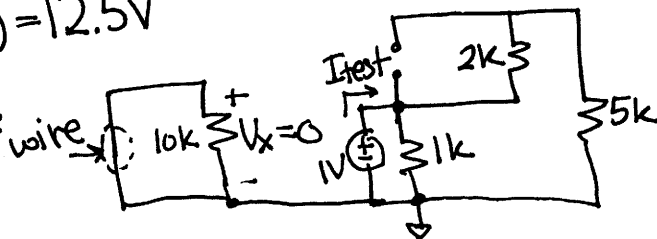
$$R_{th} = 1k \parallel 7k = \frac{1k(7k)}{8k} = 875\Omega$$



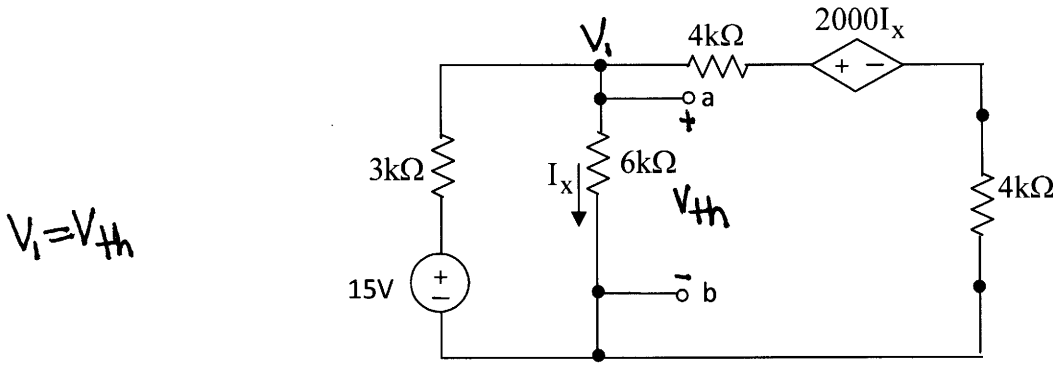3. Determine the Thevenin equivalent circuit between terminals a-b.




$V_1 = V_{th}$

$$\frac{(V_1 - 15)}{3k} + \frac{V_1}{6k} + \frac{V_1 - 2000(\frac{V_1}{6k})}{8k} = 0$$

$$V_1 \left(\frac{1}{3k} + \frac{1}{6k} + \frac{1}{8k} - \frac{2k}{6k \cdot 8k} \right) = \frac{+15}{3k}$$

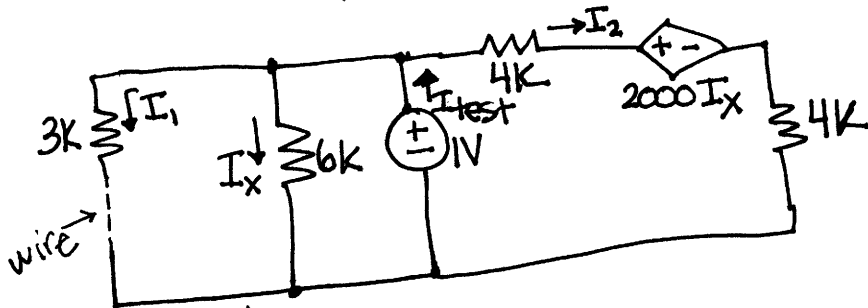where $V_1 = \frac{15}{3k(5.833 \times 10^{-4})} = 8.57V$




$I_x = \frac{1}{6k}$


$$+\frac{(1)}{3k} + \frac{1}{6k} - I_{test} + \frac{(1 - 2000(\frac{1}{6k}))}{8k} = 0$$

$$I_{test} = 3.33 \times 10^{-4} + 1.667 \times 10^{-4} + 8.33 \times 10^{-5} = 5.83 \times 10^{-4}$$
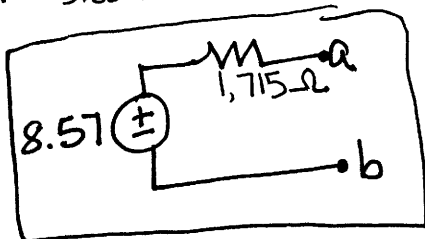
$$R_{th} = \frac{1}{5.83 \times 10^{-4}} = 1,715$$



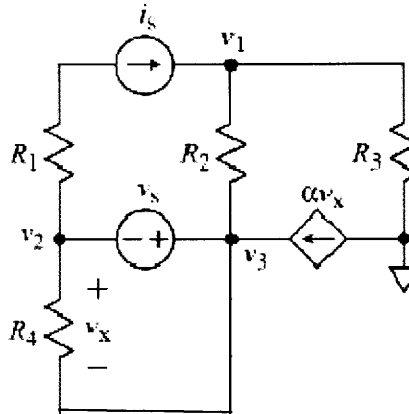4. For the circuit shown, write three independent equations for the node voltages v_1 , v_2 , and v_3 . The quantity V_x must not appear in the equations.



5. Solve the equations in Problem 4 to find v_1 , v_2 , and v_3
6. From Problem 4, calculate the power in the dependent source. State whether it is consuming or producing power.

$$\textcircled{1} -i_s + \frac{(v_2 - v_3)}{R_2} + \frac{v_1}{R_3} = 0$$

$$\textcircled{2} \frac{(v_2 - v_3)}{R_4} + i_s + \frac{(v_3 - v_1)}{R_2} + \frac{(v_3 - v_2)}{R_4} - \alpha(v_2 - v_3) = 0$$

$$v_s = v_3 - v_2 \rightarrow v_2 = v_3 - v_s$$

$$\textcircled{2} +i_s + \frac{(v_3 - v_1)}{R_2} - \alpha(-v_s) = 0$$

$$v_1 = i_s R_2 + \alpha v_s R_2 + v_3$$

plug into $\textcircled{1}$

$$-i_s + \frac{(v_3 - v_s - v_3)}{R_2} + \frac{(i_s R_2 + \alpha v_s R_2 + v_3)}{R_3} = 0$$

$$v_3 = i_s R_3 + \frac{v_s R_3}{R_2} - i_s R_2 - \alpha v_s R_2$$

$$v_1 = i_s R_3 + \frac{v_s R_3}{R_2}$$

$$v_2 = i_s R_3 + \frac{v_s R_3}{R_2} - i_s R_2 - \alpha v_s R_2 - v_s$$

#6 power is $\alpha V_x (-V_3)$


$$V_x = -V_s$$

$$\text{power} = \alpha (-V_s) \left[i_s R_3 + \frac{V_s R_3}{R_2} - i_s R_2 - \alpha V_s R_2 \right]$$

if $\left[i_s R_3 + \frac{V_s R_3}{R_2} - i_s R_2 - \alpha V_s R_2 \right] > 0$ then it is producing

if $\left[i_s R_3 + \frac{V_s R_3}{R_2} - i_s R_2 - \alpha V_s R_2 \right] < 0$ then it is consuming

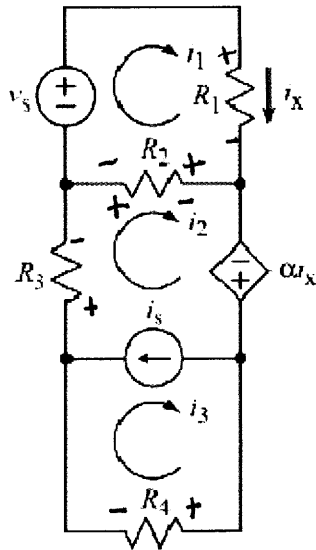7. For the circuit shown, write three independent equations for the three mesh currents, i_1 , i_2 , and i_3 . The quantity i_x must not appear in the equations.



8. Solve the equations in Problem 7 to find i_1 , i_2 , and i_3 .

$$i_x = i_1$$

$$i_s = (i_2 - i_3) \rightarrow i_3 = (i_s + i_2)$$

$$+V_s - i_1 R_1 + R_2(i_2 - i_1) = 0 \rightarrow i_1(R_1 + R_2) = \frac{i_2 R_2 + V_s}{(R_1 + R_2)}$$

$$-R_4(i_3) - R_3(i_2) + R_2(i_1 - i_2) + \alpha i_1 = 0$$

$$-R_4(i_2 - i_s) - i_2 R_3 + R_2\left(\frac{i_2 R_2 + V_s}{(R_1 + R_2)}\right) - i_2 R_2 + \alpha\left(\frac{i_2 R_2 + V_s}{(R_1 + R_2)}\right) = 0$$

$$i_2\left(R_4 + R_3 - \frac{R_2 \cdot R_2}{(R_1 + R_2)} + R_2 - \frac{\alpha R_2}{(R_1 + R_2)}\right) = +i_s R_4 + \frac{V_s R_2}{(R_1 + R_2)} + \frac{\alpha V_s}{(R_1 + R_2)}$$

$$i_2 = \frac{i_s R_4 (R_1 + R_2) + V_s (R_2 + \alpha)}{R_1 + R_2} \cdot \frac{(R_1 + R_2)}{(R_2 + R_3 + R_4)(R_1 + R_2) - R_2 R_2 - \alpha R_2}$$

$$i_3 = (\quad) - i_s$$

#8. (cont.)

$$i_1 = \frac{V_s}{(R_1 + R_2)} + \frac{R_2}{(R_1 + R_2)} \cdot \frac{i_s R_4 (R_1 + R_2) + V_s (R_2 + \alpha)}{[(R_2 + R_3 + R_4)(R_1 + R_2) - R_2 (R_2 + \alpha)]}$$